

LECTURE 12

Soo-Won Kim
swkim@korea.ac.kr

16. Nyquist-Rate D/A Converters

16.1 Decoder-Based Converters

16.2 Binary-Scaled Converters



Resistor-String Converters

The most straightforward approach = **Decoder-based converters**

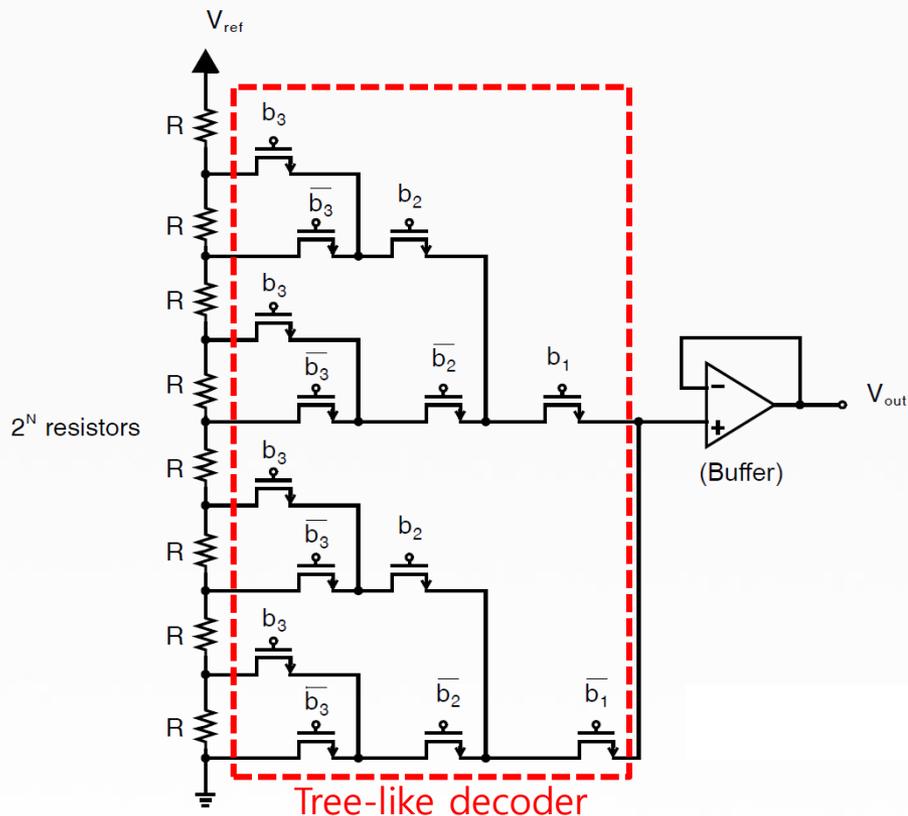


Fig. 16.1 Resistor-string 3-bit D/A converter with a transmission-gate, tree-like decoder

➡ $V_{out} = b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3}$

스위치의 ON/OFF 동작에 따라 저항에 연결된 전압 중에 오직 하나만이 출력으로 나온다. 이를 아날로그 버퍼에 연결함으로써 원하는 아날로그 전압을 얻는다.


😊 Monotonic
 Accuracy (depend on R)

😞 **Limitation on speed**
 Power consumption
 Require 2^N resistors



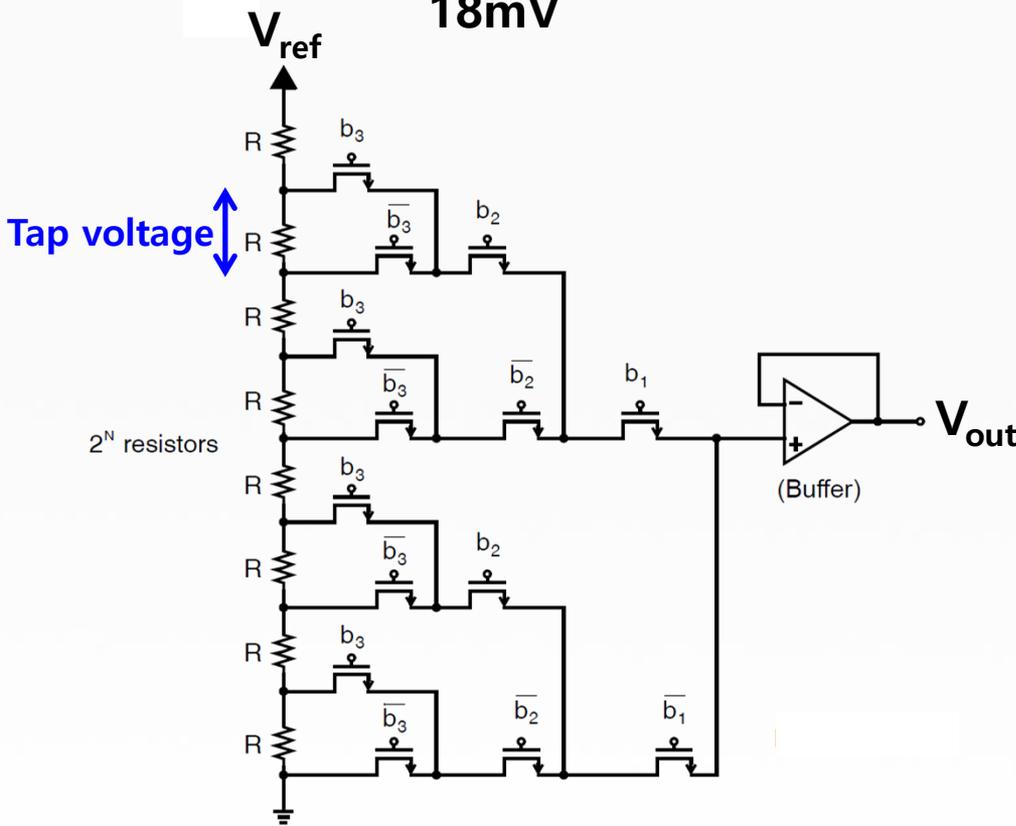Example 1


Calculate (a) The **tap voltage** from the resistor string if $V_{ref} = 5V$
 (b) The **output voltage** if the op-amp has an offset voltage of **18mV**



Input Binary Bits			Tap voltage	V_{out}
b_3	b_2	b_1		
0	0	0	0	0.018
0	0	1	0.625	0.643
0	1	0	1.25	1.268
0	1	1	1.875	1.893
1	0	0	2.5	2.518
1	0	1	3.125	3.143
1	1	0	3.75	3.768
1	1	1	4.375	4.393


Fig. 16.1 Resistor-string 3-bit D/A converter with a transmission-gate, tree-like decoder

➡ Need to reduce the offset voltage

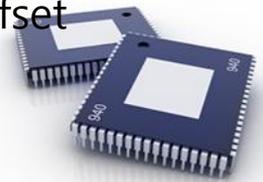

Resistor-String Converters

Large series resistors → one resistor

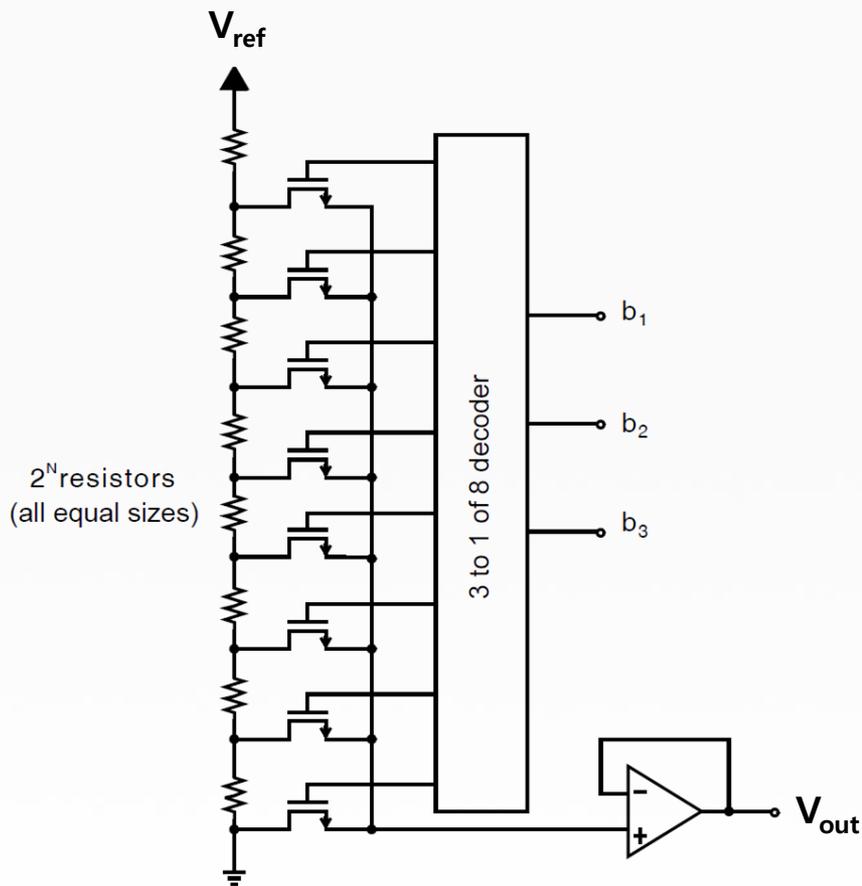

➡ $V_{out} = b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3}$

스위치가 직렬로 여러 단을 연결되면 동작속도가 기하급수적으로 느려진다. 이를 개선하기 위해 디지털 Decoder 를 설계한다.



Switch resistors ↓
Speed ↑



Large capacitive loading
Digital decoder area

Fig. 16.2 Resistor-string 3-bit D/A converter with digital decoding



Folded Resistor-String Converters

To reduce the amount of digital decoding and large capacitive loading

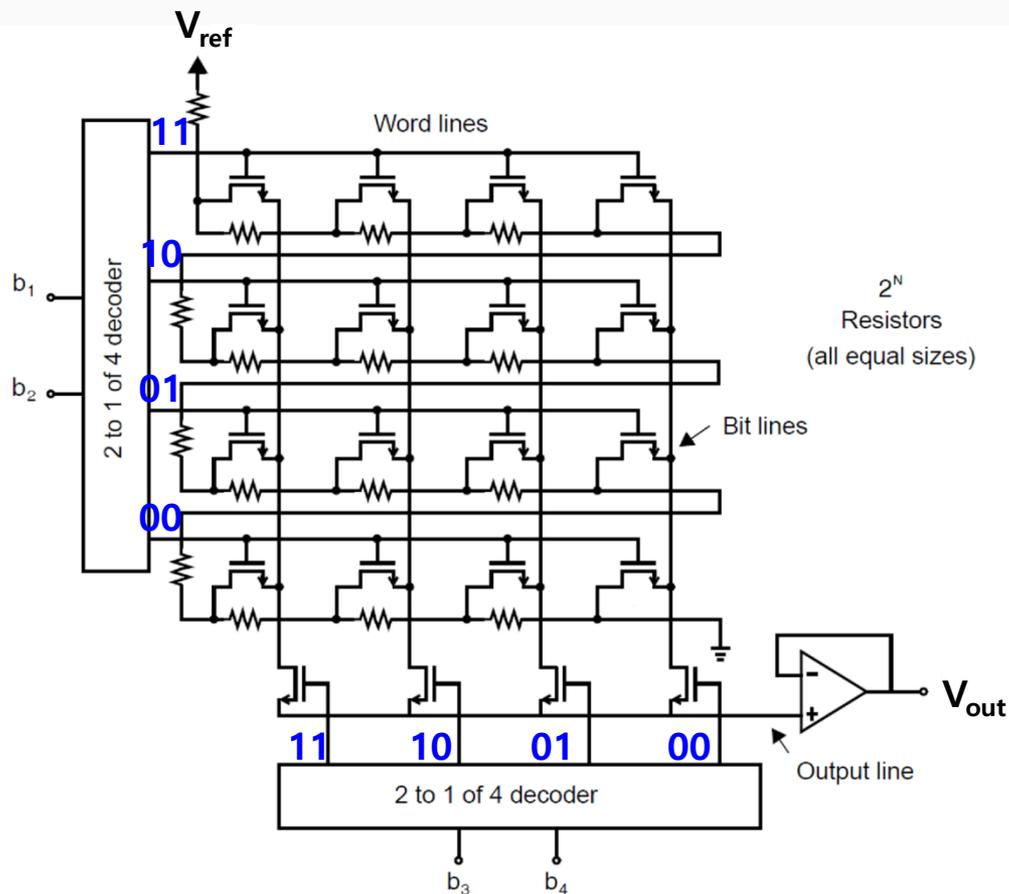


Fig. 16.4 A 4-bit folded resistor-string D/A converter

Similar to digital memory

➡ $V_{out} = b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3} + b_4 2^{-4}$

- 😊 - Reduce the decoding area
- 😊 - Reduce the capacitive loading
- 😞 - Power consumption
- ➡ - **Require 2^N resistors**



Multiple Resistor-String Converters

To reduce the amount of resistors

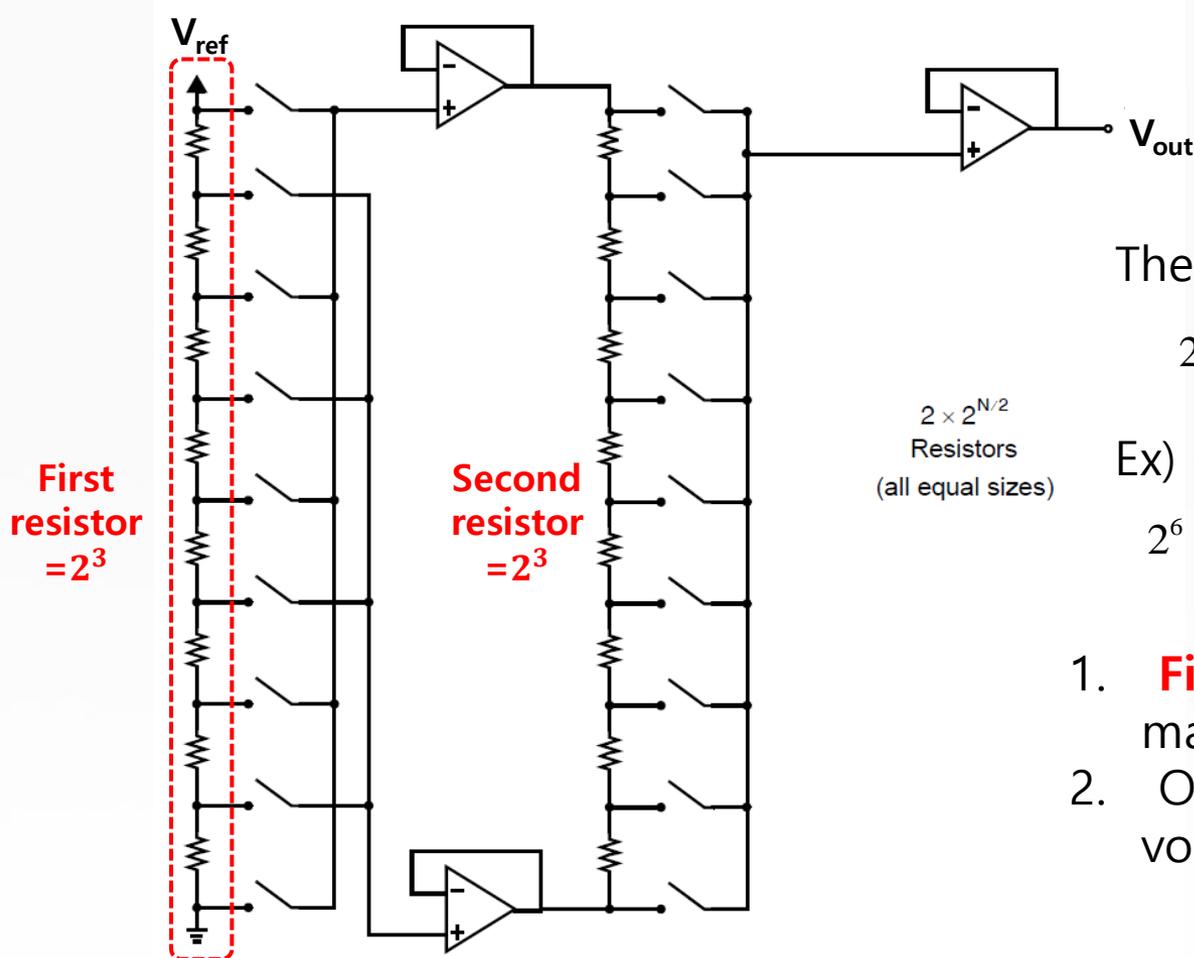


Fig. 16.5 Multiple R-string 6-bit D/A converter

The amount of resistors

$$2^N \rightarrow 2 \times 2^{N/2}$$

Ex) 6bit


$$2^6 = 64 \leftrightarrow 2 \times 2^{6/2} = 16$$

1. **First resistor** string should be matched
2. Opamps should have matched, voltage insensitive offset voltage



Multiple Resistor-String Converters

At binary code=001010

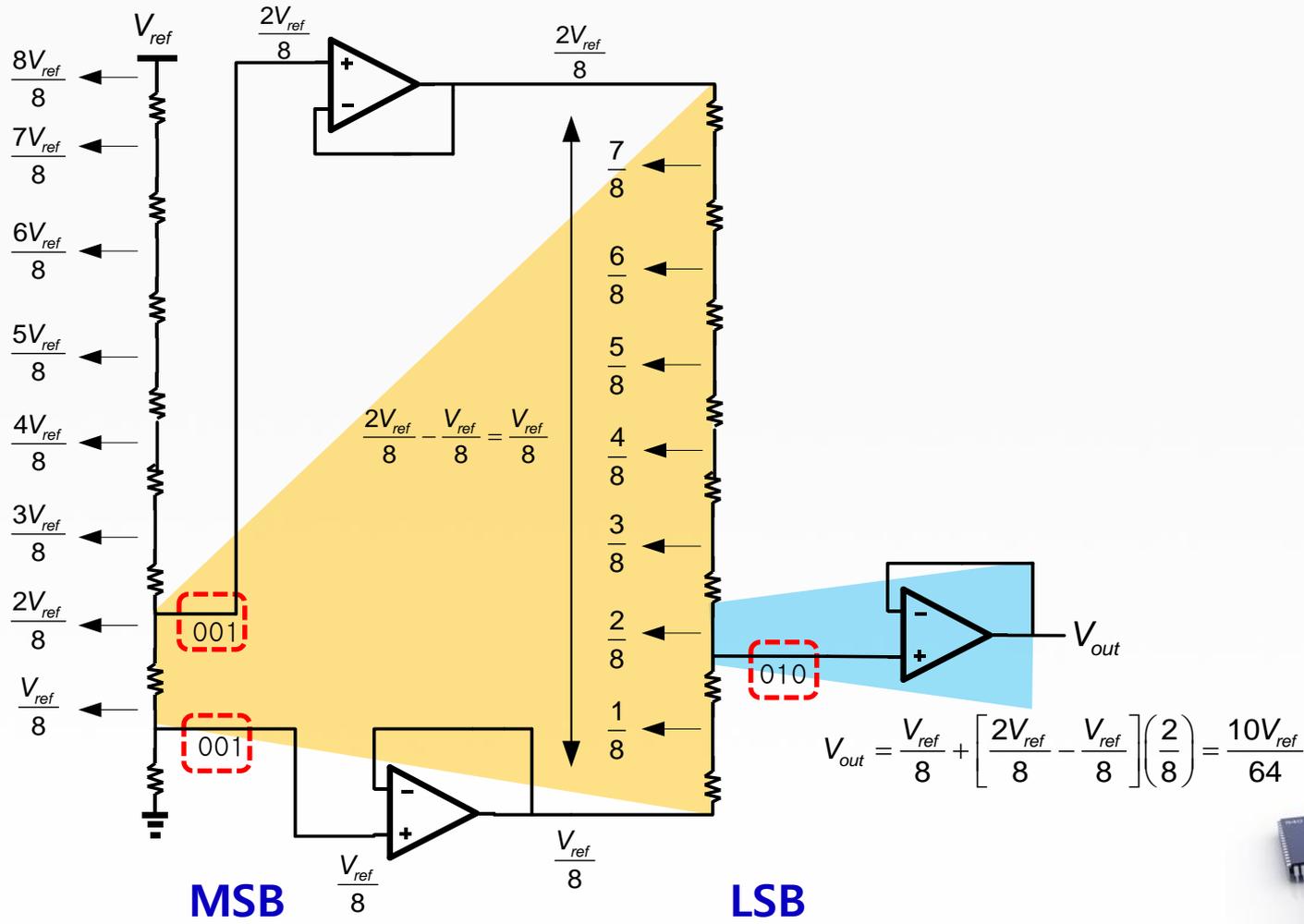

Binary-Weighted Resistor Converters

The most popular approach is binary fashion

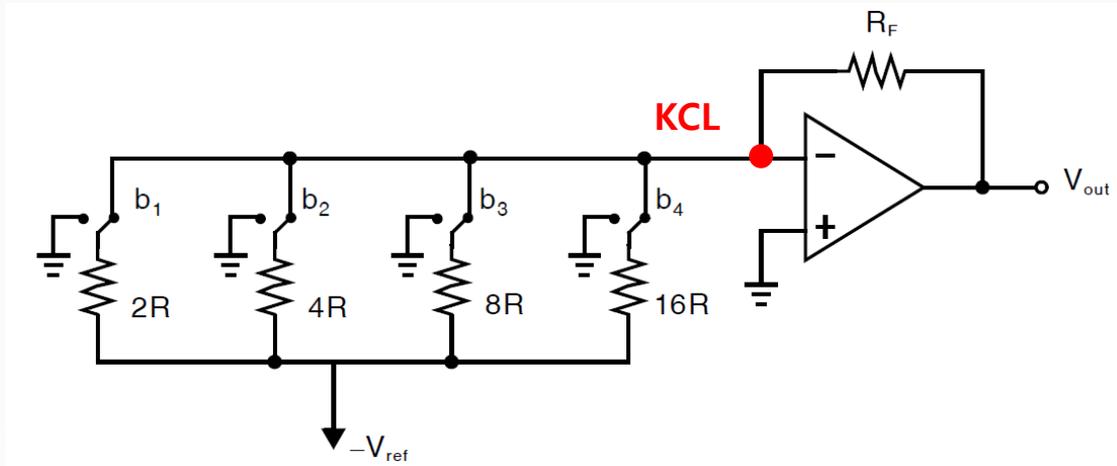


Fig. 16.7 Binary-weighted 4-bit resistor D/A converter

KCL

$$\frac{-V_{ref}}{R_{total}} = \frac{-V_{out}}{R_F}$$

$$V_{out} = -R_F V_{ref} \left(-\frac{b_1}{2R} - \frac{b_2}{4R} - \frac{b_3}{8R} - \dots \right)$$

$$= \left(\frac{R_F}{R} V_{ref} \right) B_{in} \quad (16.2)$$

$$B_{in} = b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3} + \dots$$

😊 Only N resistors

😞 - No guarantee of monotonicity
 - **Resistor and current ratios are on the order of 2^N**



Binary-Weighted Resistor Converters

Reduce the magnitude of resistors

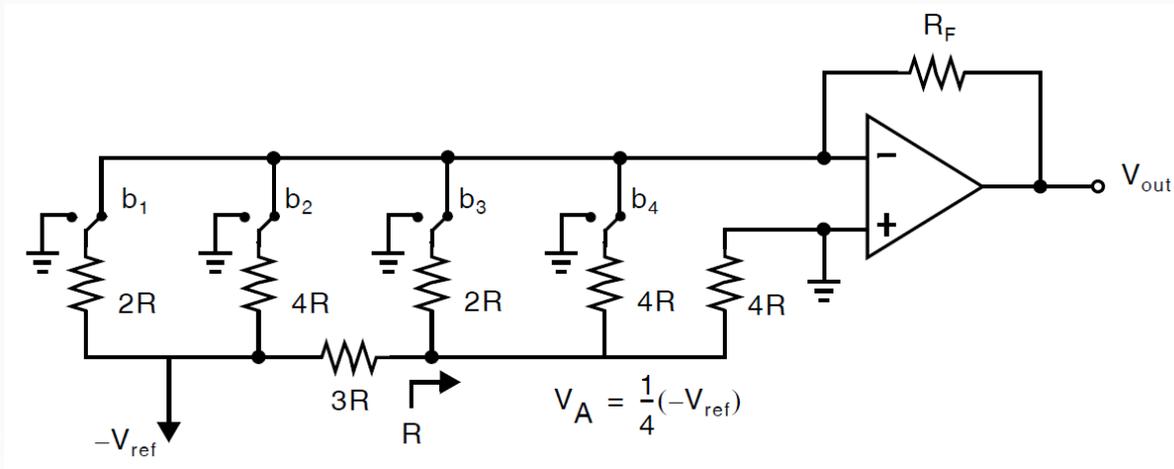


Fig. 16.8 Reduced-resistance-ratio 4-bit D/A converter

$$V_{out} = -R_F V_{ref} \left(-\frac{b_1}{2R} - \frac{b_2}{4R} - \frac{b_3}{8R} - \dots \right)$$

$$= \left(\frac{R_F}{R} V_{ref} \right) B_{in}$$

$$B_{in} = b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3} + \dots$$


Same relationship as in the previous binary-weighted case

➡ Arrives at a structure, R-2R ladder



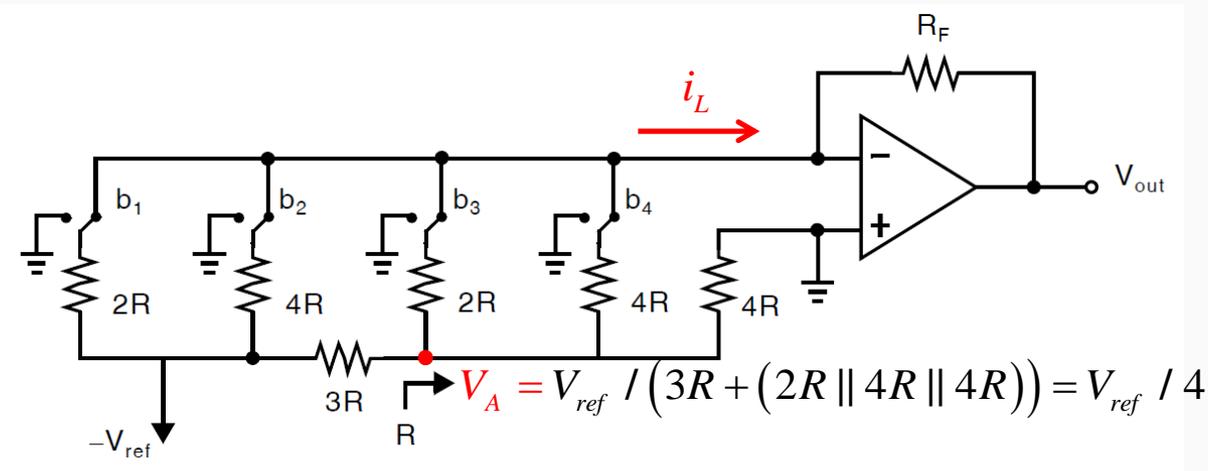Example 2

Calculate the V_{out} when $b_1b_2b_3b_4 = 0001, 0011, 0101, 1001$



$$V_{out} = \left(\frac{R_F}{R} V_{ref} \right) B_{in} \quad (16.2)$$

Fig. 16.8 Reduced-resistance-ratio 4-bit D/A converter

• $b_1b_2b_3b_4 = 0001$

$$i_L = V_{ref} / 16R$$

$$V_{out} = \frac{R_F}{16R} V_{ref}$$

• $b_1b_2b_3b_4 = 0011$

$$i_L = 3V_{ref} / 16R$$

$$V_{out} = \frac{3R_F}{16R} V_{ref}$$

• $b_1b_2b_3b_4 = 0101$

$$i_L = V_{ref} / 4R + V_{ref} / 16R$$

$$V_{out} = \frac{5R_F}{16R} V_{ref}$$

• $b_1b_2b_3b_4 = 1001$

$$i_L = V_{ref} / 2R + V_{ref} / 16R$$

$$V_{out} = \frac{9R_F}{16R} V_{ref}$$



R-2R Based D/A Converters

A very popular architecture for D/A converter

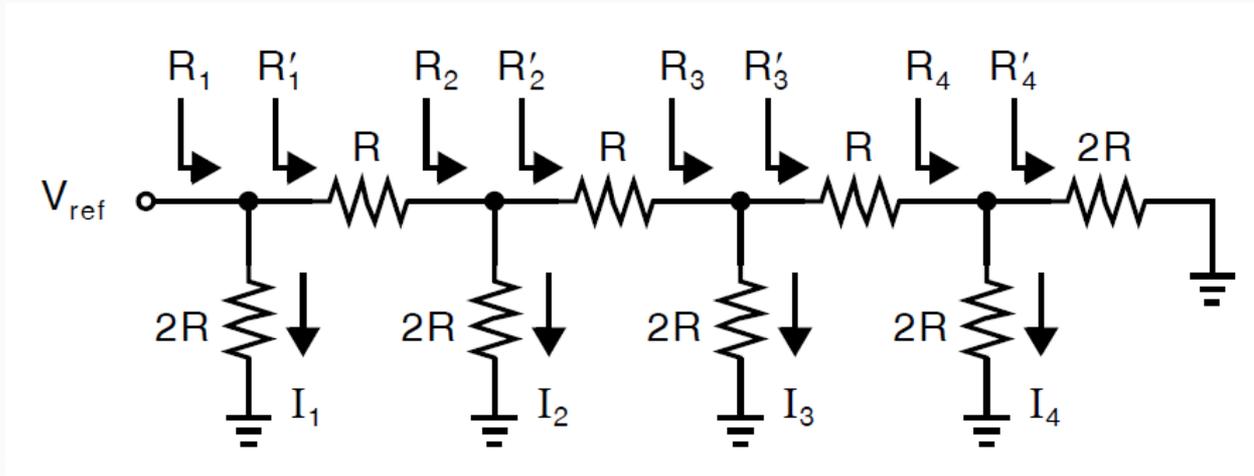


Fig. 16.9 R-2R-Based Converters

$$\begin{aligned}
 R'_4 &= 2R \\
 R_4 &= 2R \parallel 2R = R \\
 R'_3 &= R + R_4 = 2R \\
 R_3 &= 2R \parallel R'_3 = R
 \end{aligned}
 \tag{16.4}$$

$$I_1 = \frac{V_{\text{ref}}}{2R} \tag{16.5}$$

$$I_2 = \frac{V_{\text{ref}}}{4R} \tag{16.6}$$

$$I_3 = \frac{V_{\text{ref}}}{8R} \tag{16.7}$$



R-2R Based D/A Converters

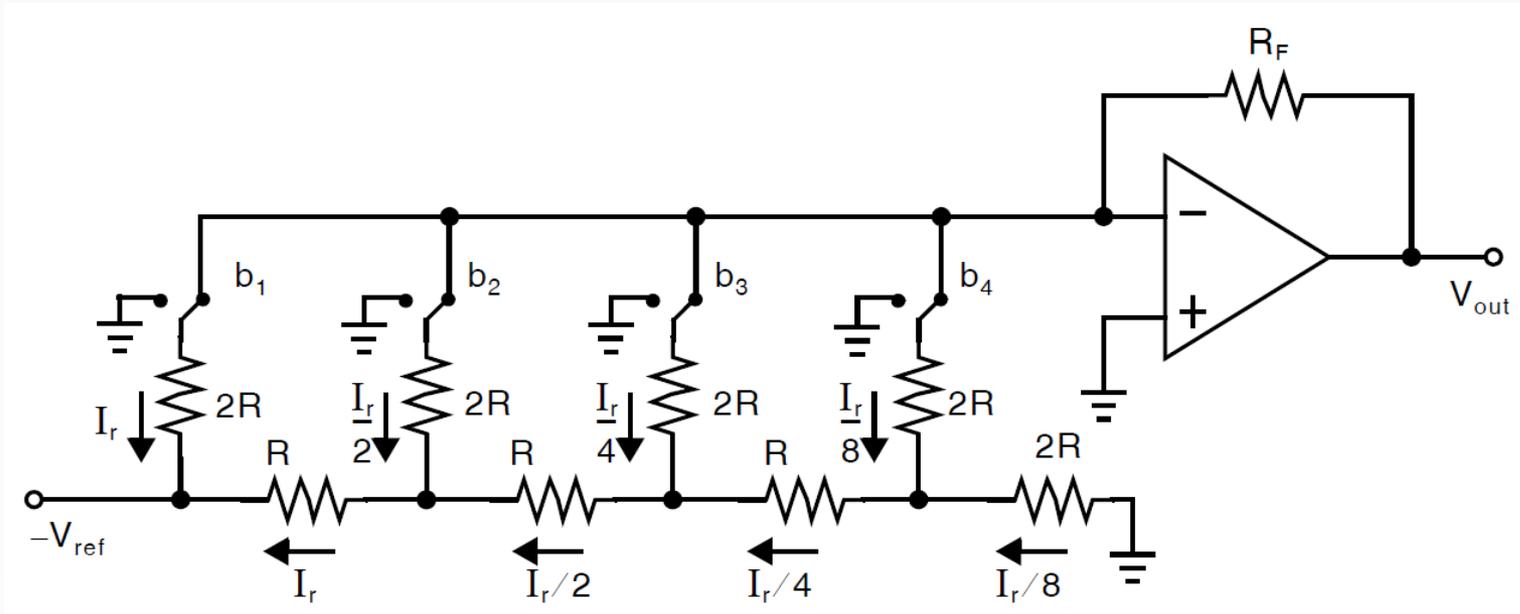


Fig. 16.10 4-bit R-2R-Based Converters

$$I_r = \frac{V_{ref}}{2R} \quad (16.8)$$


$$V_{out} = R_F \sum_{i=1}^N \frac{b_i I_r}{2^{i-1}} = V_{ref} \left(\frac{R_F}{R} \right) \sum_{i=1}^N \frac{b_i}{2^i} \quad (16.9)$$



- Small size
- Good matching (only R and 2R)




- Should scale switch sizes for good accuracy(unequal current)
- **Offset**

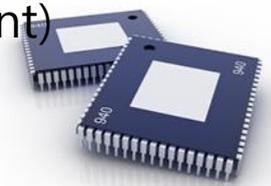

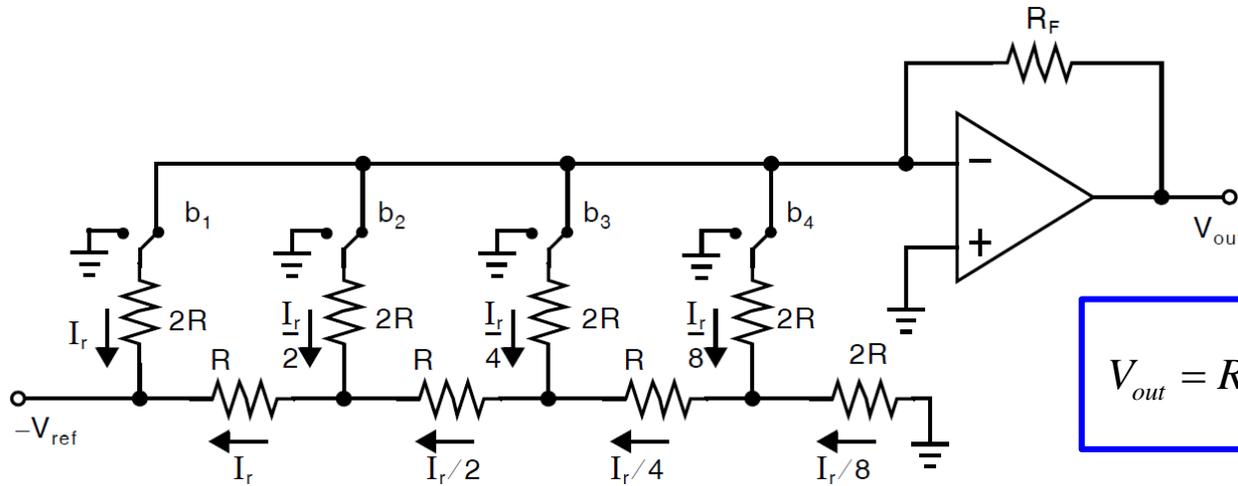Example 3

Calculate the V_{out} when $b_1b_2b_3b_4 = 0010, 1001, 0111$



$$V_{out} = R_F \sum_{i=1}^N \frac{b_i I_r}{2^{i-1}} = V_{ref} \left(\frac{R_F}{R} \right) \sum_{i=1}^N \frac{b_i}{2^i} \quad (16.9)$$

Fig. 16.10 4-bit R-2R-Based Converters

- $b_1b_2b_3b_4 = 0010$

$$V_{out} = V_{ref} \left(\frac{R_F}{R} \right) \cdot \left(\frac{1}{8} \right)$$

$$= V_{ref} \left(\frac{R_F}{8R} \right)$$

- $b_1b_2b_3b_4 = 1001$

$$V_{out} = V_{ref} \left(\frac{R_F}{R} \right) \cdot \left(\frac{1}{2} + \frac{1}{16} \right)$$

$$= V_{ref} \left(\frac{9R_F}{16R} \right)$$

- $b_1b_2b_3b_4 = 0111$

$$V_{out} = V_{ref} \left(\frac{R_F}{R} \right) \cdot \left(\frac{1}{4} + \frac{1}{8} + \frac{1}{16} \right)$$

$$= V_{ref} \left(\frac{7R_F}{16R} \right)$$



Charge-Redistribution Switched-Capacitor Converters

Replace resistors to capacitor array

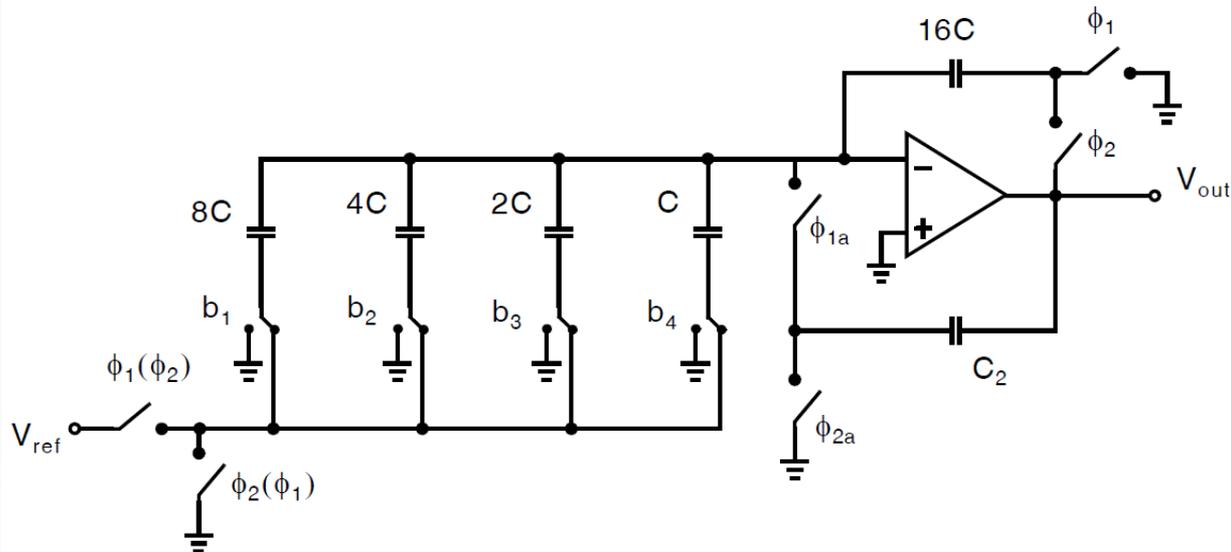


Fig. 16.12 Binary-array charge-redistribution D/A converter

Resistors  Capacitors

1. Insensitive to opamp input offset
2. Doesn't affect opamp gain


$$V_{out} = \left(\frac{C}{16C} V_{ref} \right) B_{in}$$

$$B_{in} = b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3} + \dots$$



Charge-Redistribution Switched-Capacitor Converters

To reduce the capacitor

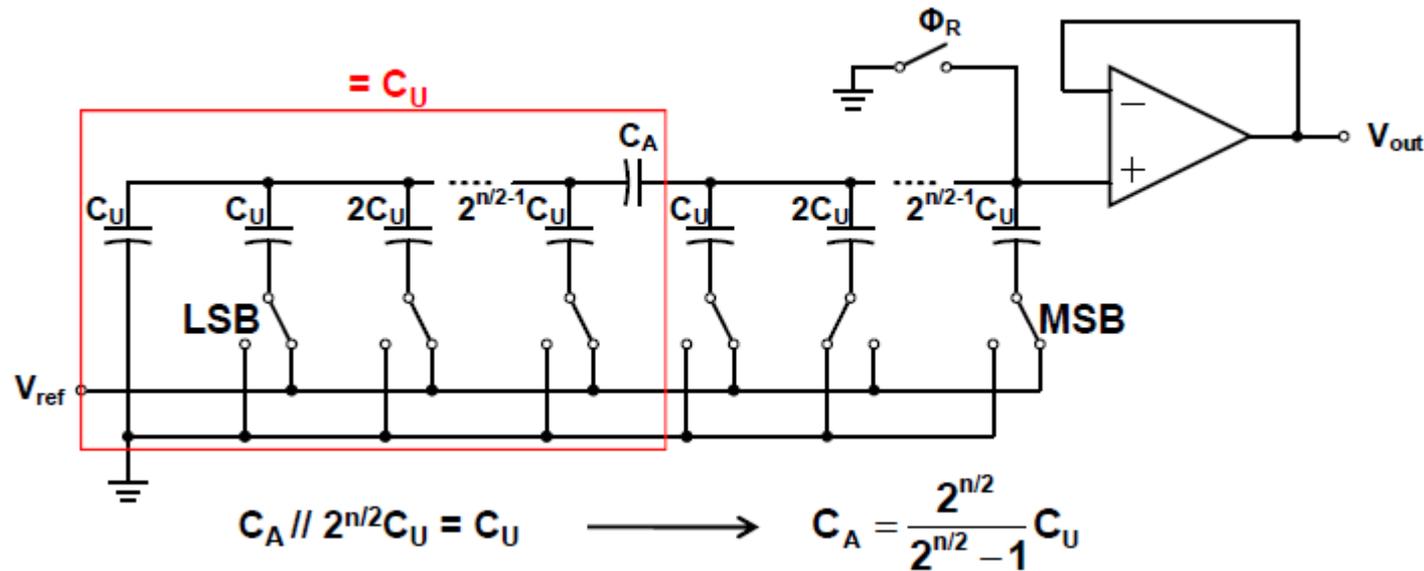

- 12-bit full binary: $C_{TOT} = 2^{12}C_U$.
- With attenuation capacitor.
 - $C_A = 1.015873C_U$.
 - $C_{TOT} = 2 \times 2^6C_U + 1.015873C_U$.
 - Matching is difficult.
 - Even division ($n/2$) is not necessary. m -bit (MSBs) & n -bit (LSBs) division possible.

