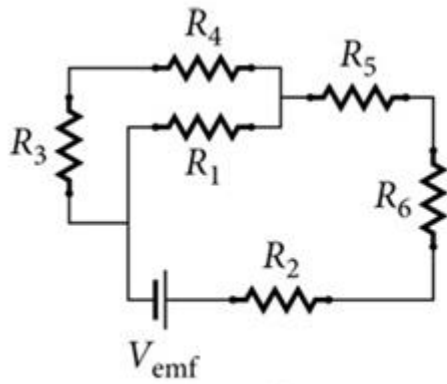



# Copyright statement

- The images and the pictures in this lecture are provided by the CDs accompanied by the books
  1. University Physics, Bauer and Westfall, McGraw-Hill, 2011.
  2. Principles of Physics, Halliday, Resnick, and Walker, Wiley, 8<sup>th</sup> and 9<sup>th</sup> Ed.
- The rest is made by me.


# Example 2




(a)

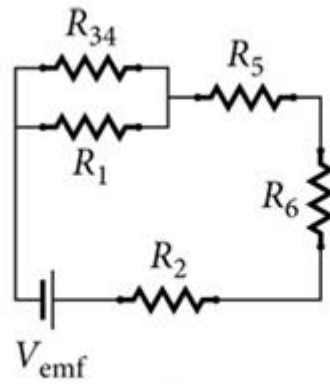

(b)

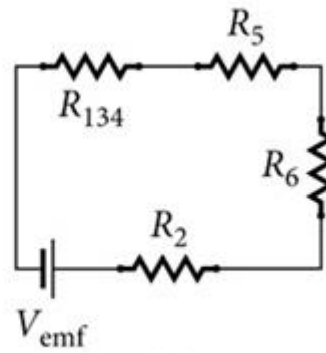


(c)

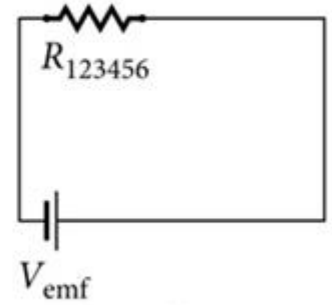

(d)

# Energy and power in circuits


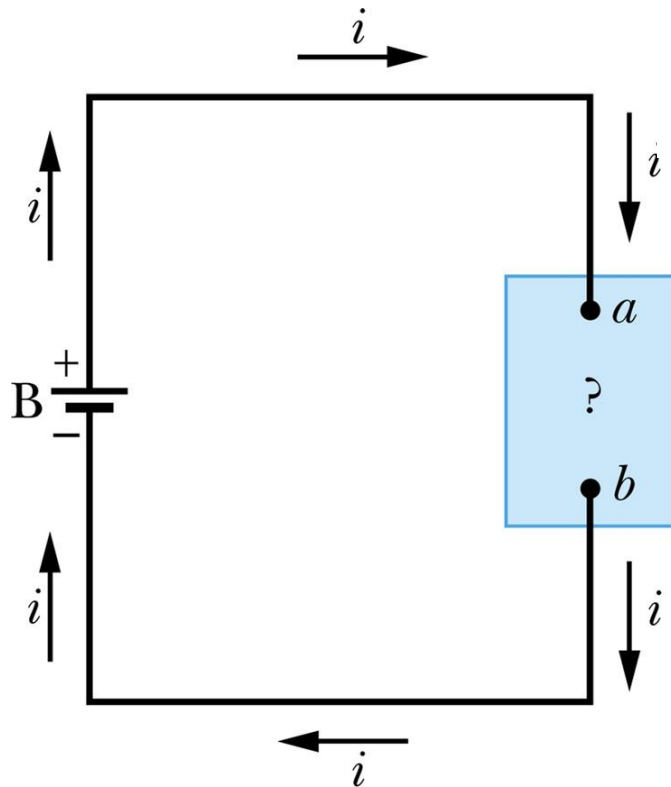


$$dU = dqV = i dtV \rightarrow P = iV = i^2 R = \frac{V^2}{R}$$

SI unit:  $V \cdot A$

$$1V \cdot A = \left(1 \frac{J}{C}\right) \left(1 \frac{C}{s}\right) = 1 \frac{J}{s} = 1W$$

# Problem 1

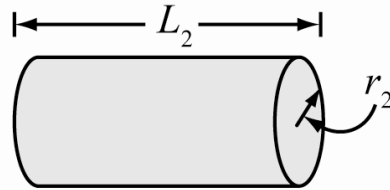
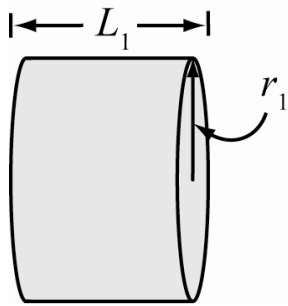


$$\frac{\Delta R}{R} = ?$$

# Problem 25.37




# Problems 25.46, 47

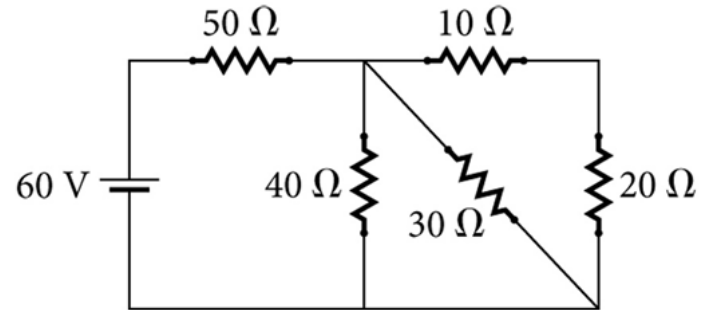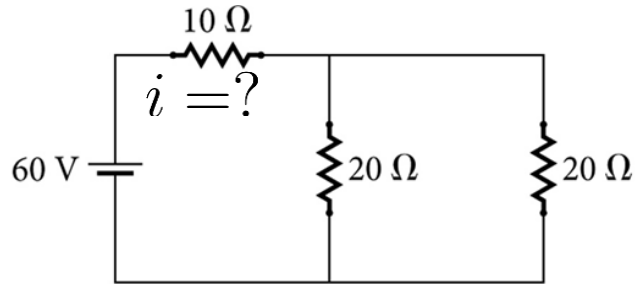


$$R_{\text{eq}} = ?$$

# Problem 25.48

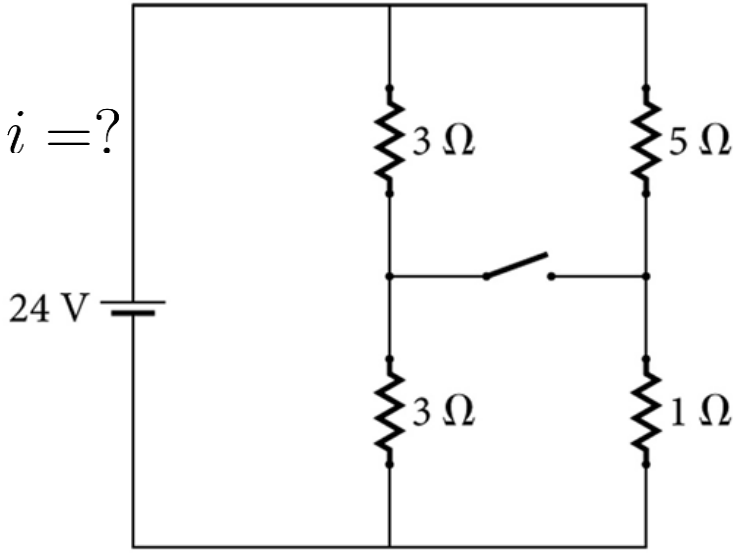


# Chap. 26 Direct current circuits


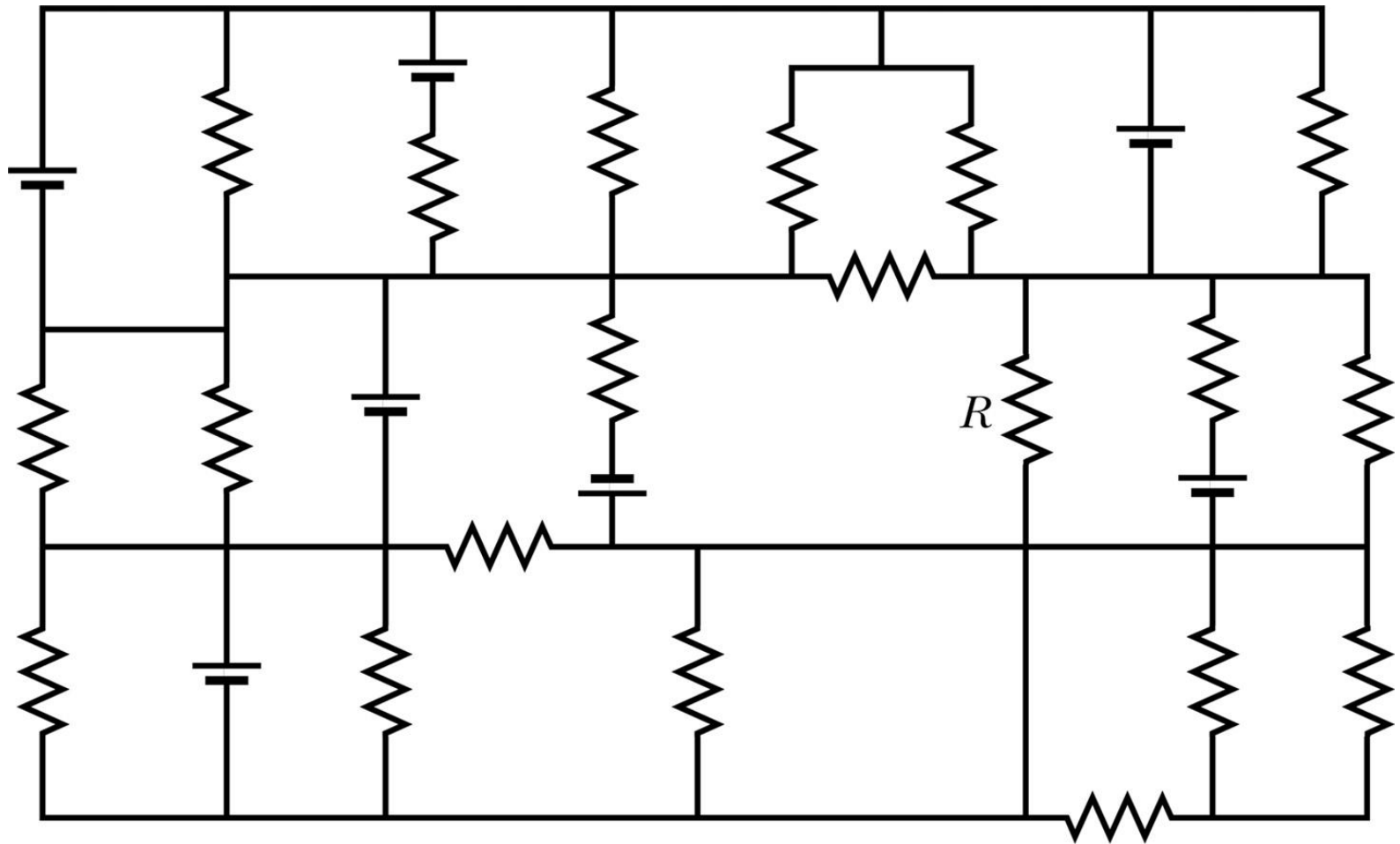




# Electromotive force (emf)

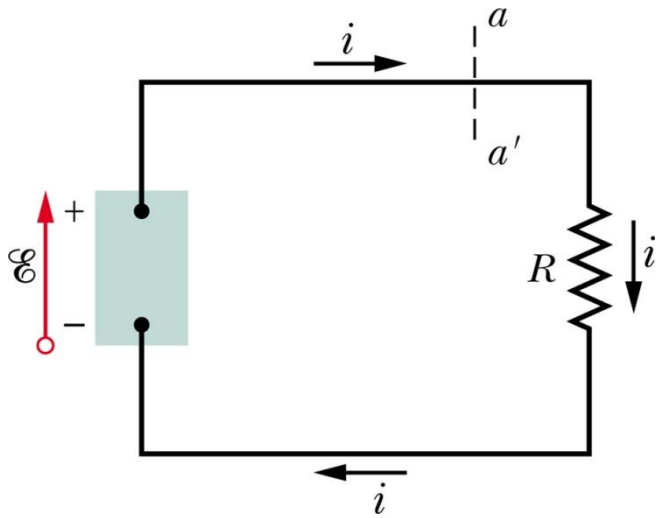

$$\mathcal{E} = \frac{dW}{dq}$$

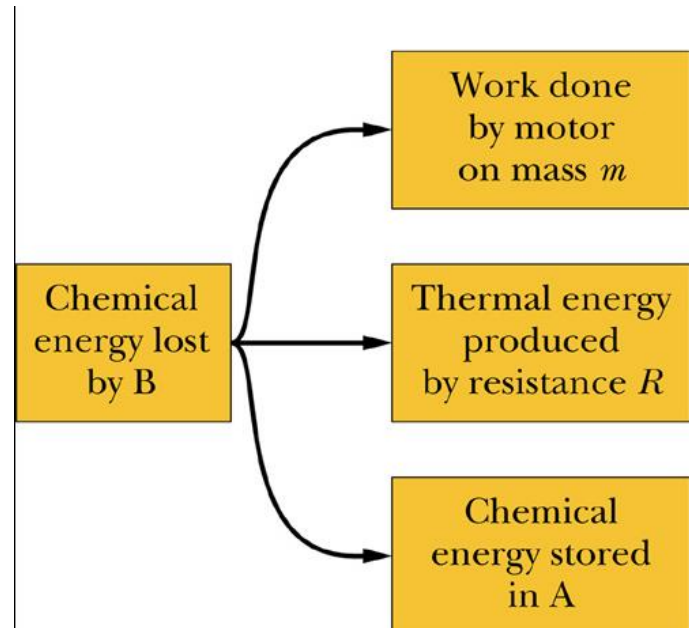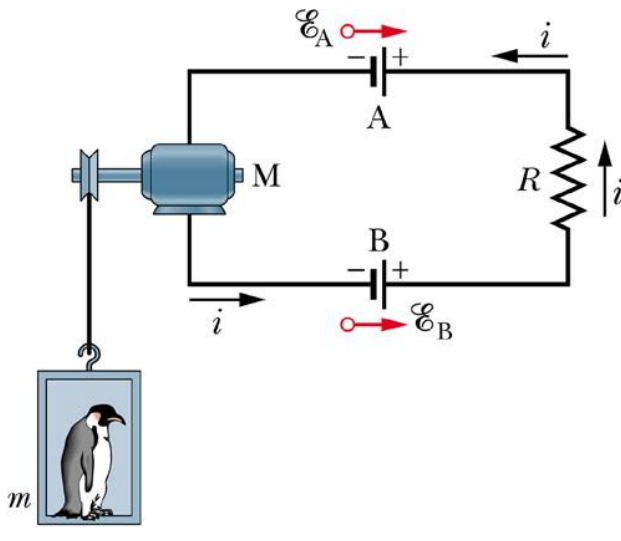


# Kirchhoff's rules (Junction rule)

The sum of the currents at a junction is conserved.


$$\sum_{k=1}^n i_k = 0$$
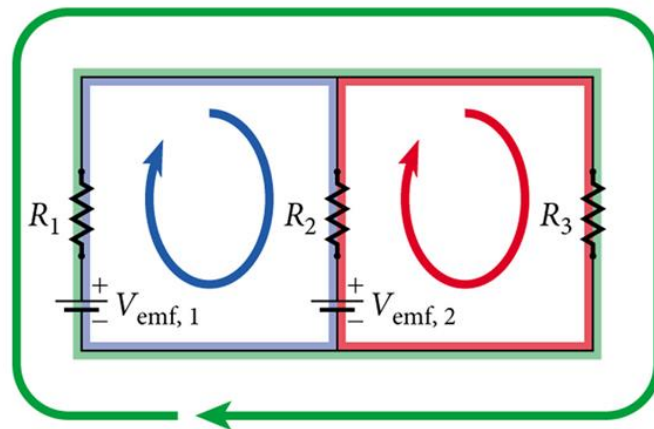
## Kirchhoff's Loop Rule

The potential difference around a complete circuit loop must sum to zero.



# Single-loop circuit

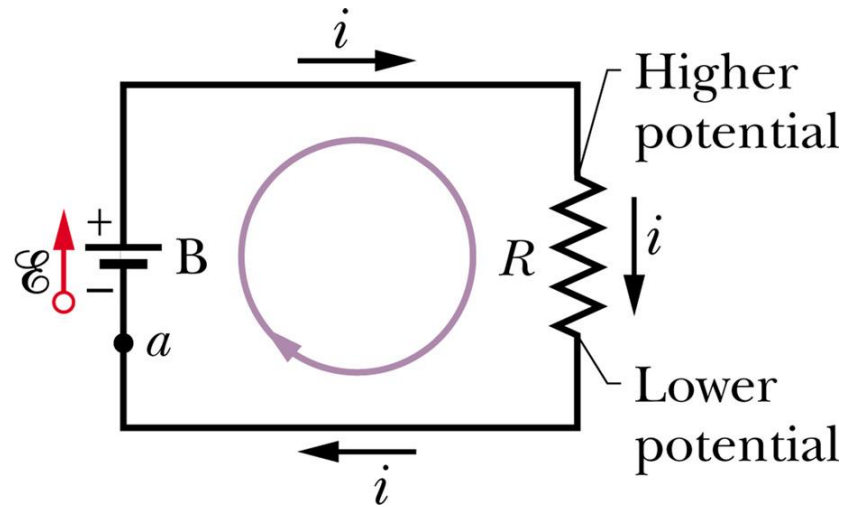

Kirchhoff's rule

Energy method

$$dW = \mathcal{E}dq = \mathcal{E}idt$$

$$\mathcal{E}idt = i^2 Rdt$$

$$\mathcal{E} = iR$$


$$i = \frac{\mathcal{E}}{R}$$

Potential method

$$V_a + \mathcal{E} - iR = V_a$$

$$i = \frac{\mathcal{E}}{R}$$


# Internal resistance

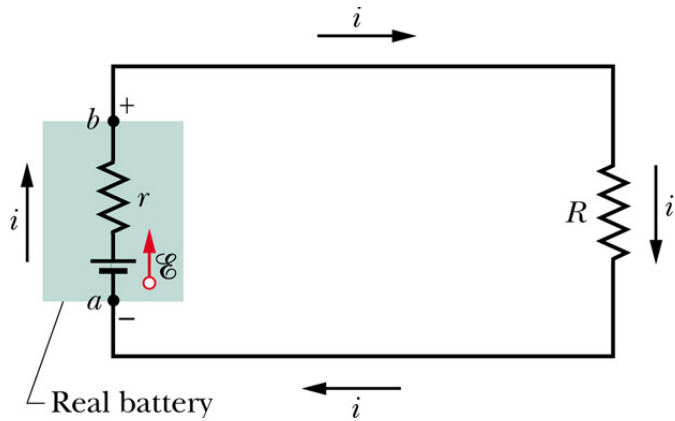

current  $\mathcal{E} - ir - iR = 0$

$$i = \frac{\mathcal{E}}{R + r}$$

Potential difference between a battery

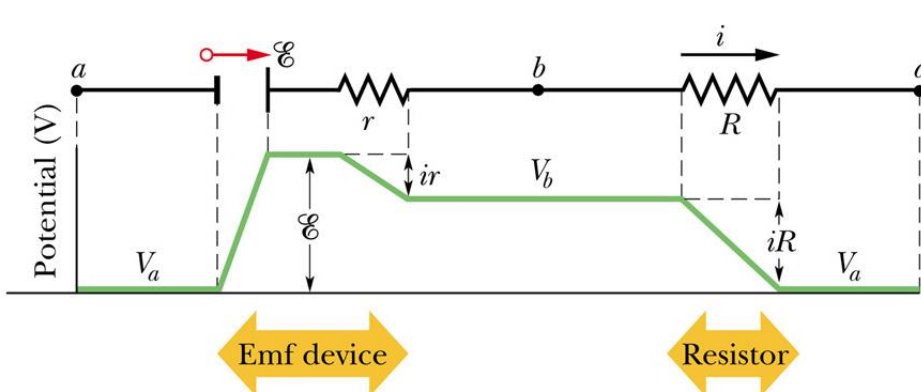


$$V_a + \mathcal{E} - ir = V_b$$

$$V_a - V_b = \mathcal{E} - ir = \mathcal{E} \frac{R}{R + r}$$

$$V_b - iR = V_a$$

$$V_a - V_b = iR = \mathcal{E} \frac{R}{R + r}$$

# Power, potential and emf

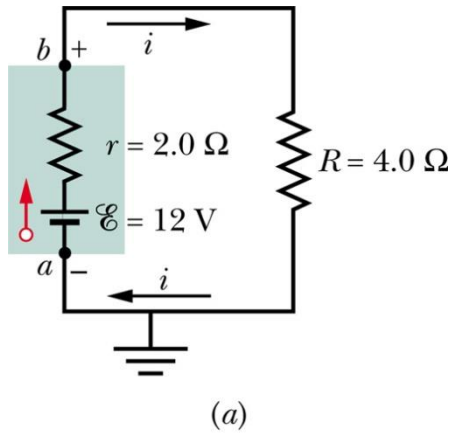


Power from emf to charges



$$P = iV$$

$$P = i(\mathcal{E} - ir) = \underbrace{i\mathcal{E}}_{\text{기전력의 일률 } P_{\text{emf}}} - \underbrace{i^2 r}_{\text{내부소모율 } P_r}$$


기전력의 일률  $P_{\text{emf}}$

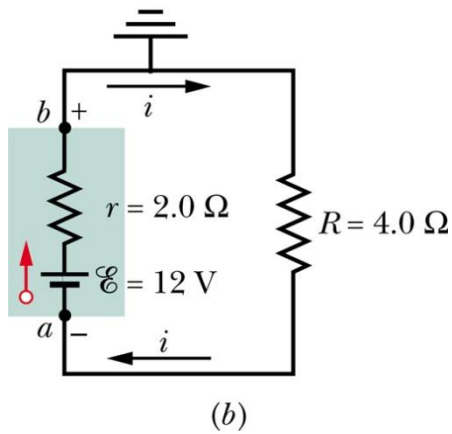

# Example 1

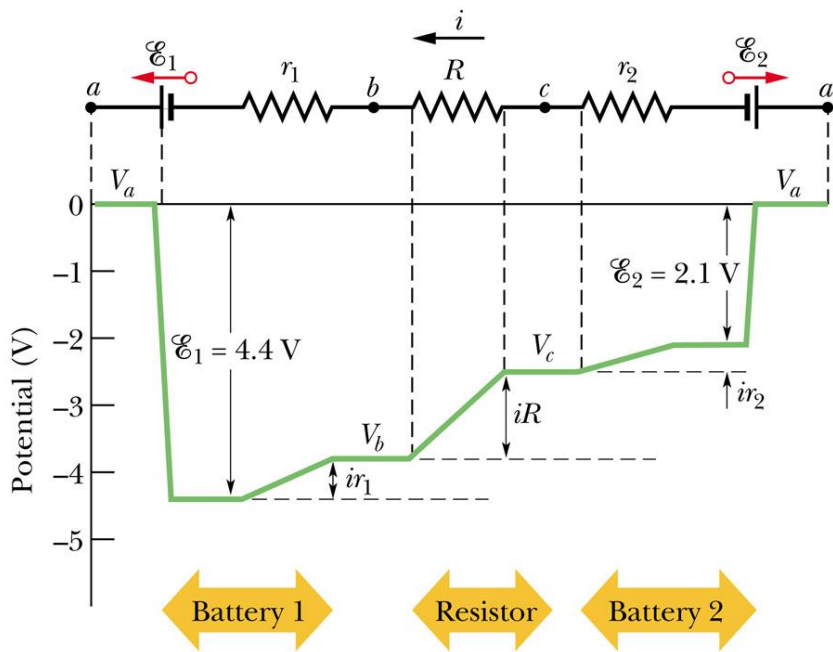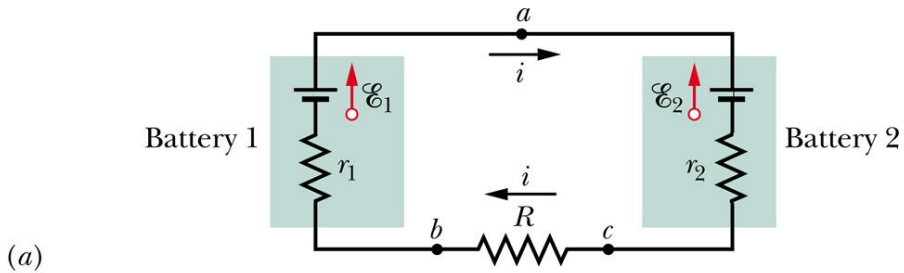

# Resistors in series

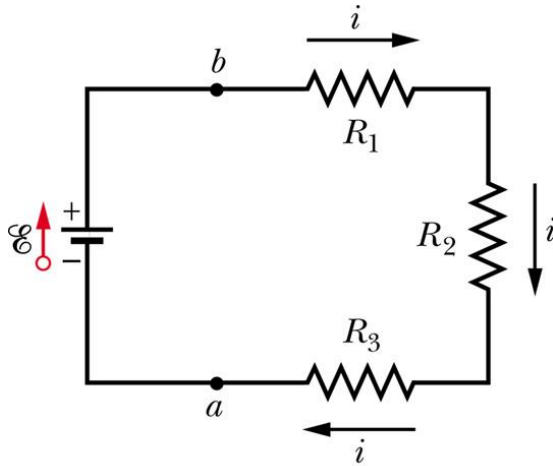


(a)

$$\mathcal{E} - iR_1 - iR_2 - iR_3 = 0$$

$$i = \frac{\mathcal{E}}{R_1 + R_2 + R_3} = \frac{\mathcal{E}}{R_{\text{eq}}}$$

$$R_{\text{eq}} = R_1 + R_2 + R_3$$

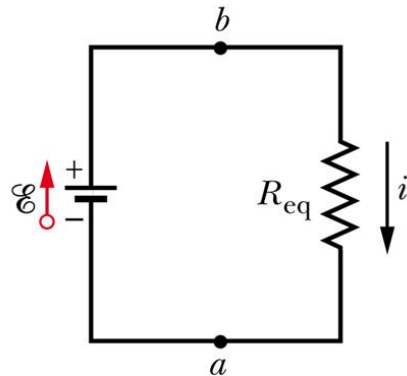


(b)

$n$  resistors connected in series

$$R_{\text{eq}} = \sum_{i=1}^n R_i$$


# Resistors in parallel

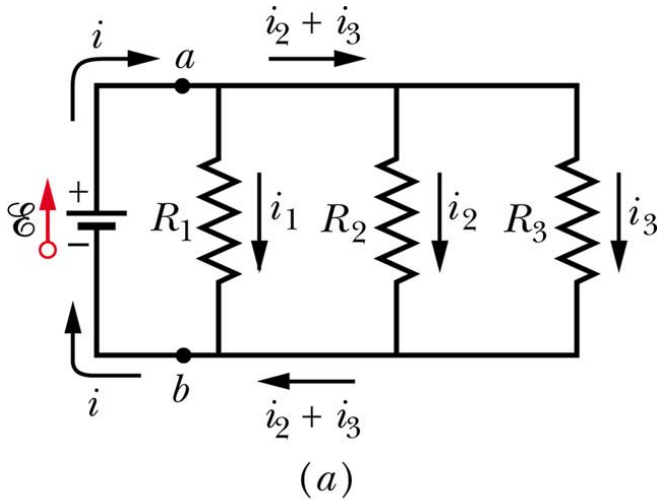

$$i_1 = \frac{V}{R_1}, \quad i_2 = \frac{V}{R_2}, \quad i_3 = \frac{V}{R_3}$$

$$i = i_1 + i_2 + i_3 = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$i = \frac{V}{R_{\text{eq}}}$$

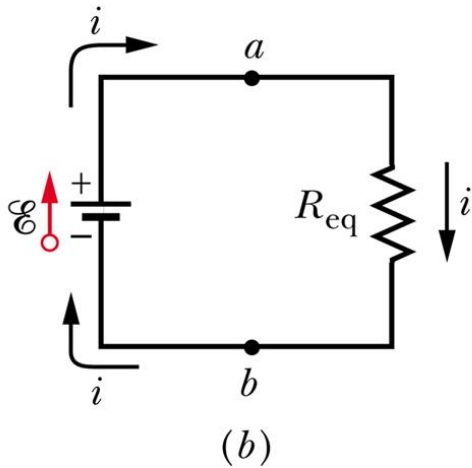


$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

n resistors connected in parallel

$$\frac{1}{R_{\text{eq}}} = \sum_{i=1}^n \frac{1}{R_i}$$



# Multiloop circuits

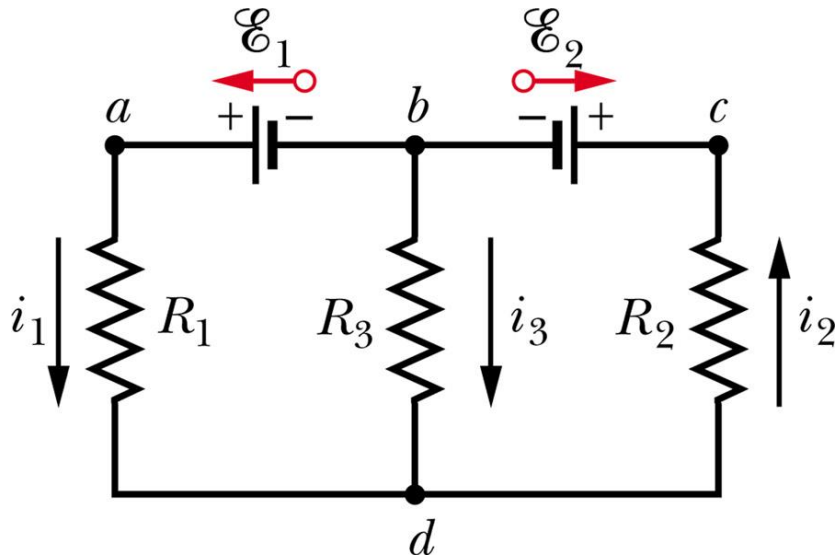

Branch rule:  $i_2 = i_1 + i_3$

Loop rule:

(bad)  $\mathcal{E}_1 - i_1 R_1 + i_3 R_3 = 0$


(bdc)  $-i_3 R_3 - i_2 R_2 - \mathcal{E}_2 = 0$

(badc)  $\mathcal{E}_1 - i_1 R_1 - i_2 R_2 - \mathcal{E}_2 = 0$

Not an independent equation!

# Solved problem 26.2

## The Wheatstone bridge

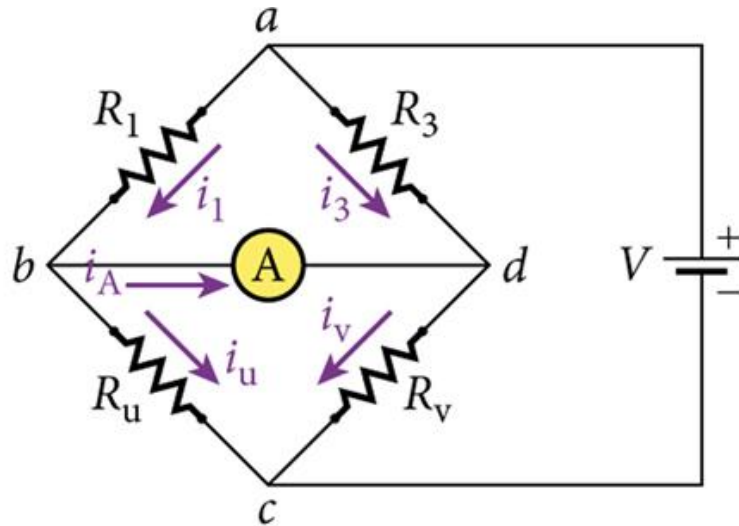


$$\text{adb} \quad -i_3 R_3 + i_A R_A + i_1 R_1 = 0$$

$$\text{cbd} \quad i_u R_u - i_A R_A - i_V R_V = 0$$


$$\text{b} \quad i_1 = i_A + i_u$$

$$\text{d} \quad i_3 + i_A = i_V$$


# Example 2

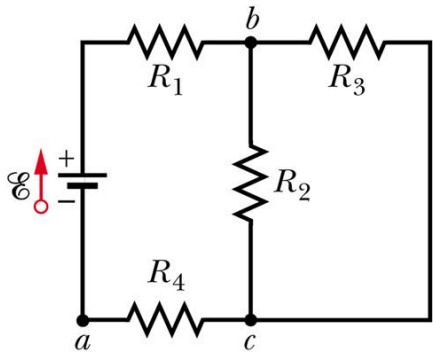

(a)

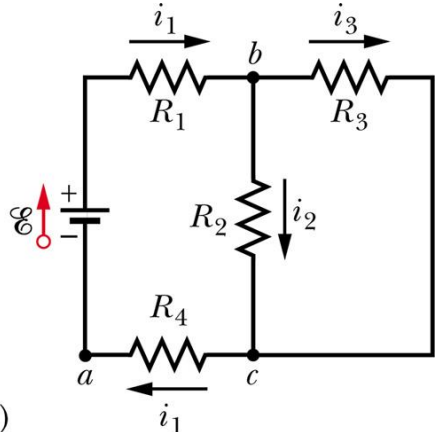


(b)

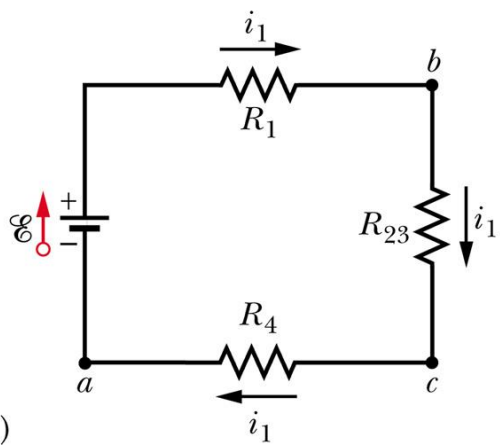


(c)


# Example 3

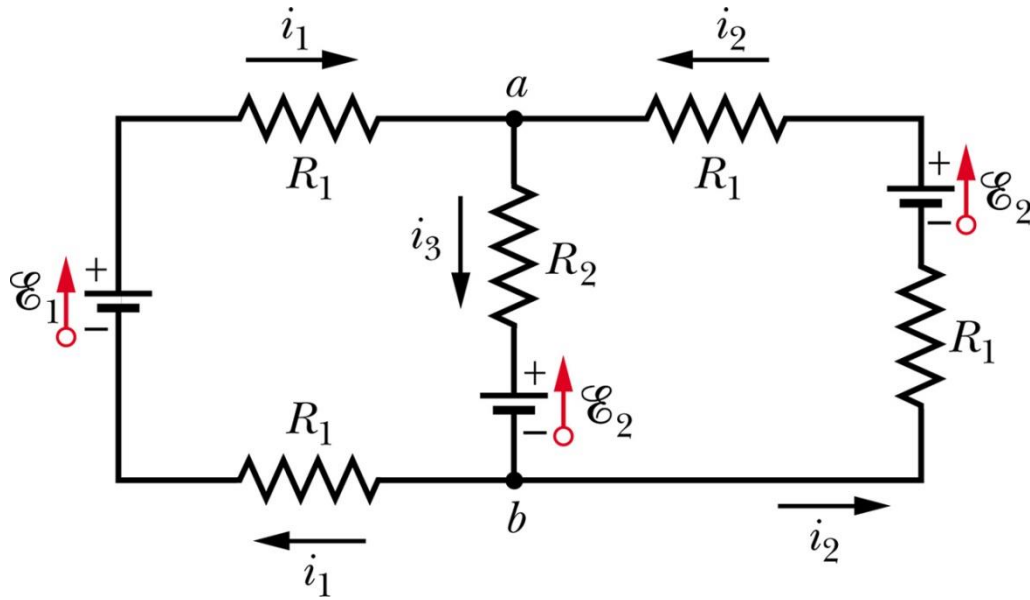

# Voltmeter and ammeter

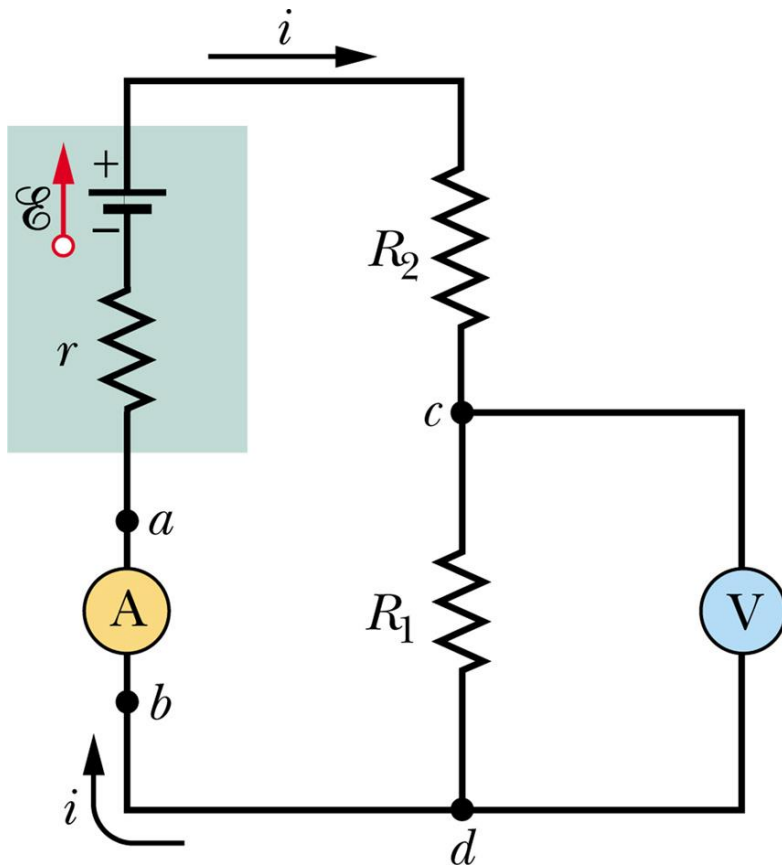

# RC circuit

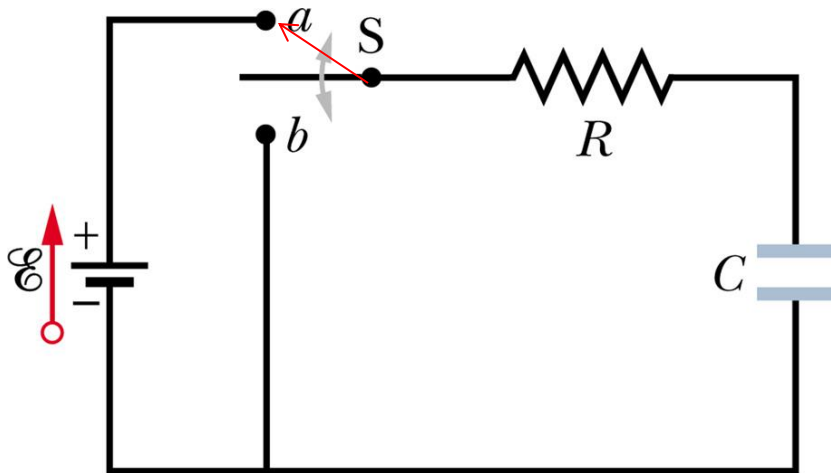

Charging a capacitor

$$\mathcal{E} - iR - \frac{q}{C} = 0 \quad i = \frac{dq}{dt}$$

$$R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E}$$

$t = 0$ 일 때  $q = 0$ 므로

$$A = -C\mathcal{E}$$

$$q(t) = C\mathcal{E}(1 - e^{-t/RC})$$

우선  $\mathcal{E} = 0$ 인 경우 (homogeneous eq.)

$q = Ae^{at}$  라고 놓으면, 위 식은

$$Ra + \frac{1}{C} = 0 \rightarrow a = -\frac{1}{RC}$$

$\mathcal{E} \neq 0$  일 경우 가장 간단한 해는  $q = C\mathcal{E}$

$$q(t) = Ae^{-t/RC} + C\mathcal{E}$$