

# LECTURE 16

Soo-Won Kim  
[swkim@korea.ac.kr](mailto:swkim@korea.ac.kr)

# Lecture 16

## 17. Nyquist-rate A/D converter

17.1 Integrating converters

17.2 Successive-approximation converter

17.3 Algorithmic (or cyclic) A/D converter

17.4 Pipelined A/D converter

**17.5 Flash converters**

**17.6 Two-step A/D converters**




**17.7 Interpolating A/D converters**

17.8 Folding A/D converters

17.9 Time-interleaved A/D converters




# ADC speed

   

Topology	Conversion rate	Resolution
Flash	<5G samples/s	Up to 8bit
Two-step	<100M samples/s	Up to 16bit
interpolating	<3G samples/s	Up to 6bit



# Flash converters

 

High-speed  
Monotonic(thermometer code)



Area & Power consumption  
Require  $2^N$  resistors & comparator  
Large input capacitor  
**Bubble error**


 


Fig. A 3-bit flash A/D converter
 
# Example 1

Find the digital output during the operation of the 3-bit flash A/D converter.

Assume that  $V_{in} = 1.23V, 2.4V, 3.6V$ ,  $V_{ref} = 5V$ .



$V_{r1} = \frac{0.5 \cdot R}{8 \cdot R} \times V_{ref} = 0.3125V$	$V_{r5} = \frac{4.5 \cdot R}{8 \cdot R} \times V_{ref} = 2.8125V$
$V_{r2} = \frac{1.5 \cdot R}{8 \cdot R} \times V_{ref} = 0.9375V$	$V_{r6} = \frac{5.5 \cdot R}{8 \cdot R} \times V_{ref} = 3.4375V$
$V_{r3} = \frac{2.5 \cdot R}{8 \cdot R} \times V_{ref} = 1.5625V$	$V_{r7} = \frac{6.5 \cdot R}{8 \cdot R} \times V_{ref} = 4.0625V$
$V_{r4} = \frac{3.5 \cdot R}{8 \cdot R} \times V_{ref} = 2.1875V$	$V_{r8} = \frac{7.5 \cdot R}{8 \cdot R} \times V_{ref} = 4.6875V$
-----	
- $V_{in} = 1.23V$	- $V_{in} = 2.4V$
$V_{r2} < V_{in} < V_{r3}$	$V_{r4} < V_{in} < V_{r5}$
<b>Thermometer 00000011</b>	<b>00001111</b>
↓	↓
<b>Binary 010</b>	<b>100</b>
-----	
- $V_{in} = 3.6V$	
$V_{r6} < V_{in} < V_{r7}$	
<b>00111111</b>	<b>110</b>
↓	↓

Fig. A 3-bit flash A/D converter

# Flash converters

## Bubble error removal

 


Fig. 17.24 A 3-bit flash A/D converter



# Two-step A/D converters

 


Fig. 17.29 An 8-bit two-step A/D converter

😊 Area & power consumption ↓  
Reduce the number of comparators  
Ex) 8-bit A/D converter


😢 Speed limitation by bandwidth &  
settling time of gain amp  
Require accurate gain amp

Flash ADC  
Comparato  
r :  $2^8 = 256$

Two-step ADC  
Comparator :  
 $2 \times 2^4 = 32$


 
# Two-step A/D converters (Two-step Flash ADC)



## Example 2

Find the digital output during the operation of the 4-bit two-step A/D converter(flash ADC). Assume that  $V_{in} = 1.23V$ ,  $3.6V$ ,  $V_{ref} = 5V$ .

 


Fig. 17.29 An 4-bit two-step A/D converter

- First 2bits

$$V_{r1} = \frac{1 \cdot R}{4 \cdot R} \times V_{ref} = 1.25V$$

$$b_1, b_2 = 0, 0$$

$$V_1 = 0V$$

$$V_q = V_{in} - V_1 \\ = 1.23 - 0 = 1.23$$

$$V_{gain} = 4 \cdot 1.23 \\ = 4.92V$$

- Lower 2bits

$$V_{gain} > V_{r3}$$

$$b_3, b_4 = 1, 1$$



## Example 2(Cont.)

Find the digital output during the operation of the 4-bit two-step A/D converter(flash ADC). Assume that  $V_{in} = 1.23V, 3.6V, V_{ref} = 5V$ .

 


Fig. 17.29 An 4-bit two-step A/D converter

- First 2bits

$$V_{r2} < V_{in} < V_{r3}$$

$$b_1, b_2 = 1, 0$$

$$V_1 = 2.5V$$

$$\begin{aligned} V_q &= V_{in} - V_1 \\ &= 3.6 - 2.5 = 1.1V \end{aligned}$$

$$\begin{aligned} V_{gain} &= 4 \cdot 1.1 \\ &= 4.4V \end{aligned}$$

- Lower 2bits

$$V_{gain} > V_{r3}$$

$$b_3, b_4 = 1, 1$$



$$V_{r1} = \frac{1 \cdot R}{4 \cdot R} \times V_{ref} = 1.25V$$

$$V_{r2} = \frac{2 \cdot R}{4 \cdot R} \times V_{ref} = 2.5V$$

$$V_{r3} = \frac{3 \cdot R}{4 \cdot R} \times V_{ref} = 3.75V$$

## Example 3

If the gain of gain amp is 3.4, Find the digital output during the operation of the 4-bit two-step A/D converter(flash ADC). Assume that  $V_{in} = 3.6V$ ,  $V_{ref} = 5V$ .

 


Fig. 17.29 An 4-bit two-step A/D converter

- First 2bits

$$V_{r2} < V_{in} < V_{r3}$$

$$b_1, b_2 = 1, 0$$

$$V_1 = 2.5V$$

$$\begin{aligned} V_q &= V_{in} - V_1 \\ &= 3.6 - 2.5 = 1.1V \end{aligned}$$

$$\begin{aligned} V_{gain} &= 3.4 \cdot 1.1 \\ &= 3.74V \end{aligned}$$

- Lower 2bits

$$V_{r2} < V_{gain} < V_{r3}$$

$$b_3, b_4 = 1, 0$$




$$V_{r1} = \frac{1 \cdot R}{4 \cdot R} \times V_{ref} = 1.25V$$




$$V_{r2} = \frac{2 \cdot R}{4 \cdot R} \times V_{ref} = 2.5V$$

$$V_{r3} = \frac{3 \cdot R}{4 \cdot R} \times V_{ref} = 3.75V$$

# Interpolating A/D converters

 


Differential Input amplifier

   

Variation of output voltage  
( $V_x$  and  $V_y$ )

 -  $V_1 = 2/3V_{BIAS}$ ,  $V_2 = V_{BIAS}$ ,  $V_3 = 4/3V_{BIAS}$ ,



# Interpolating A/D converters

 


Fig. 17.31 A 4-bit interpolating A/D converter (interpolating factor of 4)

 


Fig. 17.32 Possible transfer responses for the input-comparator output signals,  $V_1$  and  $V_2$ , and their interpolated signals



monotonic

Input capacitor  $\downarrow$  (faster than flash)



Latch thresholds is critical  
Match delay to latches



## Example 4

Find the digital output during the operation of the 3-bit interpolating A/D converter. Assume that  $V_{in} = 0.23V$ ,  $0.6V$ ,  $V_{ref} = 1V$ .


 
 


Fig. 17.31 A 3-bit interpolating A/D converter (interpolating factor of 4)

 

## Example 5(Cont.)

Find the digital output during the operation of the 3-bit interpolating A/D converter. Assume that  $V_{in} = 0.23V$ ,  $0.6V$ ,  $V_{ref} = 1V$ .

 


Fig. 17.31 A 3-bit interpolating A/D converter  
(interpolating factor of 4)

