

LECTURE 3

Soo-Won Kim
swkim@korea.ac.kr

4. Frequency Response of Electronic Circuits

4.1 Frequency Response of Linear Systems

4.2 Frequency Response of Elementary Transistor Circuits



4.3 Cascode Gain Stage

4.4 Source-Follower Amplifier

4.5 Differential Pair





Gain Roll-off of Amplifier

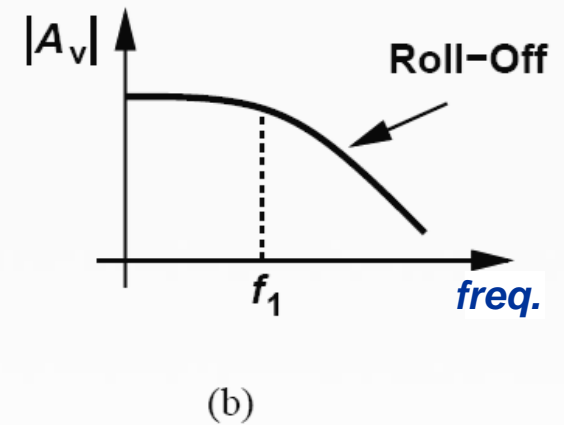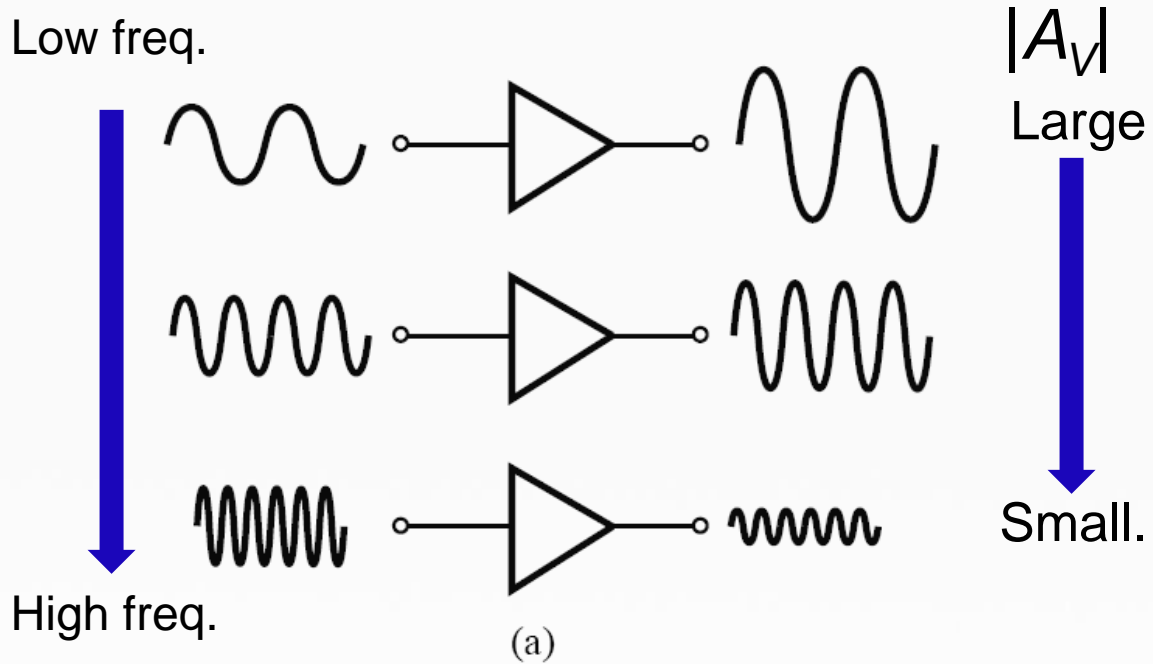

$$\text{freq.} \uparrow \Rightarrow |A_V| \rightarrow 0$$




Gain Roll-off: Common Source

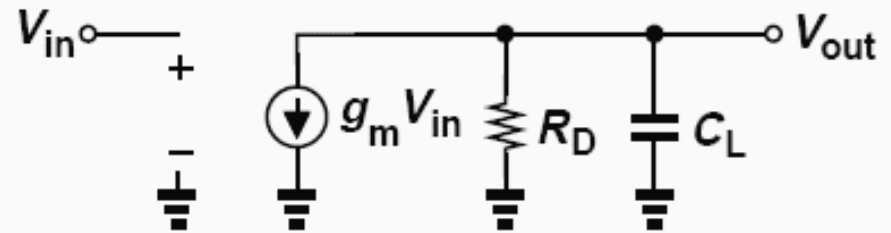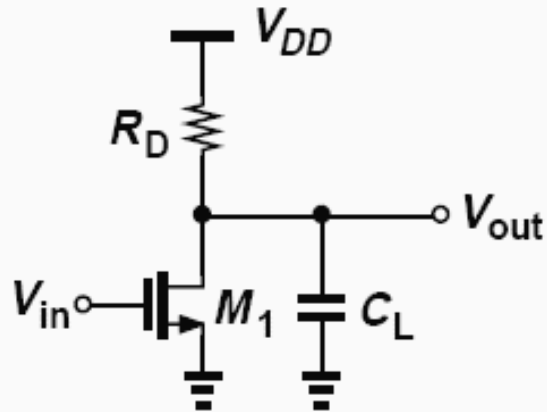

$$V_{out} = -g_m V_{in} \left(R_D \parallel \frac{1}{C_L s} \right)$$
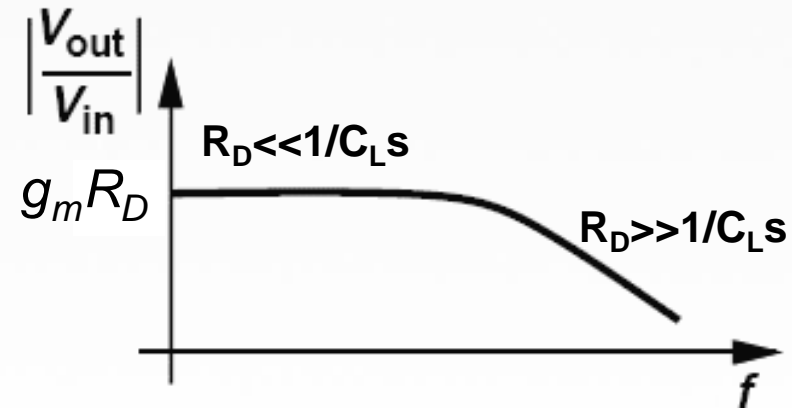
$$f \uparrow \Rightarrow \frac{1}{C_L s} = 0 \Rightarrow A_v \rightarrow 0$$



Bode Plot

Recall the electrical circuit theorem

$$H(s) = A_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 + \frac{s}{\omega_{z2}}\right) \dots}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \dots}$$

ω_z : zero frequency



➤ Increase by **20dB/decade**

ω_p : pole frequency

➤ Decrease by **20dB/decade**




Example: Bode Plot

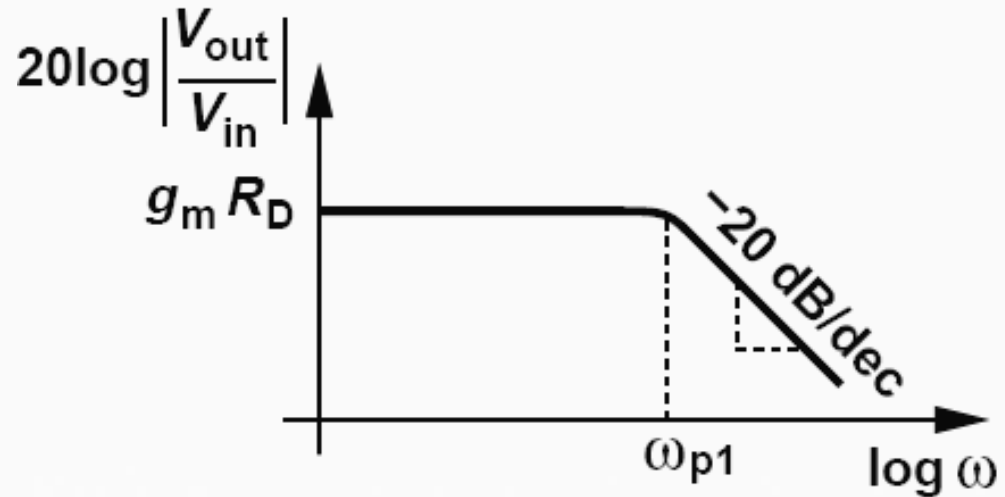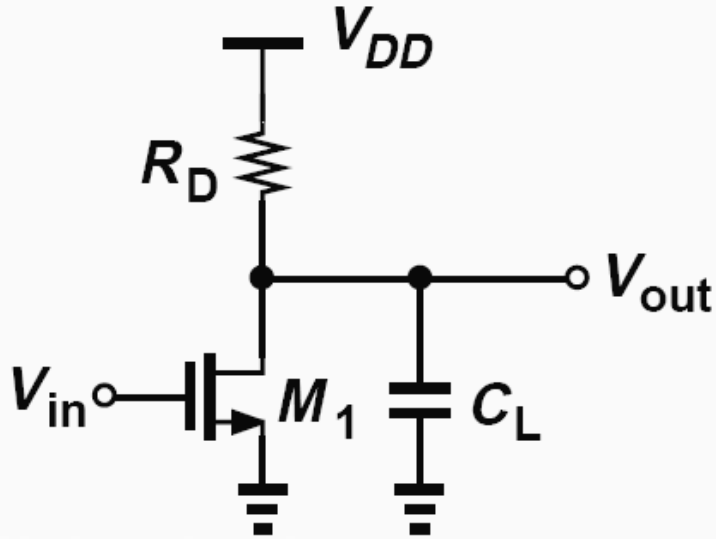


$$\frac{V_{out}}{V_{in}} = \frac{-g_m R_D}{1 + \frac{s}{1/R_D C_L}}$$

$$|\omega_{p1}| = \frac{1}{R_D C_L}$$

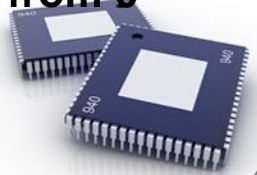The circuit only has one pole (no zero) at $1/(R_D C_L)$, so the slope drops from 0 to -20 dB/dec as ω pass ω_{p1} .



Circuit with Floating Capacitor

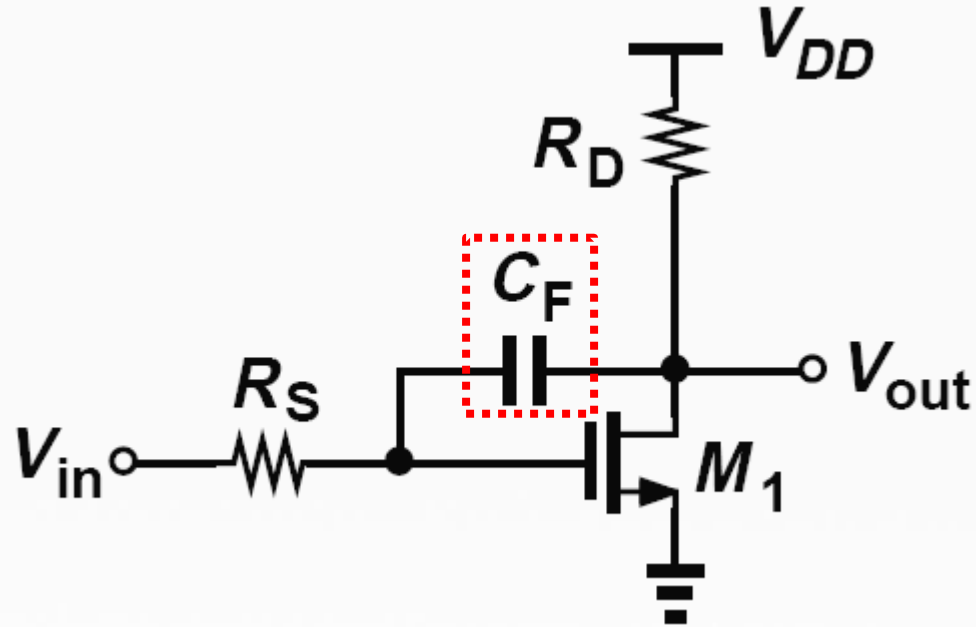


The **pole** of a circuit is computed by finding the **effective resistance** and **capacitance** from a node to GROUND.

➡ **Miller's theorem**




Miller's Theorem

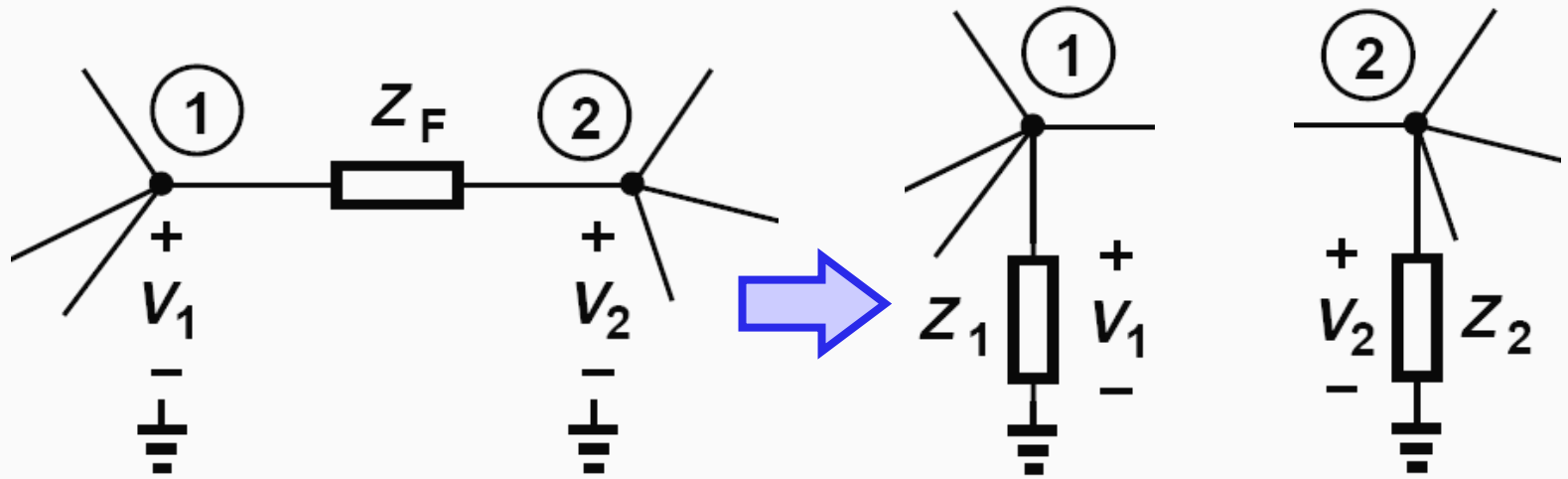

$$\frac{V_1 - V_2}{Z_F} = \frac{V_1}{Z_1}$$

$$\frac{V_2 - V_1}{Z_F} = \frac{V_2}{Z_2}$$

$$A_V = \frac{V_2}{V_1}$$

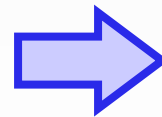


$$Z_1 = \frac{Z_F}{1 - A_V}$$

$$Z_2 = \frac{Z_F}{1 - 1/A_V}$$





Miller's Multiplication

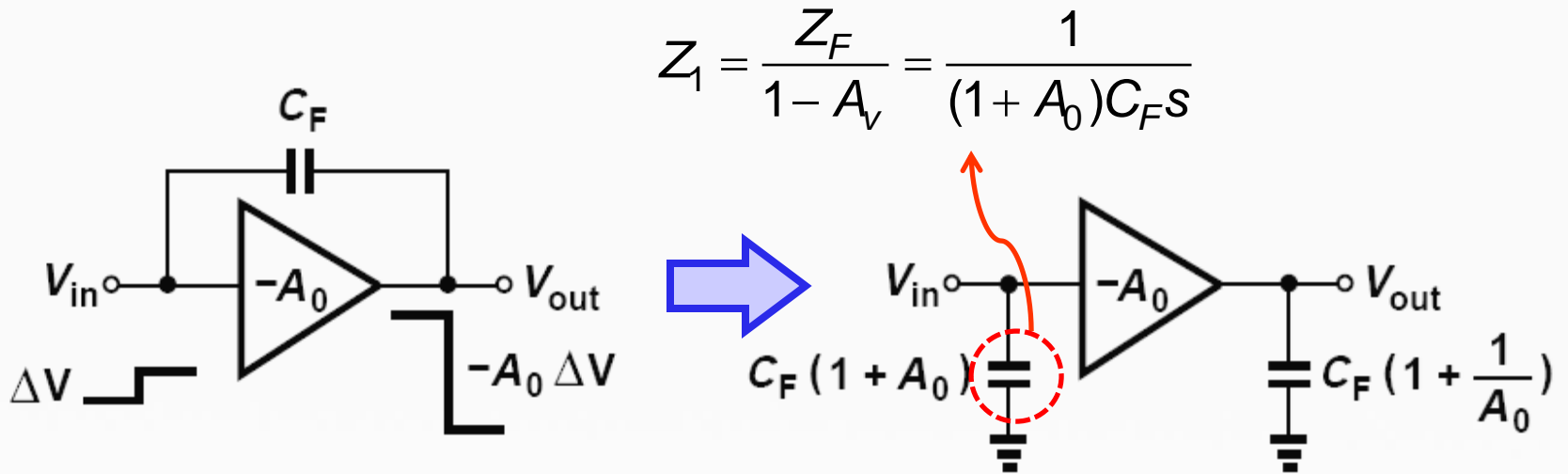

The input capacitor is larger than the original floating capacitor
(Miller multiplication)



Example: Miller Theorem

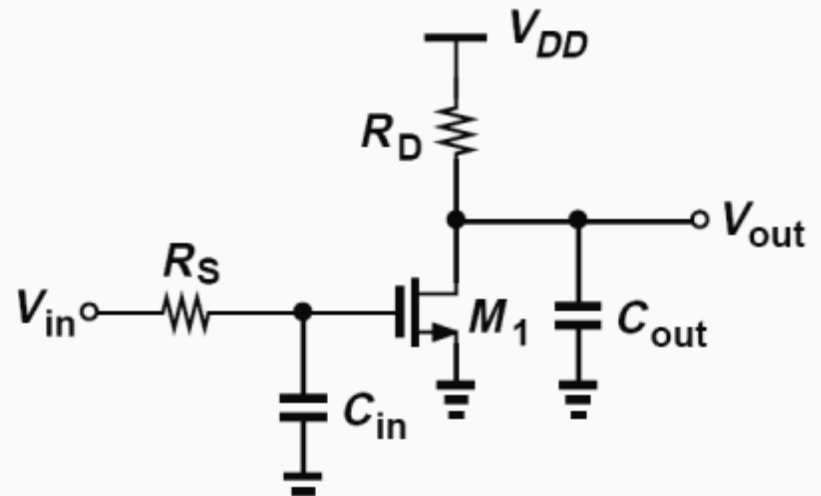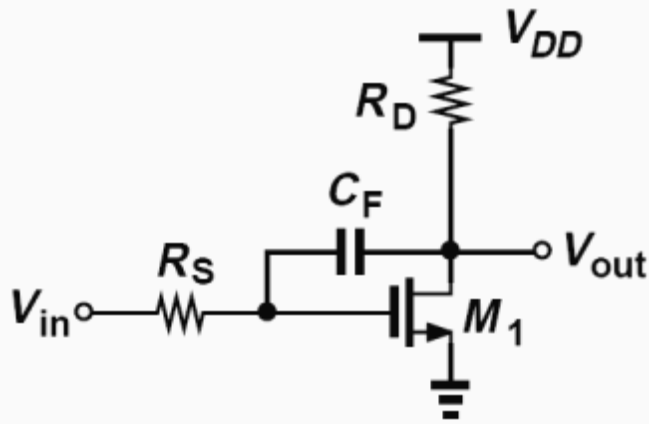

$$A_0 = -g_m R_D$$

$$C_{in} = (1 - A_0)C_F = (1 + g_m R_D)C_F$$

$$C_{out} = (1 - 1/A_0)C_F = \left(1 + \frac{1}{g_m R_D}\right)C_F$$

$$\omega_{p,in} = \frac{1}{R_S \cdot C_{in}} = \frac{1}{R_S (1 + g_m R_D) C_F}$$

$$\omega_{p,out} = \frac{1}{R_D \cdot C_{out}} = \frac{1}{R_D \left(1 + \frac{1}{g_m R_D}\right) C_F}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{-g_m R_D}{\left(1 + \frac{s}{\omega_{p,in}}\right) \left(1 + \frac{s}{\omega_{p,out}}\right)}$$




Demerits

1. Discard zeros
2. Approximating gain




MOS Intrinsic Capacitances ?

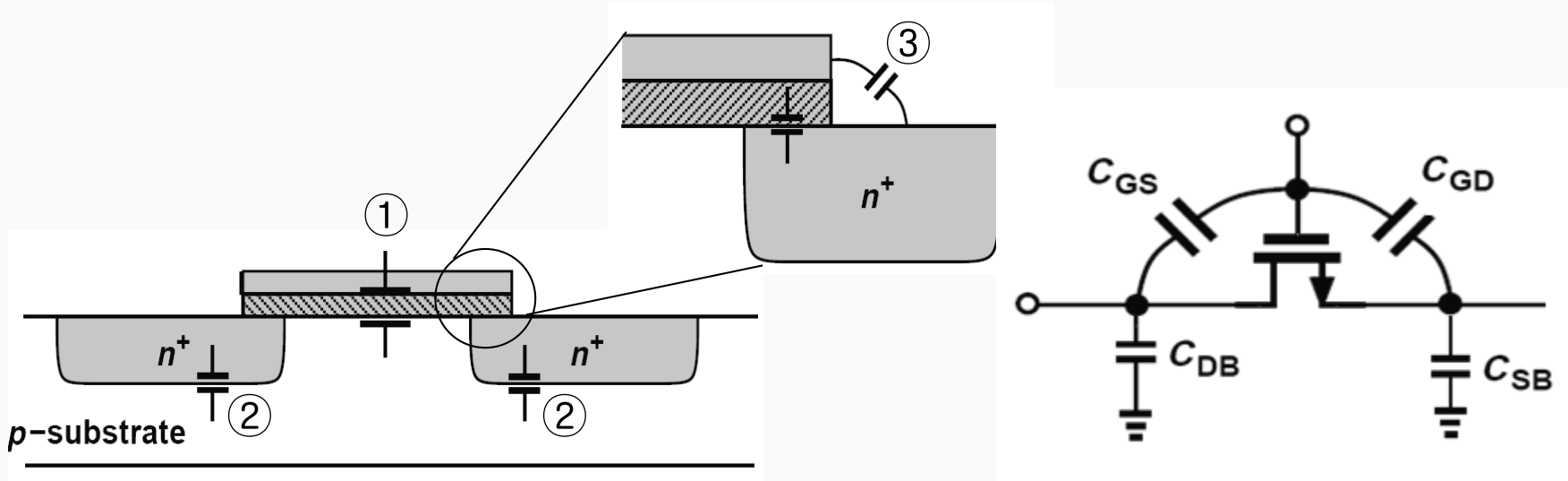

- ① Oxide capacitance ② Junction capacitances ③ Overlap capacitance


Small-signal equivalent circuit

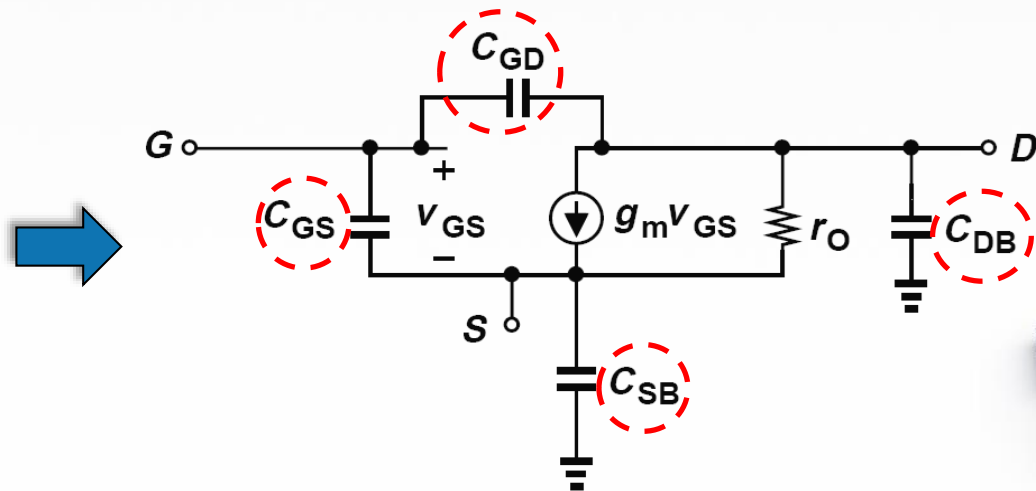

Frequency Response of CS Stage

Use the Miller theorem

$$r_o = \infty$$

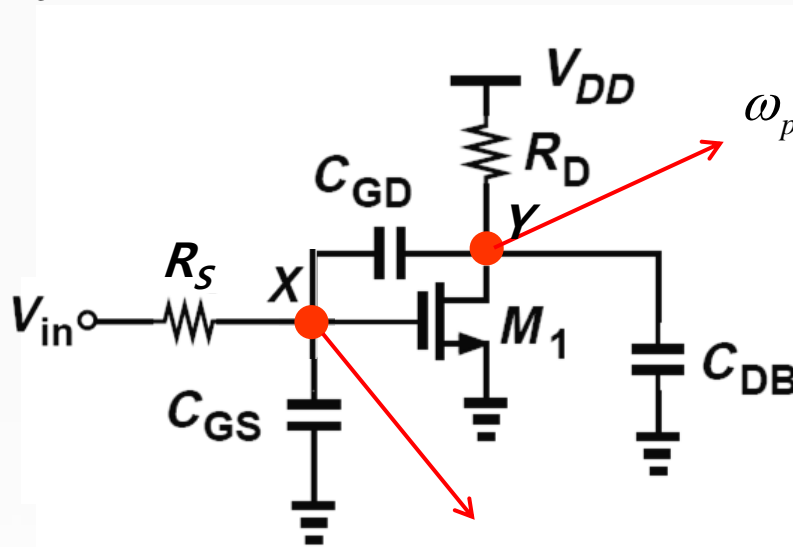

$$\omega_{p,Y} = \frac{1}{R_D \left[C_{DB} + \left(1 + \frac{1}{g_m R_D} \right) C_{GD} \right] s}$$

Miller theorem



$$\omega_{p,X} = \frac{1}{R_S \left[C_{GS} + \left(1 + g_m R_D \right) C_{GD} \right] s}$$

Miller theorem



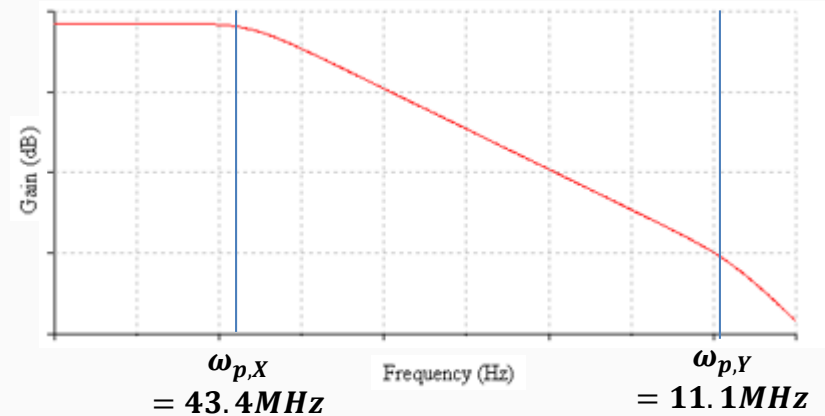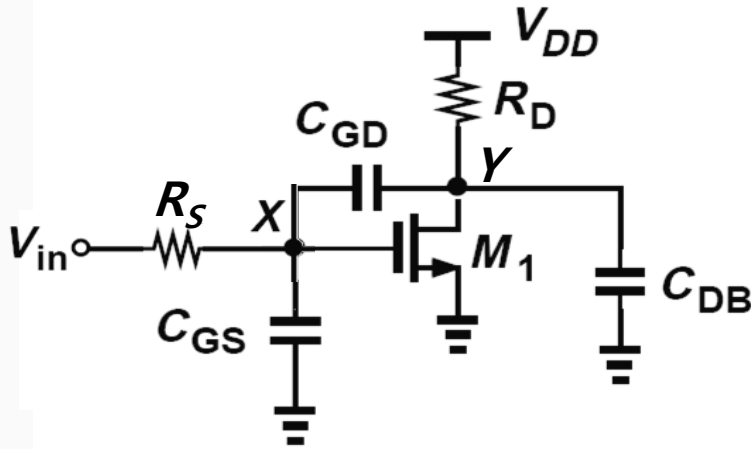
Example 1

Calculate the $\omega_{p,X}$, $\omega_{p,Y}$ (if, $g_m = 150\mu A/V$, $R_S = 100k\Omega$, $R_D = 40k\Omega$, $C_{GS} = 23fF$, $C_{GD} = 2fF$, $C_{DB} = 35fF$)






$$\begin{aligned}\omega_{p,X} &= \frac{1}{R_S \left[C_{GS} + (1 + g_m R_D) C_{GD} \right] s} \\ &= \frac{1}{100k \cdot \left[23f + (1 + 150\mu \cdot 40k) \cdot 2f \right] \cdot 2\pi} \\ &= \frac{1}{100k \cdot \left[23f + (1 + 150\mu \cdot 40k) \cdot 2f \right] \cdot 2\pi} \\ &= 43.4MHz\end{aligned}$$
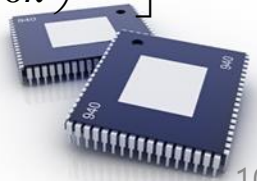
$$\begin{aligned}\omega_{p,Y} &= \frac{1}{R_D \left[C_{DB} + \left(1 + \frac{1}{g_m R_D} \right) C_{GD} \right] s} \\ &= \frac{1}{40k \cdot \left[35f + \left(1 + \frac{1}{150\mu \cdot 40k} \right) 2f \right] \cdot 2\pi} \\ &= 111.1MHz\end{aligned}$$



Frequency Response of CS Stage

Use the equivalent circuit

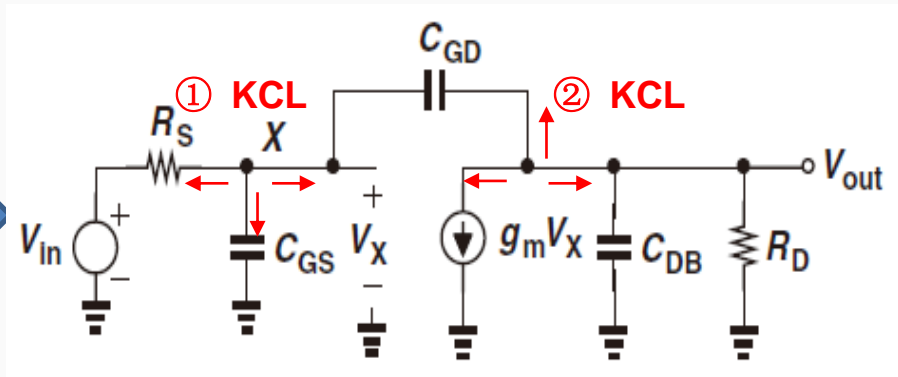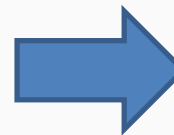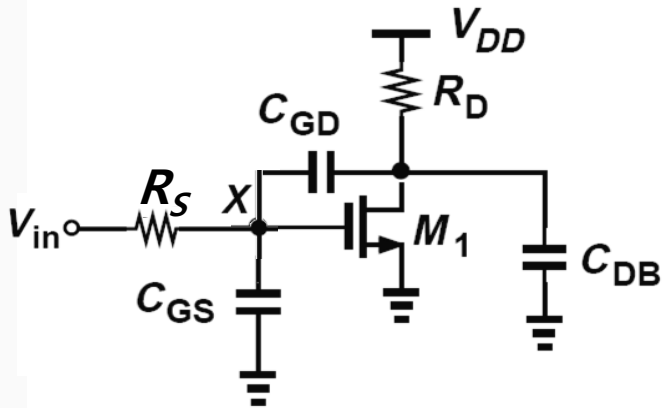

$$\textcircled{1} \quad \frac{V_X - V_{in}}{R_S} + V_X C_{GS} s + (V_X - V_{out}) C_{GD} s = 0$$


$$\textcircled{2} \quad (V_{out} - V_X) C_{GD} s + g_m V_X + V_{out} \left(\frac{1}{R_D} + C_{DB} s \right) = 0$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{GD} s - g_m) R_D}{R_S R_D \xi s^2 + [R_S (1 + g_m R_D) C_{GD} + R_S C_{GS} + R_D (C_{GD} + C_{DB})] s + 1}$$

$$(\xi = C_{GS} C_{GD} + C_{GS} C_{DB} + C_{GD} C_{DB})$$



Frequency Response of CS Stage

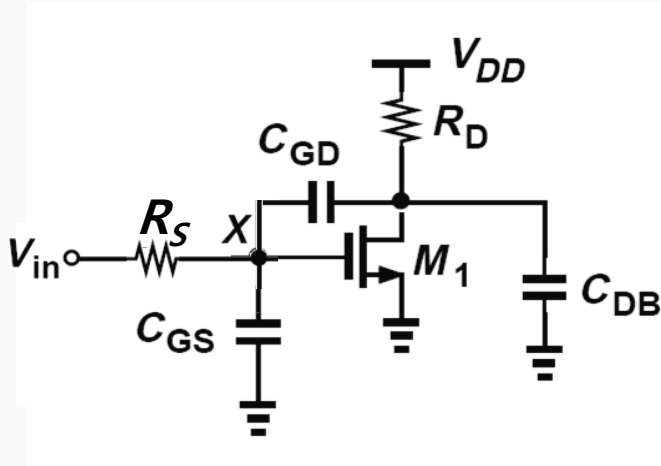


Use the equivalent circuit

$$\omega_{p1} = \frac{1}{R_S (1 + g_m R_D) C_{GD} + R_S C_{GS} + R_D (C_{GD} + C_{DB})}$$

$$\omega_{p2} = \frac{R_S (1 + g_m R_D) C_{GD} + R_S C_{GS} + R_D (C_{GD} + C_{DB})}{R_S R_D (C_{GS} C_{GD} + C_{GS} C_{DB} + C_{GD} C_{DB})}$$

$$\text{If, } C_{GS} \gg \frac{(1 + g_m R_D) C_{GD} + R_D (C_{GD} + C_{DB})}{R_S}$$

$$= \frac{1}{R_D (C_{GD} + C_{DB})}$$

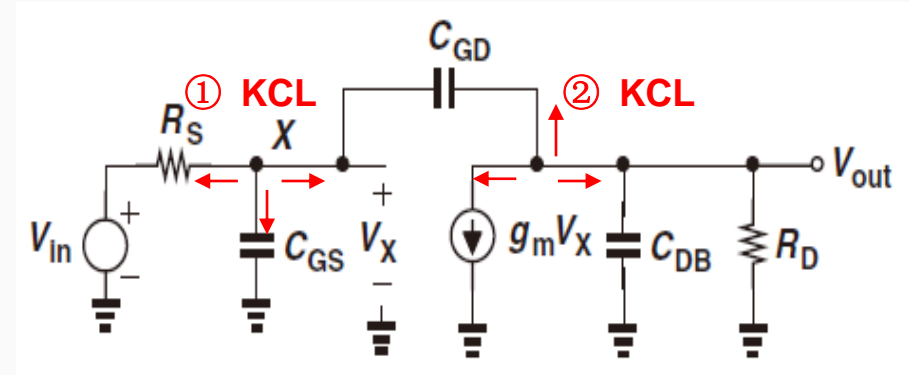

Use the Miller theorem


$$\omega_{p1} = \frac{1}{R_S [C_{GS} + (1 + g_m R_D) C_{GD}] s}$$

$$\omega_{p2} = \frac{1}{R_D [C_{DB} + (1 + \frac{1}{g_m R_D}) C_{GD}] s}$$



Frequency Response of CG Stage



$$r_o = \infty$$

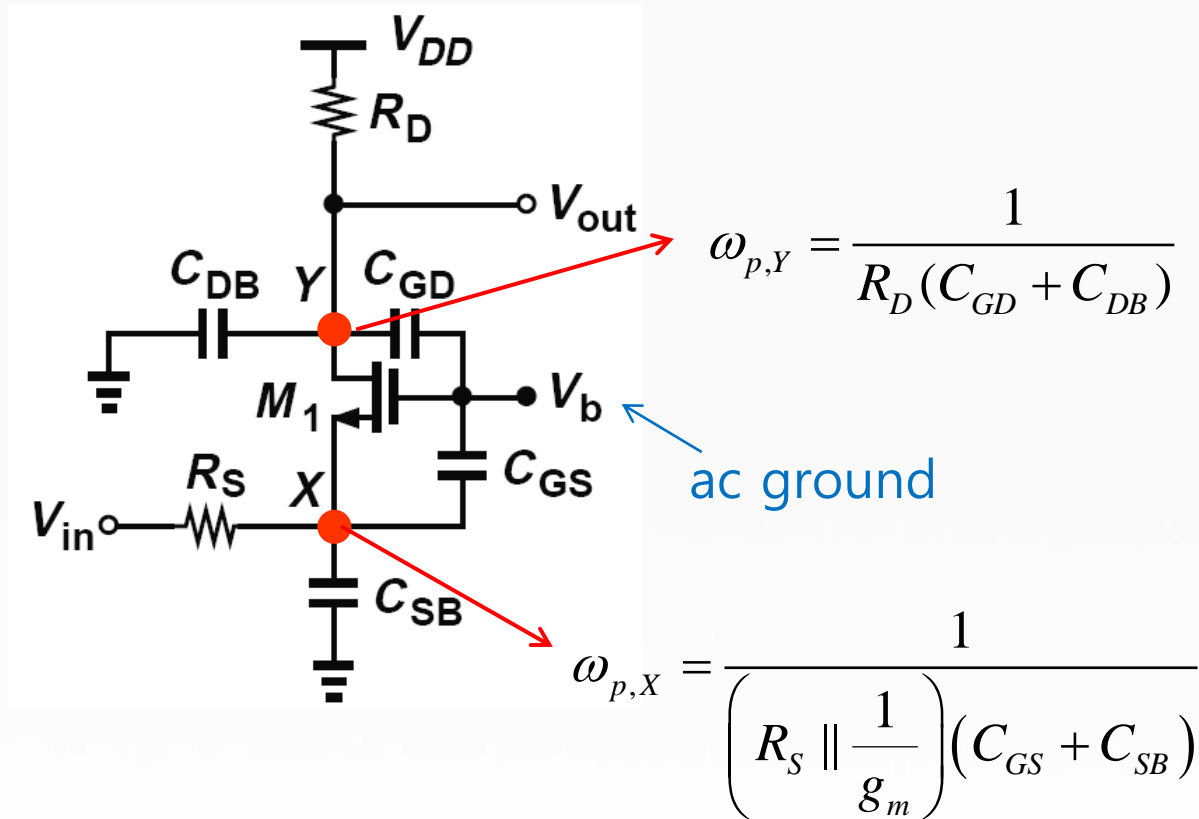

High speed (No miller effect)



Frequency Response of SF Stage

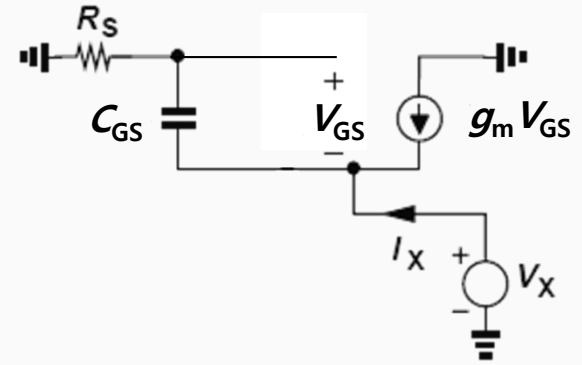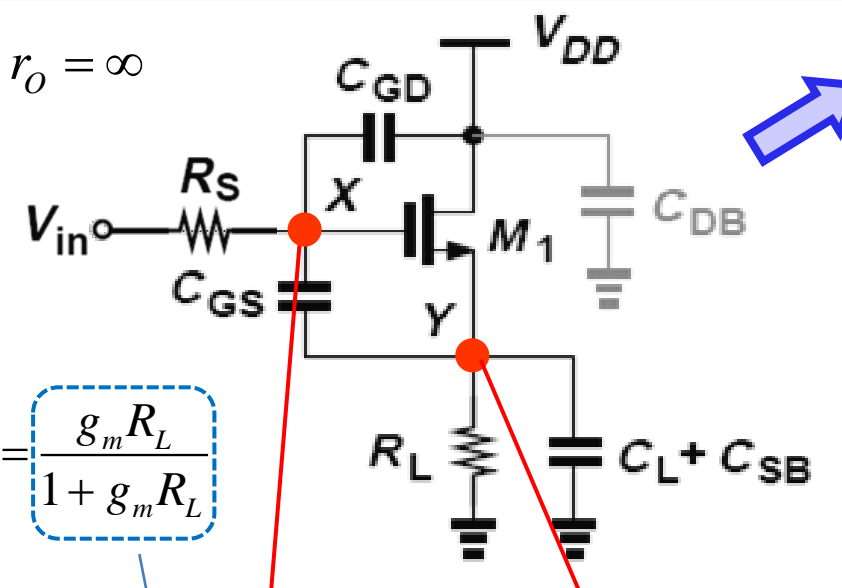

$$A_v = \frac{R_L}{R_L + \frac{1}{g_m}} = \frac{g_m R_L}{1 + g_m R_L}$$

$$\omega_{p,X} = \frac{1}{R_S \cdot (C_{GD} + (1 - A_v) C_{GS})}$$

$$= \frac{1}{R_S \cdot \left(C_{GD} + \frac{C_{GS}}{1 + g_m R_L} \right)}$$

$$(I_X + g_m V_{GS}) \left(\frac{1}{C_{GS} s} \right) = -V_{GS}$$


$$V_{GS} = -I_X \frac{1}{C_{GS} s + g_m}$$

Using KVL


$$(I_X + g_m V_{GS}) R_S - V_{GS} = V_X$$

$$\therefore Z_{out} = \frac{V_X}{I_X} = \frac{R_S C_{GS} s + 1}{C_{GS} s + g_m}$$
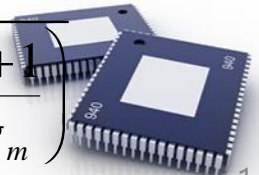
$$\omega_{p,Y} = \frac{1}{R_L \cdot \left(C_L + C_{SB} + \frac{R_S C_{GS} s + 1}{C_{GS} s + g_m} \right)}$$





Output Impedance of Source Follower

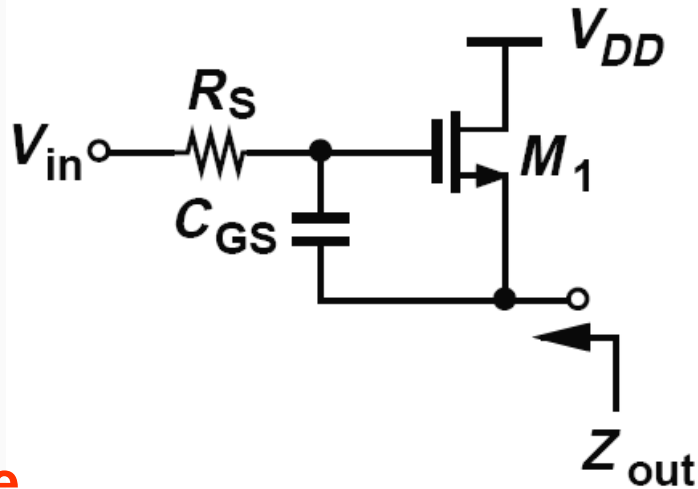


$$Z_{out} = \frac{V_X}{I_X} = \frac{R_S C_{GS} s + 1}{C_{GS} s + g_m}$$

$$\left. \begin{aligned} s = 0 &\Rightarrow Z_{out} = \frac{1}{g_m} \\ s = \infty &\Rightarrow Z_{out} = R_S \end{aligned} \right\}$$


Source
Follower

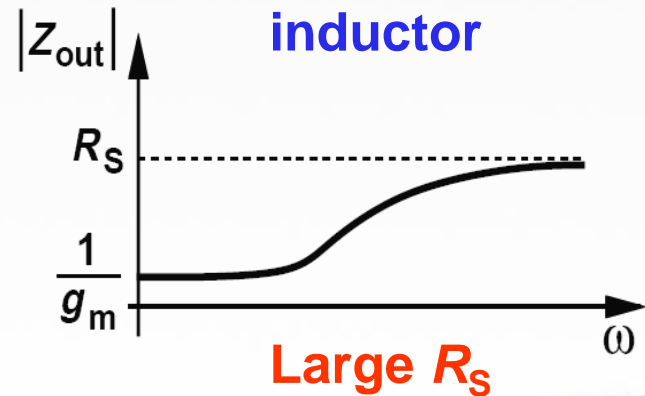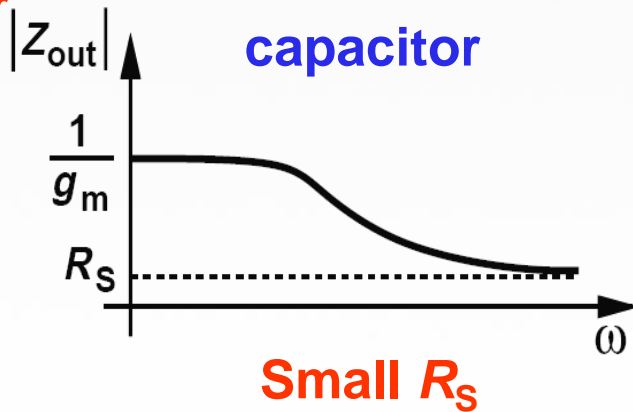


Poles of MOS Cascode

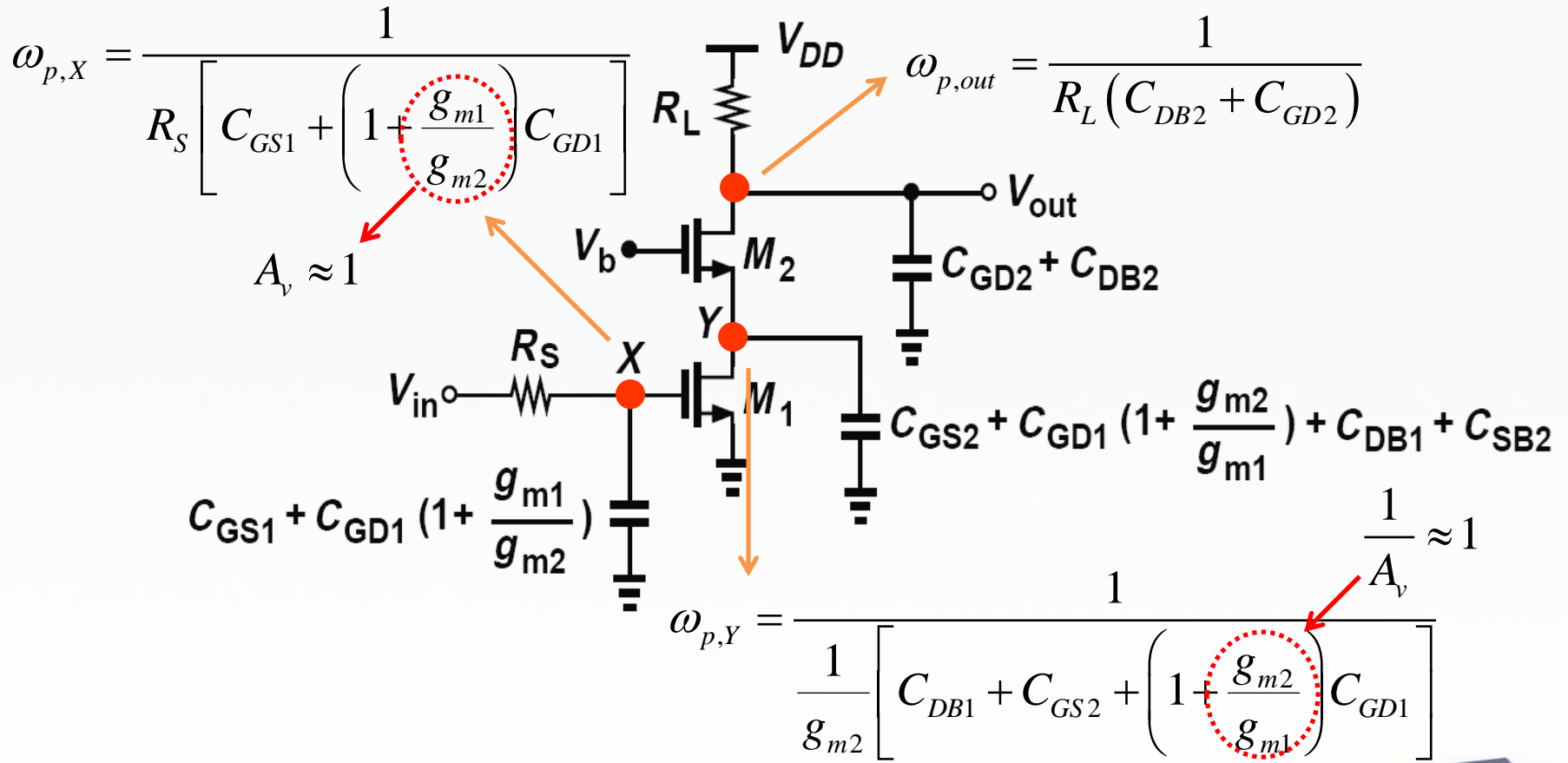

High speed(reject the miller effect)

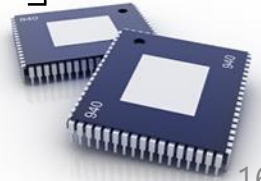

Differential Pair Frequency Response

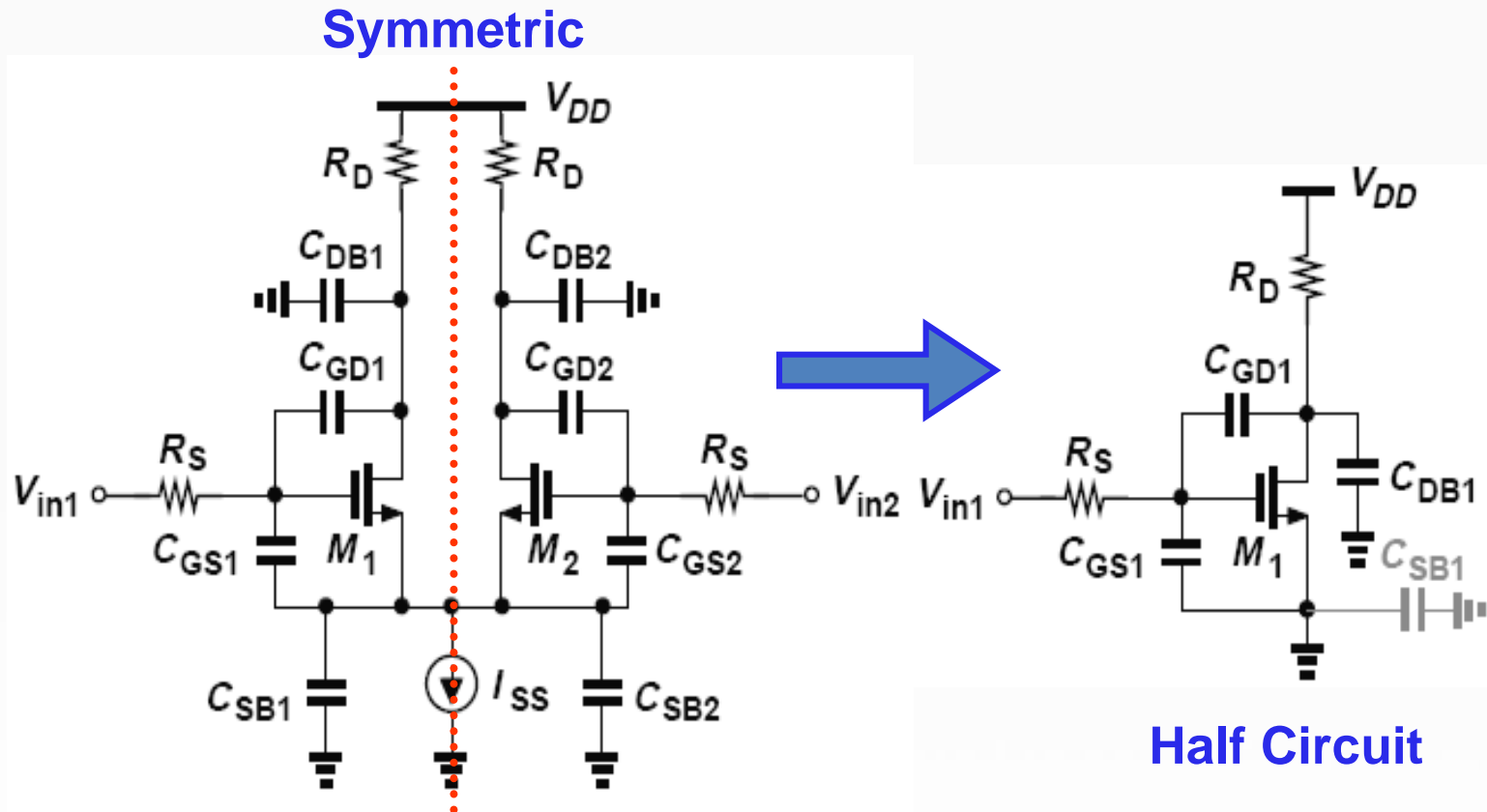

its transfer function, I/O impedances, locations of poles/zeros are the **same as that of the half circuit's**.

