

# LECTURE 2

Soo-Won Kim  
[swkim@korea.ac.kr](mailto:swkim@korea.ac.kr)

# **3. Basic Current Mirrors and Single-Stage Amplifiers**

**3.1 Simple CMOS Current Mirrors**

**3.2 Common-Source Amplifier**

**3.3 Source-Follower or Common-Drain Amplifier**

**3.4 Common-Gate Amplifier**

**3.5 Source-Degenerated Current Mirrors**


**3.6 Cascode Current Mirrors**

**3.7 Cascode Gain Stage**

**3.8 MOS Differential Pair and Gain Stage**




# Differential Pair

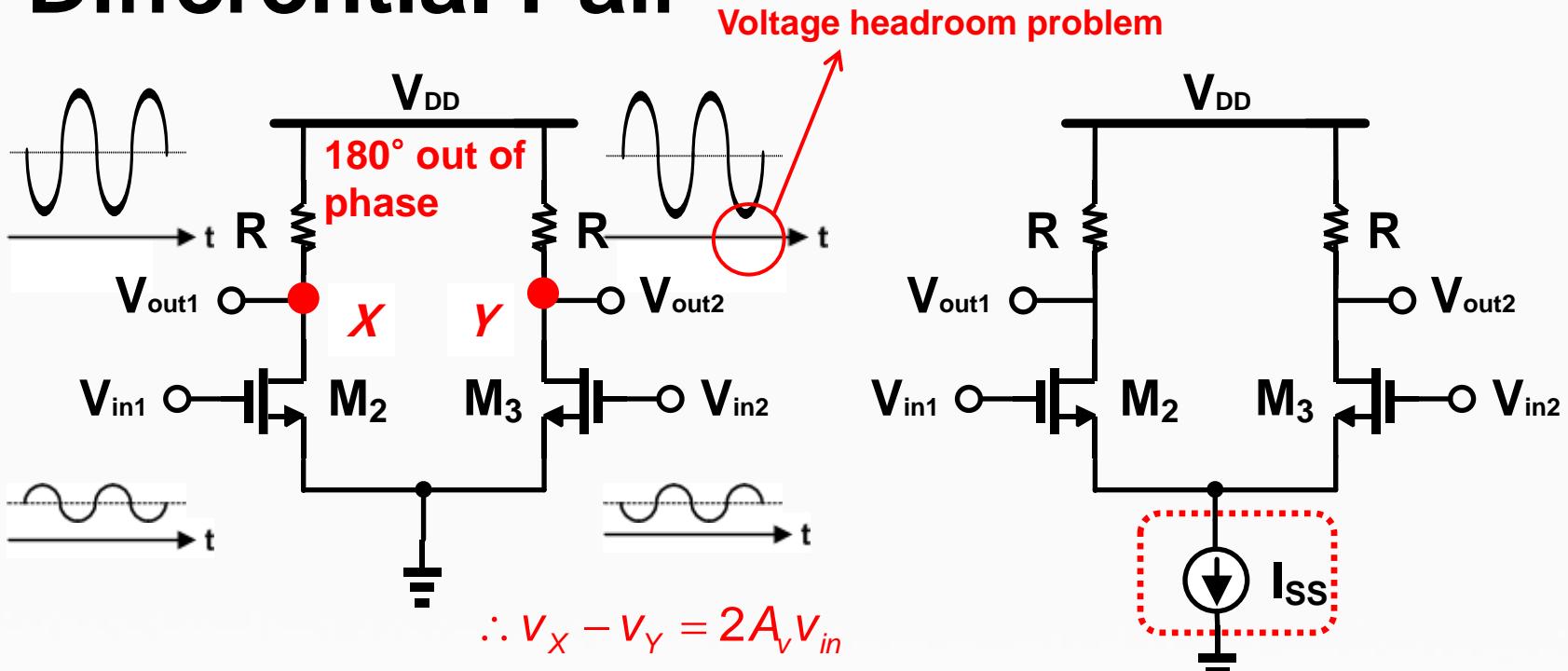

## Merits

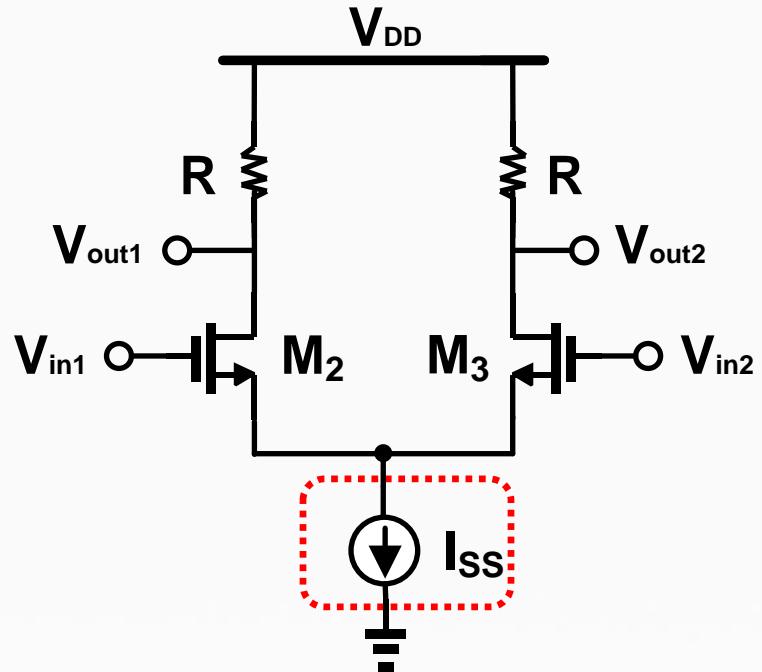1. High noise rejection
2. High output swings




Constant current source  
(Tail current source)



The  $g_m$  and the output CM level are varying



# Common-Mode Response

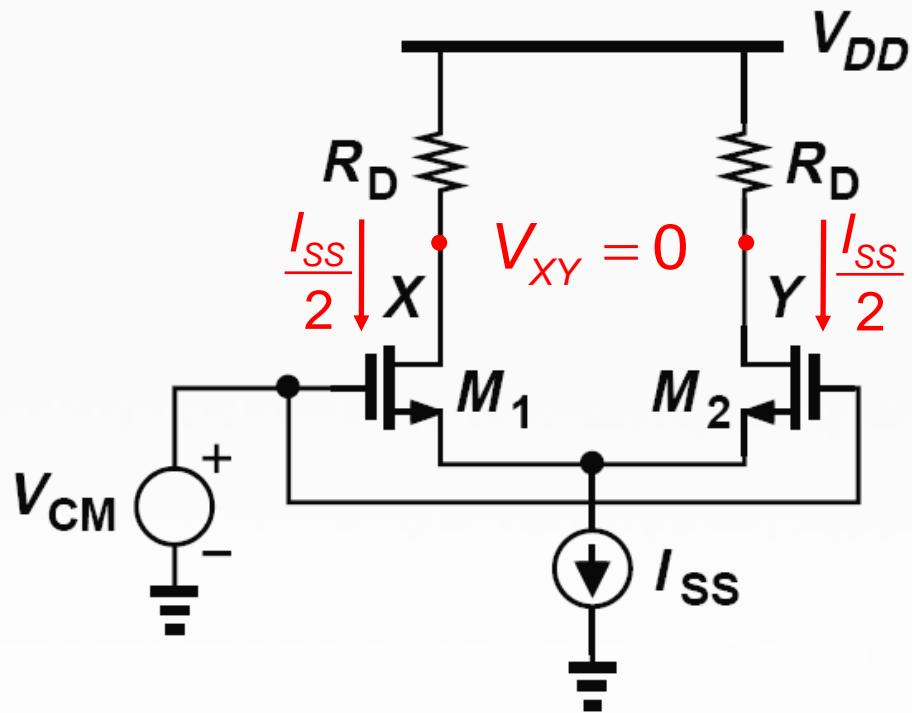

$$V_{G1} = V_{G2} = V_{CM}, \quad I_{D1} = I_{D2} = \frac{I_{SS}}{2}$$

$$V_X = V_Y = V_{DD} - R_D \frac{I_{SS}}{2}$$

$$V_{out,CM} \Rightarrow V_{XY} = 0$$

For operation in saturation region

$$V_{DS} > V_{GS} - V_{TH}$$

$$V_D > V_G - V_{TH}$$

$$V_{CM} < V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH}$$



# Example 1

a) Gain이 5이고 Power consumption이 2mW인 NMOS differential pair를 설계하는데, differential pair를 따르는 단이 적어도 1.6V의 Output CM level을 요구하는 것을 조건으로 한다.  $\mu_n C_{ox} = 100 \mu A/V^2$ ,  $\lambda = 0$ , 그리고  $V_{DD} = 1.8V$ 로 가정한다. 이때 W/L을 구하여라.

Sol) 한계 전력 소모와  $V_{DD}$ 로부터  $I_{ss}$ 를 구한다.

$$I_{ss} = 1.11mA$$

Output CM level은 다음과 같다.

$$V_{CM,out} = V_{DD} - R_D \frac{I_{ss}}{2}$$

$V_{CM,out} = 1.6V$ 를 위해서 계산을 하면  $R_D$ 는 다음과 같다.

$$R_D \leq \frac{2}{I_{ss}}(V_{DD} - 1.6) \rightarrow R_D = 360\Omega$$

$g_m R_D = 5$ 이고, 각 트랜지스터에  $\frac{I_{ss}}{2}$ 가 흐르므로

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} \frac{I_{ss}}{2}} = \frac{5}{360\Omega}$$

이에 따라서 W/L은  $\frac{W}{L} = 1738$  가 된다.



# Example 1

b) (a)의 예제에서  $V_{TH} = 0.4V$ 라면 허용 가능한 최대 input CM level은 얼마인가?

Sol)  $V_{CM,in}$ 은 다음과 같이 정리 할 수 있다.

$$V_{CM,in} < V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH}$$

$V_{CM,out} = V_{DD} - R_D \frac{I_{SS}}{2}$  이므로 정리하면 다음과 같다.




$$V_{CM,in} < V_{CM,out} + V_{TH}$$

$V_{CM,out} = 1.6V$ ,  $V_{TH} = 0.4V$  이므로

$$V_{CM,in} < 2V$$



# Differential Response

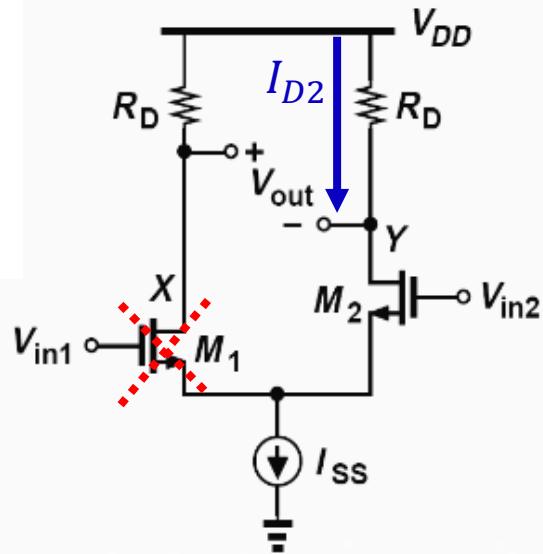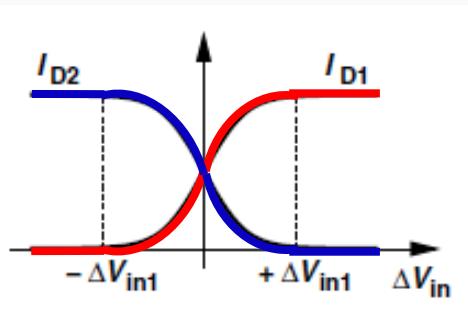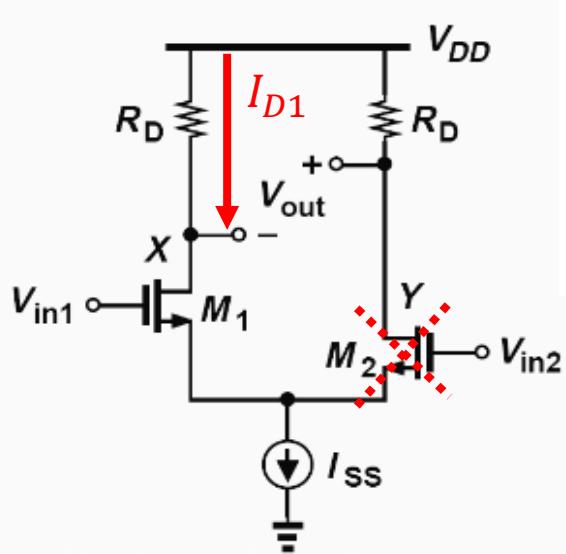

$$V_{in1} > V_{in2}$$

$$I_{D1} = I_{ss}$$

$$I_{D2} = 0$$

$$V_X = V_{DD} - R_D I_{ss}$$

$$V_Y = V_{DD}$$

$$V_{in1} < V_{in2}$$

$$I_{D2} = I_{ss}$$

$$I_{D1} = 0$$


$$V_Y = V_{DD} - R_D I_{ss}$$

$$V_X = V_{DD}$$




# Small-Signal Response

## ❖ Virtual Ground and Half Circuit

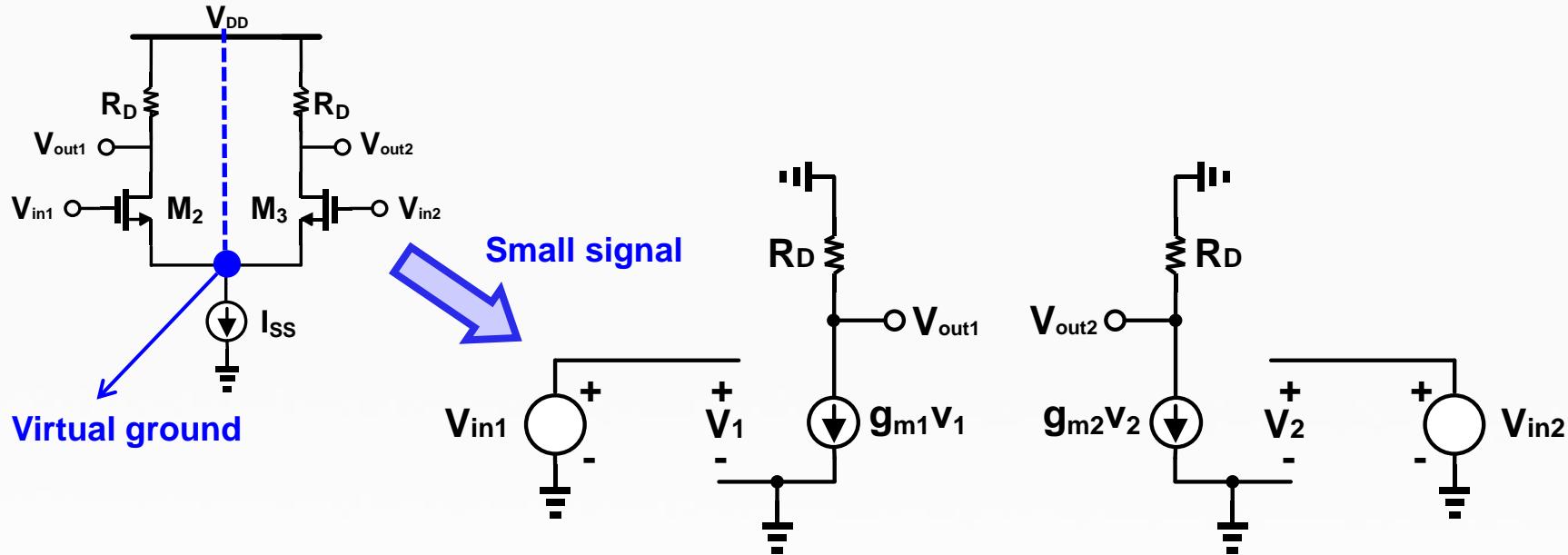

$$V_{out1} = -g_{m1}R_D V_{in1}$$

$$V_{out2} = -g_{m2}R_D V_{in2}$$

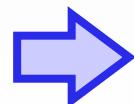


$$A_V = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = -g_{m1,2}R_D$$



# CM to DM Conversion, $A_{CM-DM}$

**Asymmetric loads( $\Delta R_D$ )**

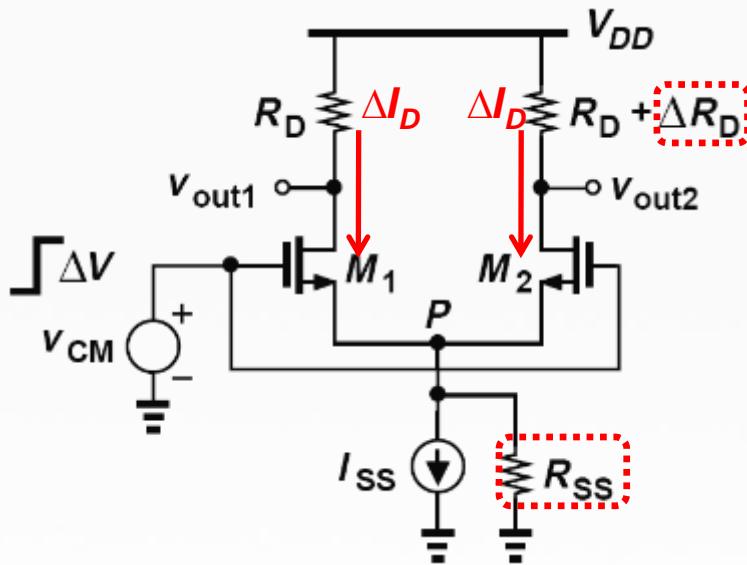

$$\Delta V_{CM} = \Delta V_{GS} + 2\Delta I_D R_{SS}$$

since  $\Delta V_{GS} = \Delta I_D / g_m$ ,

$$\Delta V_{CM} = \Delta I_D (1/g_m + 2R_{SS})$$

$$\Delta I_D = \frac{\Delta V_{CM}}{1/g_m + 2R_{SS}}$$

$$\begin{aligned}\Delta V_{out} &= \Delta V_{out1} - \Delta V_{out2} \\ &= \Delta I_D R_D - \Delta I_D (R_D + \Delta R_D) \\ &= -\Delta I_D \Delta R_D\end{aligned}$$

$$= -\frac{\Delta V_{CM}}{1/g_m + 2R_{SS}} \Delta R_D$$

$$\therefore |A_{CM-DM}| = \left| \frac{\Delta V_{out}}{\Delta V_{CM}} \right| = \frac{\Delta R_D}{\frac{1}{g_m} + 2R_{SS}}$$

In ideal case,

$$R_{SS} \rightarrow \infty,$$

$$\Delta R_D \rightarrow 0,$$


$$\therefore A_{CM-DM} = 0$$



# CMRR
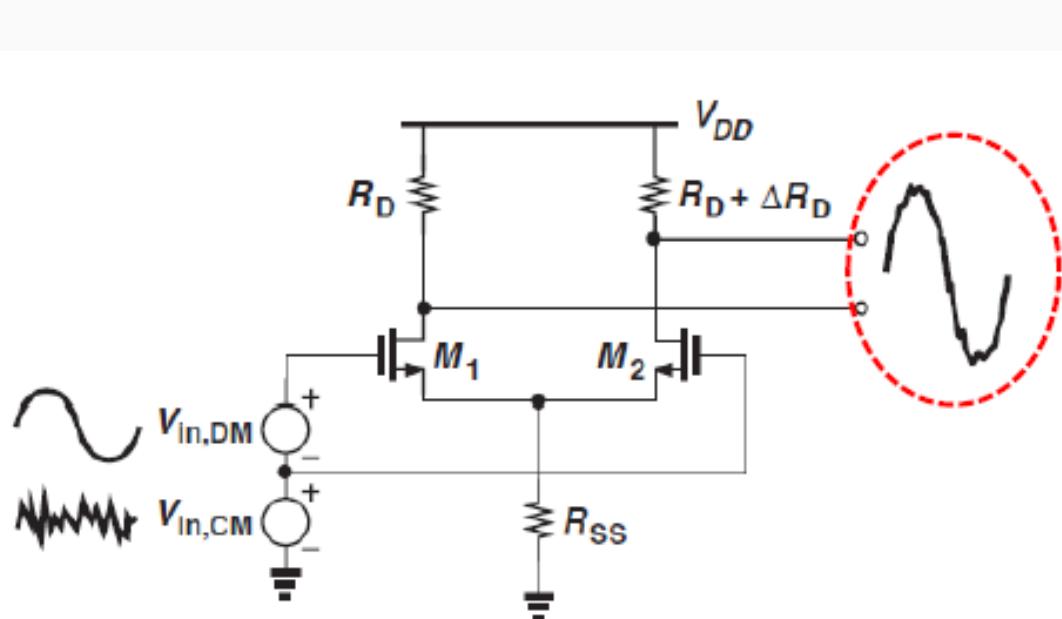
## Common-mode rejection ratio (CMRR)

: Input의 Common noise의 Variation이 얼만큼 output에서 제거되는가



$$\begin{aligned} CMRR &= \left| \frac{A_{DM}}{A_{CM-DM}} \right| \\ &= \frac{g_m \cdot R_D}{\frac{1}{g_m} + 2R_{SS}} \end{aligned}$$

In ideal case

$$A_{CM-DM} = 0,$$

$$\therefore CMRR \rightarrow \infty$$



# Example 2

$W_3 = 10\mu m$ ,  $W_4 = 11\mu m$  일 때 CMRR를 구하여라.

Sol) CMRR은 다음과 같이 정리 할 수 있다.

$$CMRR = \frac{g_m \cdot R_D}{\Delta R_D} = \frac{\frac{1+2g_{m1}R_{ss}}{R_D}}{\frac{1}{g_m} + 2R_{ss}}$$

$M_{3,4}$ 는 R로 바꾸어주면 다음과 같다.


$$R_{D1} = \frac{1}{g_{m3}}, R_{D2} = \frac{1}{g_{m4}}$$

R 값이 위와 같을 때 Miss match를 계산해주면,


$$\frac{\Delta R_D}{R_D} = \frac{R_{D1} - R_{D2}}{R_{D1}} = 1 - \frac{R_{D2}}{R_{D1}} = 1 - \frac{g_{m3}}{g_{m4}} = 1 - \frac{\sqrt{2\mu_p C_{ox} (\frac{W}{L})_3 I_D}}{\sqrt{2\mu_p C_{ox} (\frac{W}{L})_4 I_D}} = 1 - \sqrt{\frac{10}{11}} = 0.0465$$

위의 CMRR의 수식에 대입을 하면,

$$CMRR = 2248$$

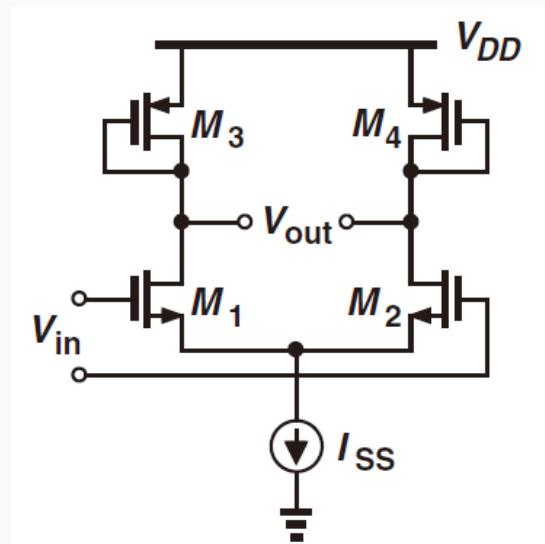
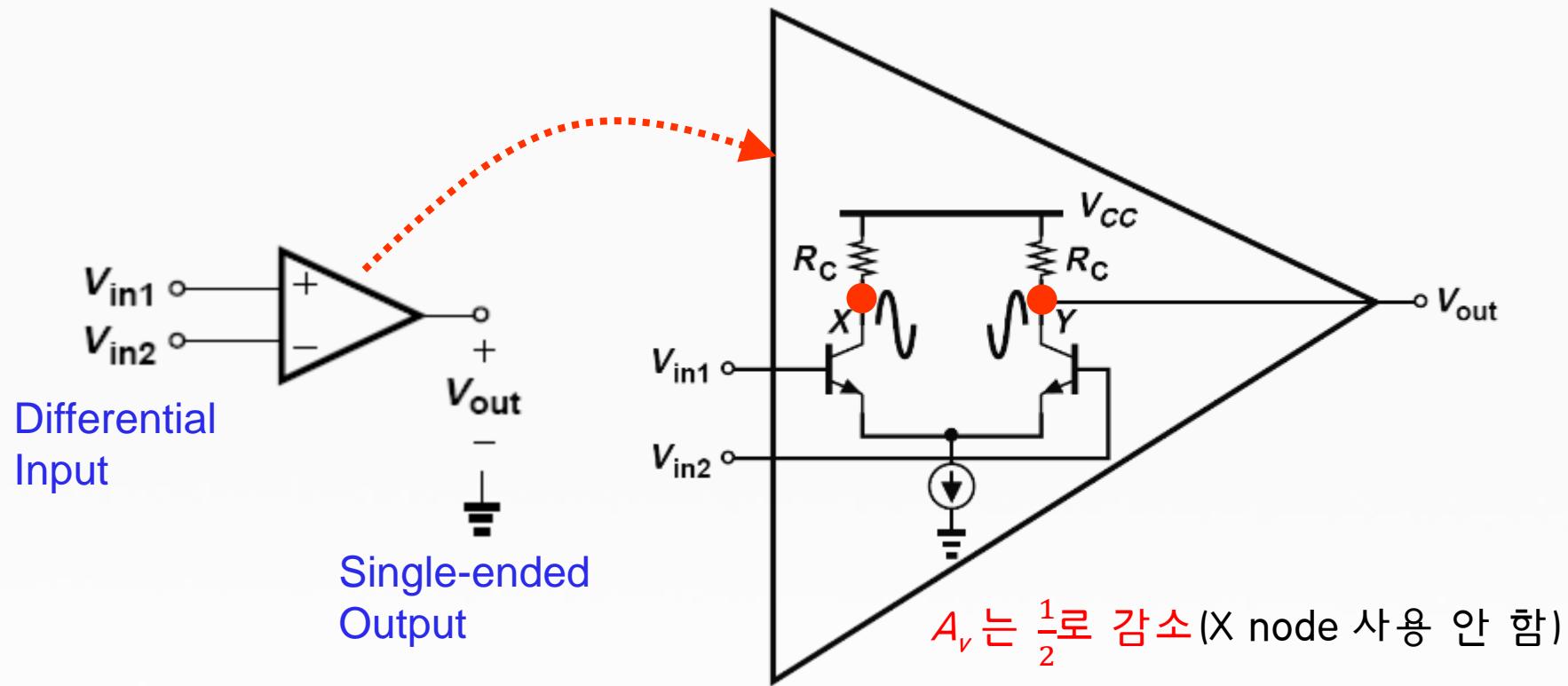
# Differential to Single-ended Conversion




Many circuits require a differential to single-ended conversion, however, the above topology is not very good. ( $A_v$  감소)



# Better Alternative


## ❖ Active load – Current mirror

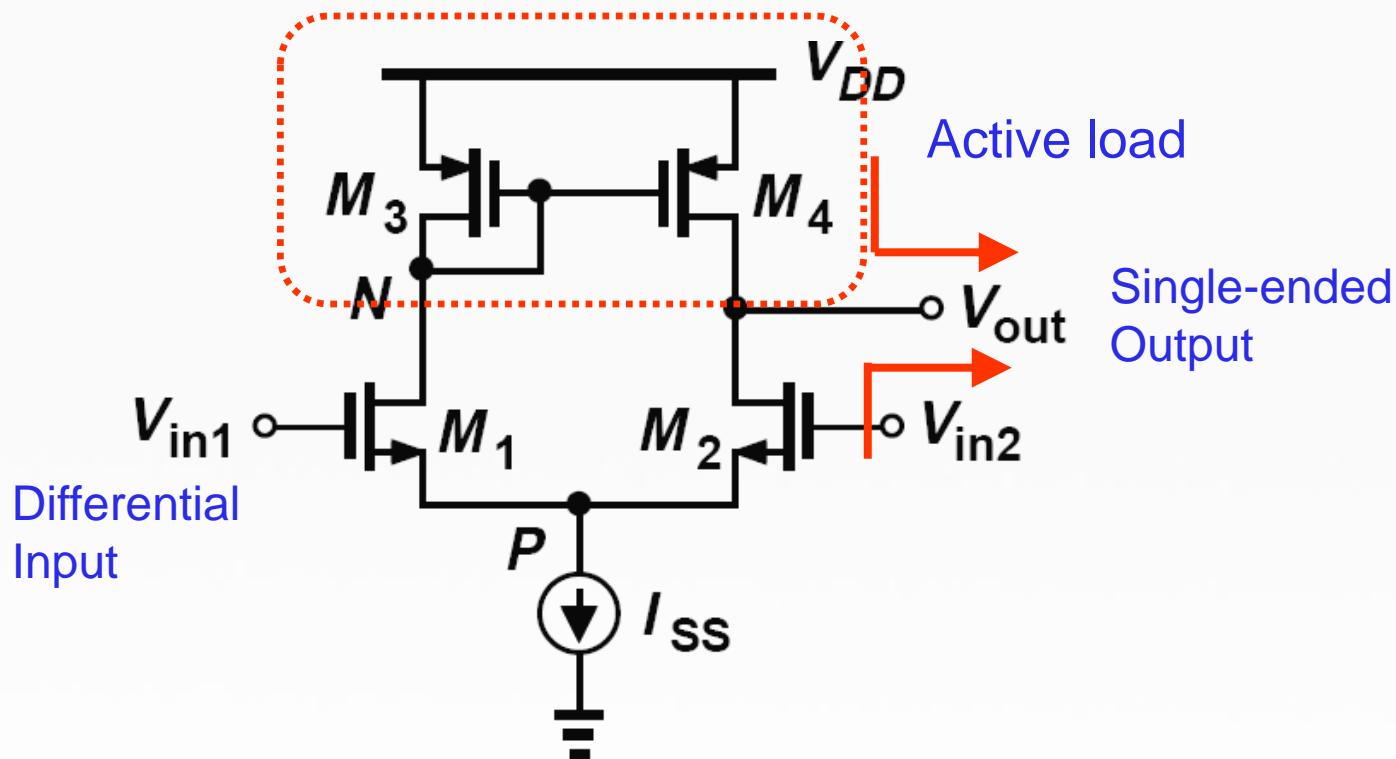

This circuit topology performs differential to single-ended conversion **with no loss of gain**.



# MOS Differential Pair with Active Load

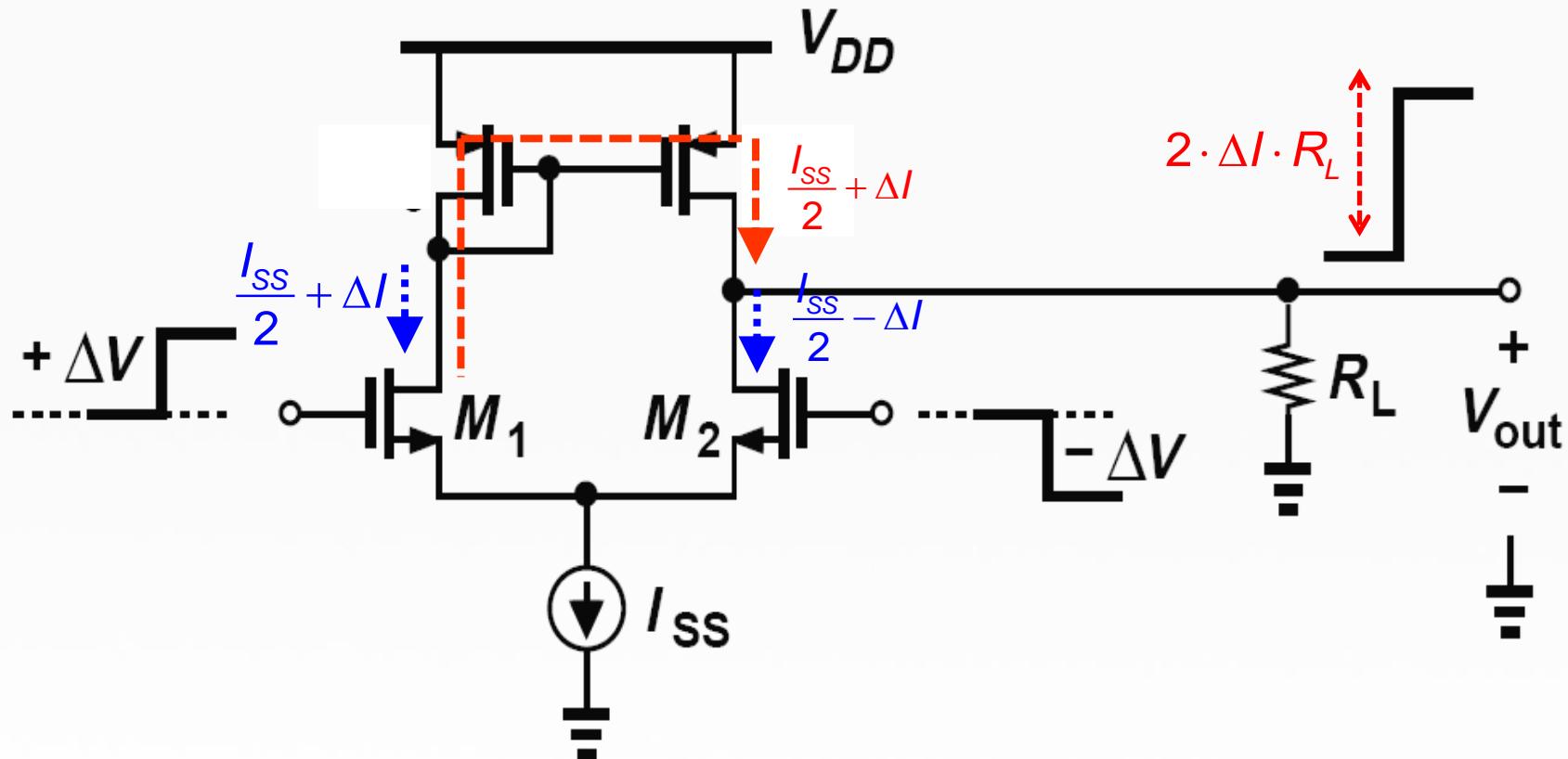


This type of load is different from the conventional “static load” and is known as an “active load”.


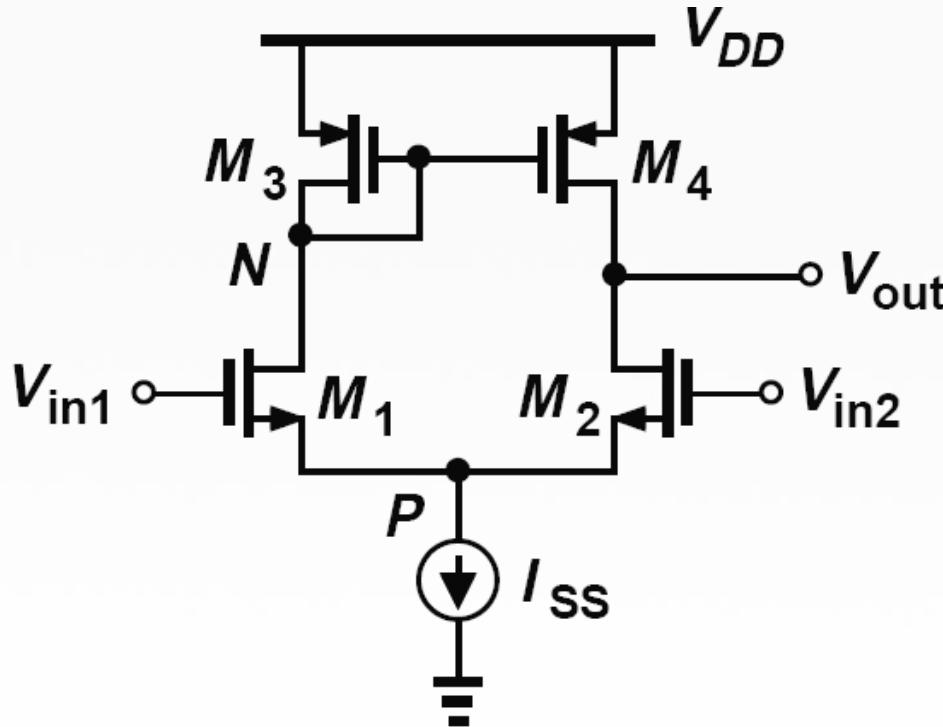
# How are the gain calculated?

❖ Gain? -> half circuit (Asymmetric load)

- > ① Small signal  
② Thevenin equivalent



# Use the small signal

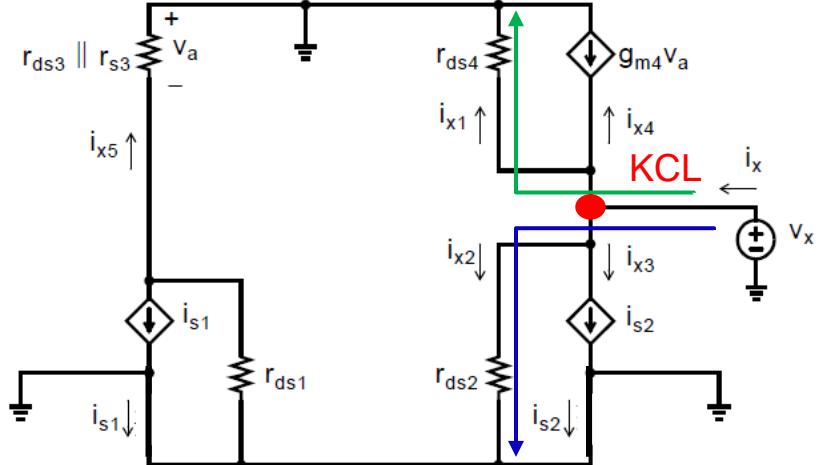
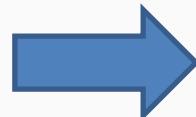
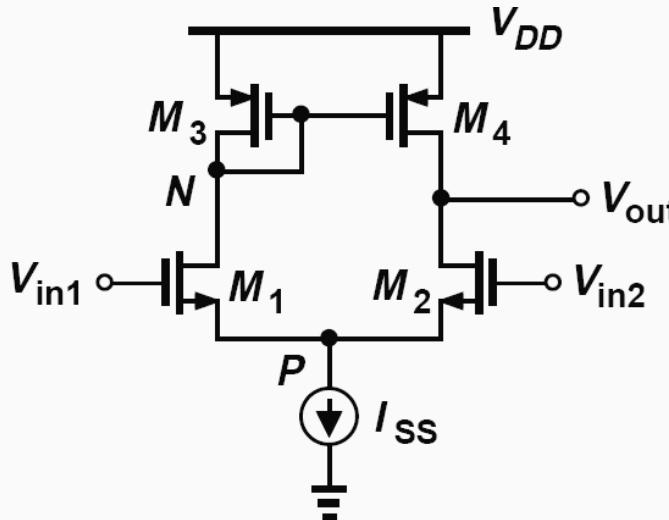


Fig. 3.20 The small-signal model

Current mirror

$$i_{x4} = i_{x5} = -i_{s1} = -i_{s2} = -i_{x3} \quad (3.76)$$

$$i_{x1} = \frac{V_x}{r_{ds4}} \quad i_{x2} = \frac{V_x}{r_{ds2}} \quad (3.73, 3.74)$$


$$i_{x1} = \frac{V_x}{r_{ds4}} \quad i_{x2} = \frac{V_x}{r_{ds2}} \quad (3.73, 3.74)$$

$$r_{out} = \frac{V_x}{i_x} = \frac{V_x}{i_{x1} + i_{x2} + i_{x3} + i_{x4}} = \frac{V_x}{\left(\frac{V_x}{r_{ds4}}\right) + \left(\frac{V_x}{r_{ds2}}\right)} \quad (3.77)$$



$$r_{out} = r_{ds2} \parallel r_{ds4} \quad (3.78)$$

$$i_{s1} = i_{s2} = -\frac{V_x}{2r_{ds2}} \quad (3.75)$$
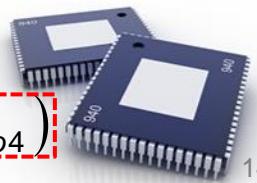
$$A_v = g_m r_{out} = g_{m1} (r_{ds2} \parallel r_{ds4}) = g_{m1} (r_{o2} \parallel r_{o4}) \quad (3.79)$$


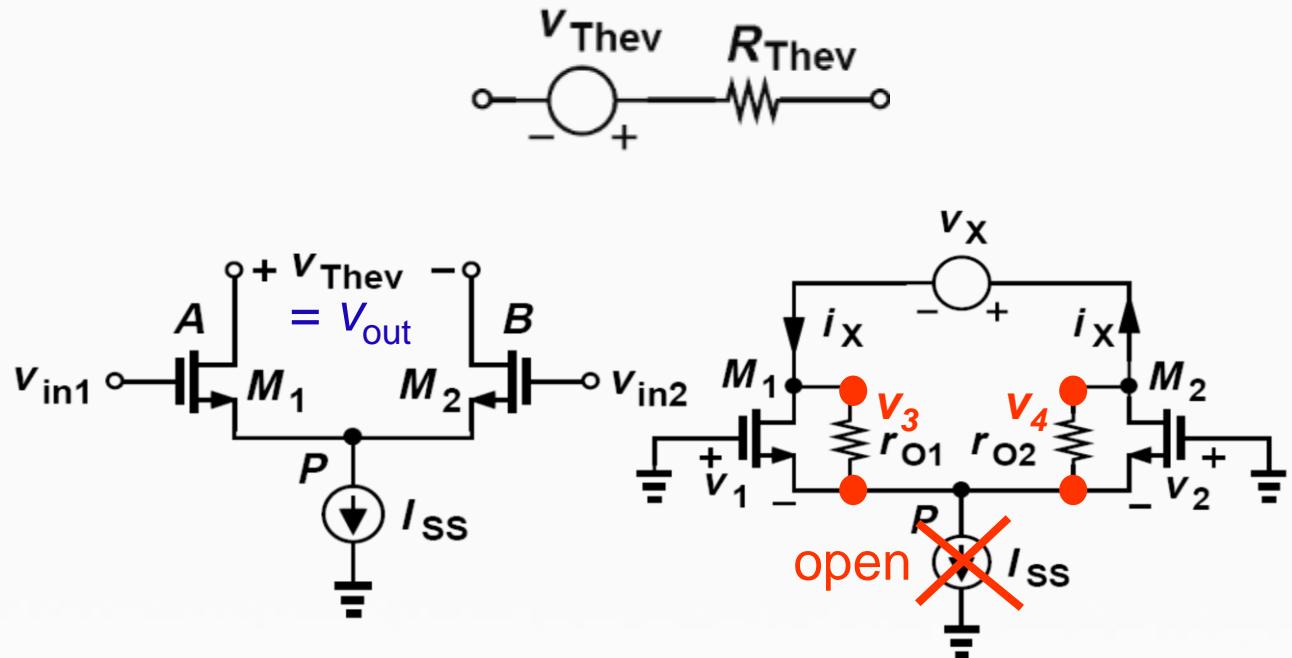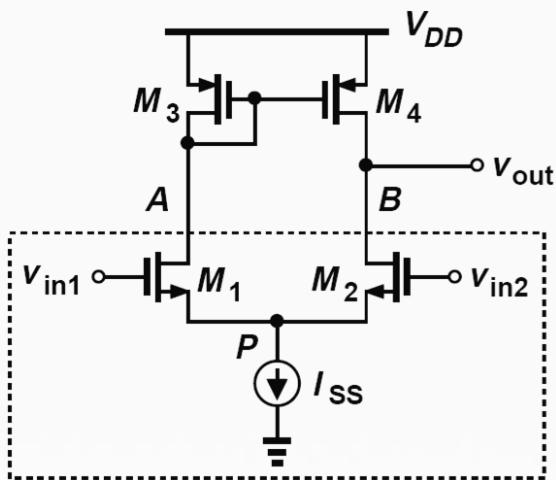
# $V_{\text{Thev}}$ and $R_{\text{Thev}}$



$$V_3 + V_4 = V_X$$

$$(i_X - g_{m1}v_1)r_{o1} + (i_X + g_{m2}v_2)r_{o2} = V_X$$


since  $v_1 = v_2$ ,  $g_{m1} = g_{m2}$ ,  $r_{o1} = r_{o2} = r_{oN}$

$$i_X r_{oN} + i_X r_{oN} = V_X$$

$$\therefore R_{\text{Thev}} = \frac{V_X}{i_X} = 2r_{oN}$$


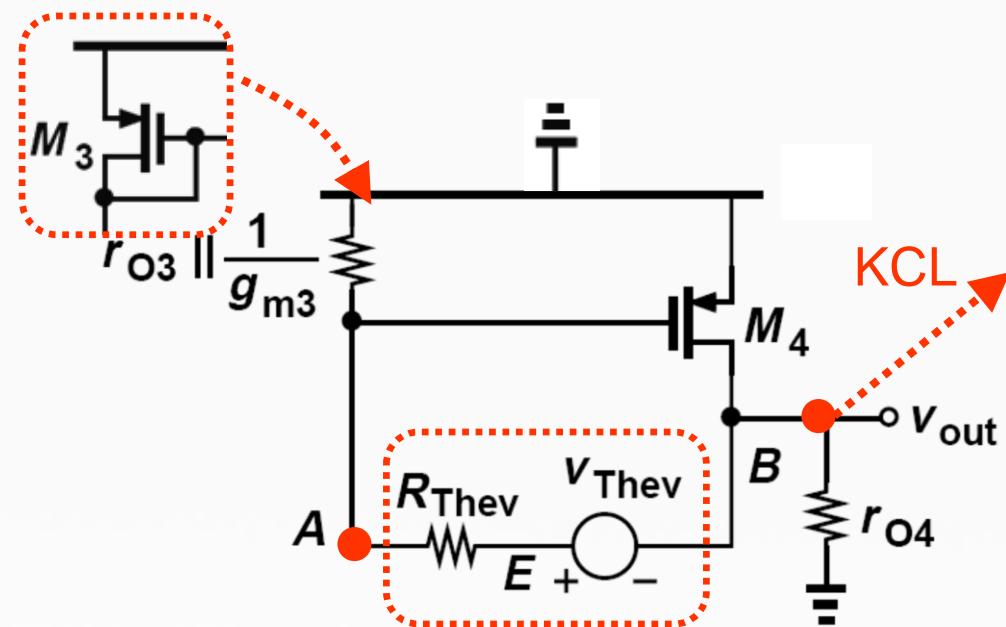
# Simplified Differential Pair with Active Load



$$\left\{ \begin{array}{l} V_{Thev} = -g_m r_{oN} (V_{in1} - V_{in2}) \\ R_{Thev} = 2r_{oN} \end{array} \right.$$

$$V_A = \frac{1/g_{m3} \parallel r_{o3}}{1/g_{m3} \parallel r_{o3} + R_{Thev}} (v_{out} + V_{Thev})$$

$$-g_{m4}(-V_A) + \frac{V_{out}}{r_{o4}} + \frac{V_{out} + V_{Thev}}{1/g_{m3} \parallel r_{o3} + R_{Thev}} = 0$$

since  $1/g_{m3} \ll r_{o3}, 1/g_{m3} \ll R_{Thev}$ ,

$$g_{m3} = g_{m4} = g_{mp}, r_{o3} = r_{o4} = r_{oP}$$

$$\frac{2}{R_{Thev}} (v_{out} + V_{Thev}) + \frac{V_{out}}{r_{oP}} = 0$$

$$V_{out} \left( \frac{1}{r_{oN}} + \frac{1}{r_{oP}} \right) = \frac{g_{mN} r_{oN} (V_{in1} - V_{in2})}{r_{oN}}$$

$$\therefore \frac{V_{out}}{V_{in1} - V_{in2}} = g_{mN} (r_{oN} \parallel r_{oP})$$

$$= g_{m1,2} (r_{o1,02} \parallel r_{o3,04})$$

