

LECTURE 13

Soo-Won Kim
swkim@korea.ac.kr

Lecture 13

16. Nyquist-Rate D/A Converters

16.2 Binary-Scaled Converters

16.3 Thermometer-Code Converters

16.4 Hybrid Converters



Current-Mode Converters

Current-mode D/A converters → **Higher-speed** applications

Resistor-based converters


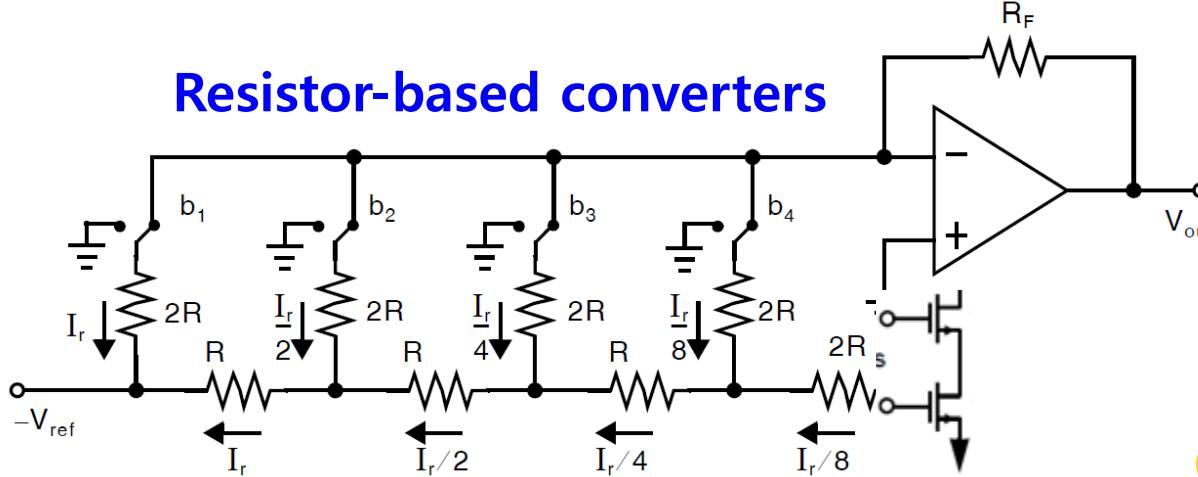


Fig. 16.10 4-bit R-2R-Based Converters

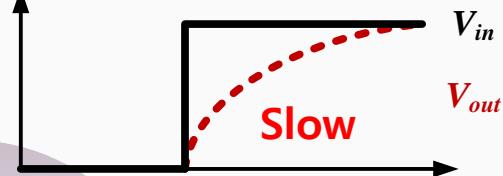

Response of resistor-based converter



Higher-speed



Glitch

Current matching

Current-mode converters


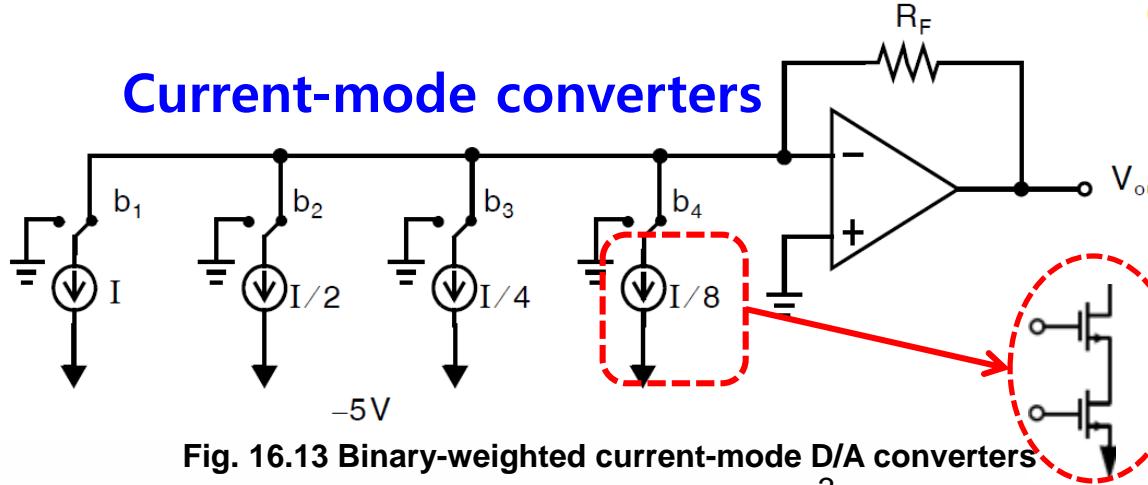


Fig. 16.13 Binary-weighted current-mode D/A converters

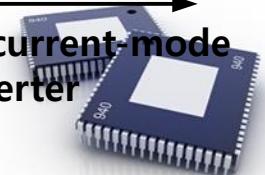

Response of current-mode converter



Glitches

Problem of current mode converters : Glitches

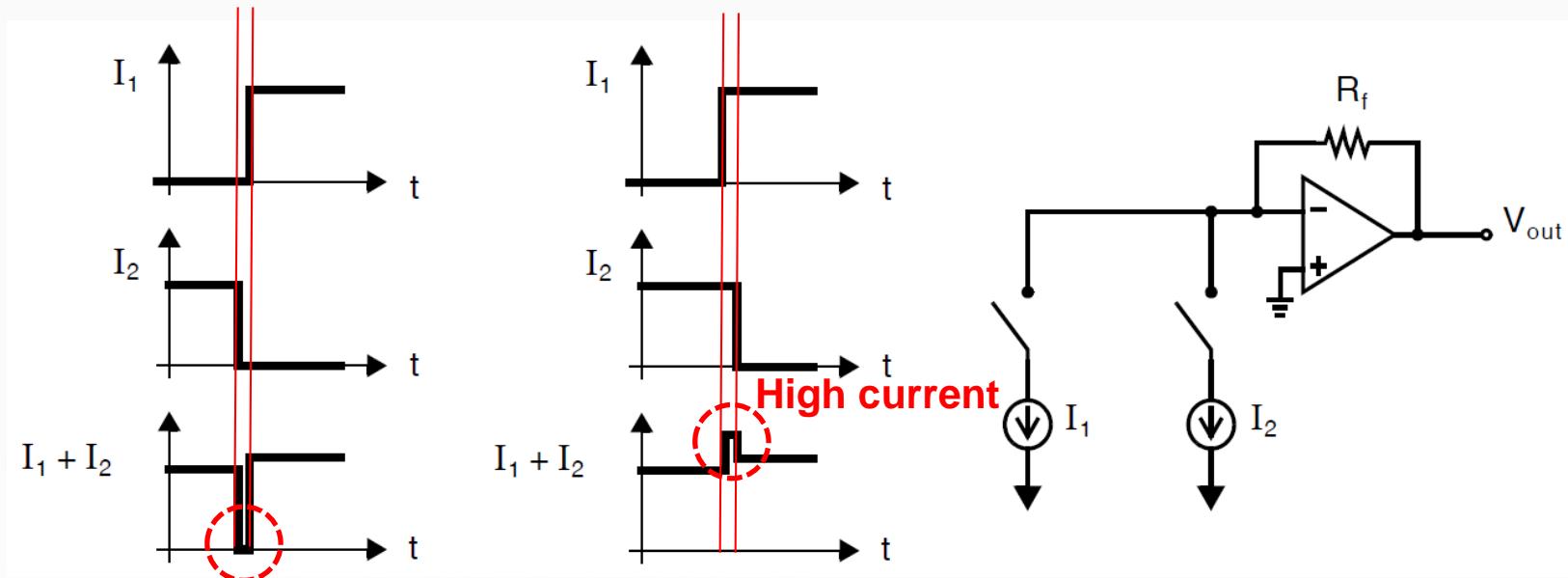


Fig. 16.14 Glitches. I_1 represents the MSB current, and I_2 represents the sum of the N-1 LSB currents

Different currents, different branch
Delays are not matched



Temporarily fall to zero or high current




Use **thermometer code** to reduce glitches




Binary code vs Thermometer code

Binary code(3bit)

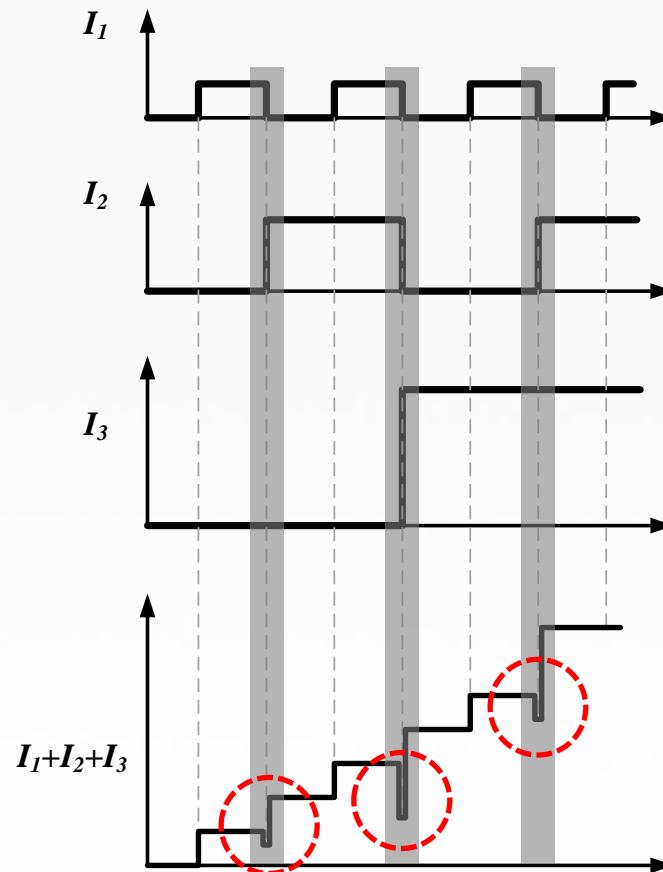

Glitch may be occurred

Thermometer code(2bit)

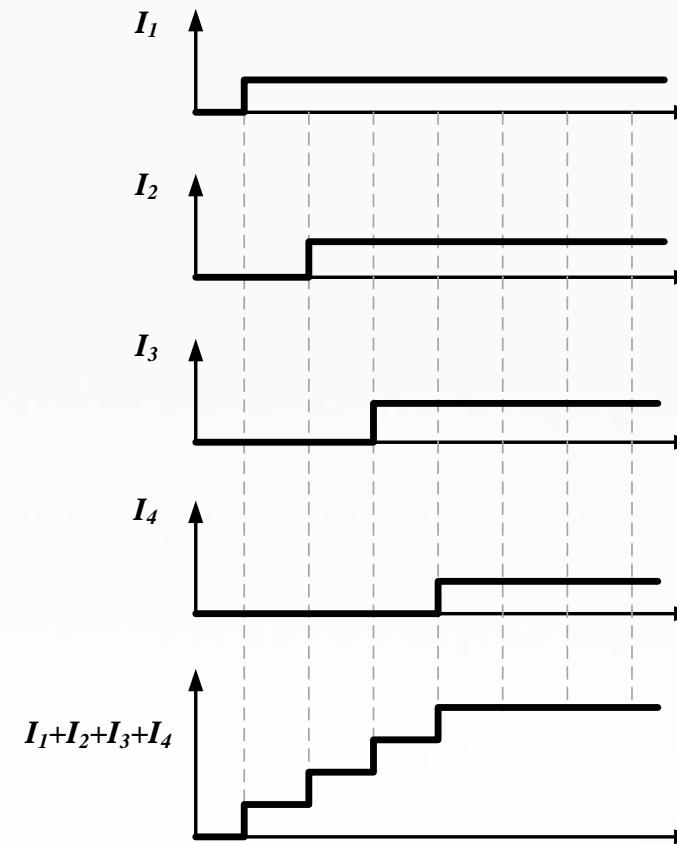

Glitch can be reduced



Thermometer-Based D/A Converters

Glitch problems → Thermometer-code

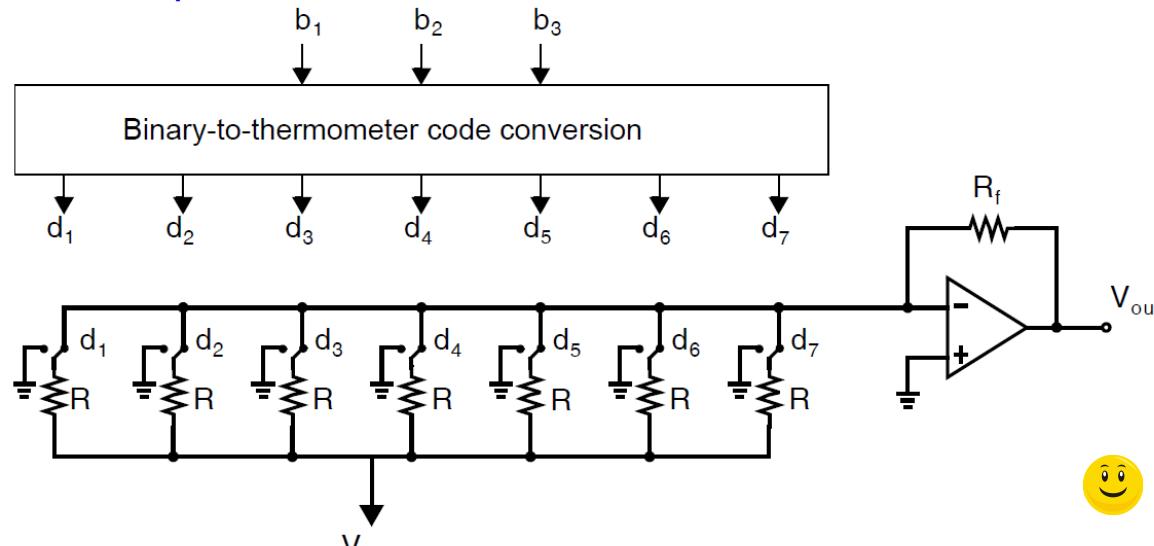


Fig. 16.15 A 3-bit thermometer-based D/A converters

Guaranteed monotonicity
Glitch ↓


:(2^{N-1} resistor

Decimal	Binary			Thermometer Code						
	b ₁	b ₂	b ₃	d ₁	d ₂	d ₃	d ₄	d ₅	d ₆	d ₇
0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1
2	0	1	0	0	0	0	0	0	1	1
3	0	1	1	0	0	0	0	1	1	1
4	1	0	0	0	0	0	1	1	1	1
5	1	0	1	0	0	1	1	1	1	1
6	1	1	0	0	1	1	1	1	1	1
7	1	1	1	1	1	1	1	1	1	1




Thermometer-Code Charge-redistribution D/A Converters

Binary-array D/A converters

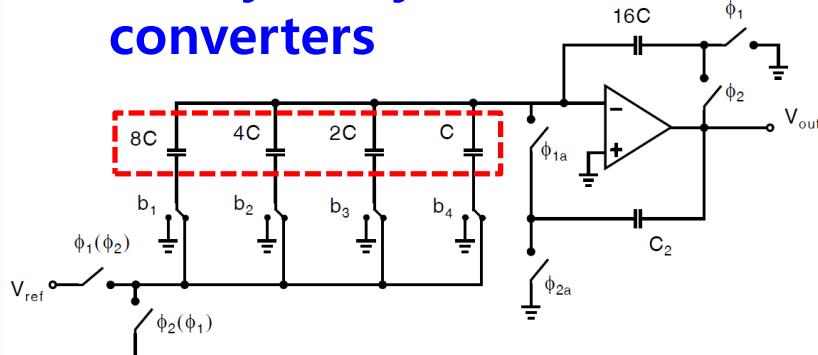

Thermometer-code D/A converters

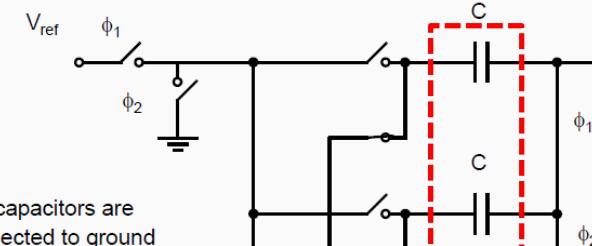


Top capacitors are connected to ground


Bottom capacitors are connected to V_{ref}

Fig. 16.12 Binary-array charge-redistribution D/A converter

at ϕ_1

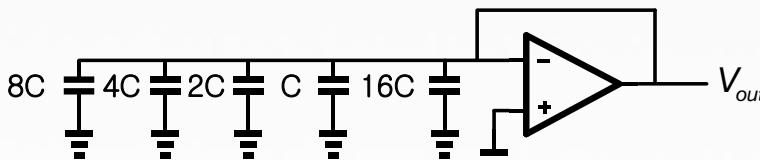

at ϕ_2 (At 1010)

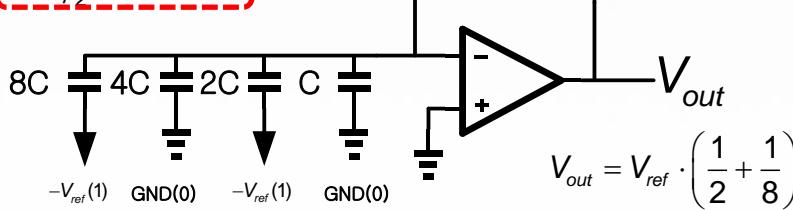

Guaranteed monotonicity Glitch ↓



2^{N-1} capacitor


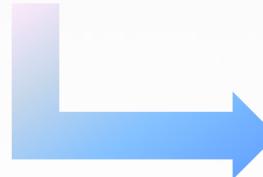


Fig. 16.16 Thermometer-code charge-redistribution D/A converters

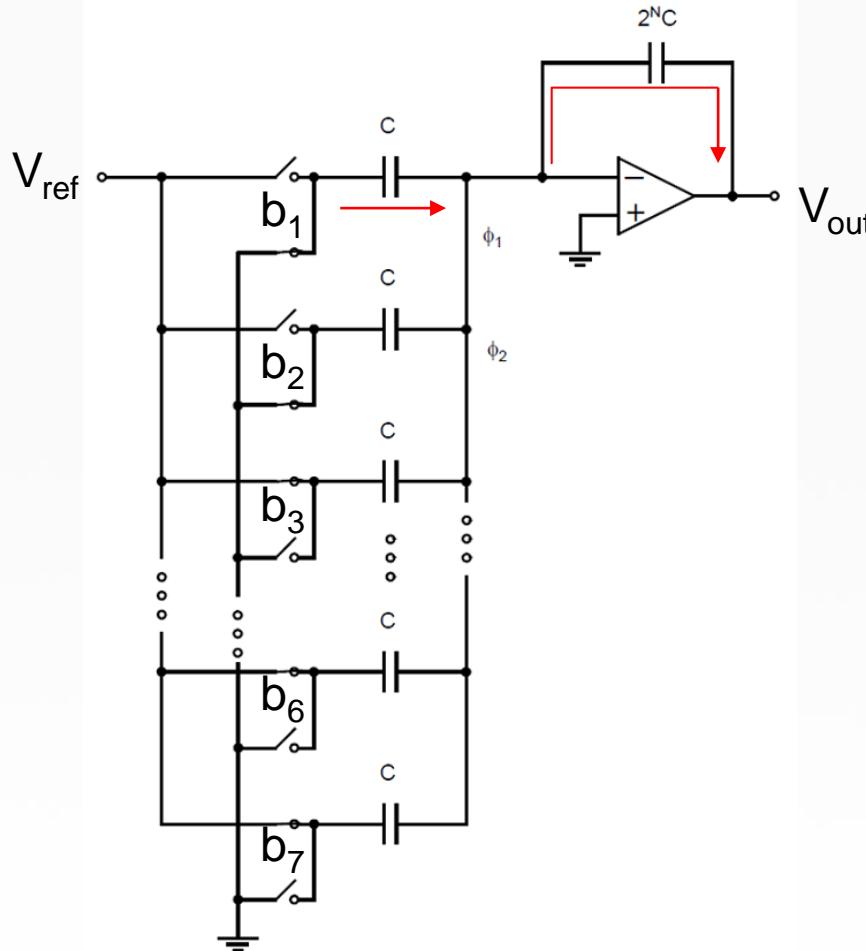Example 1

Calculate the V_{out} when $b_1b_2b_3b_4b_5b_6b_7 = 0000001, 0011111$



$$b_1b_2b_3b_4b_5b_6b_7 \Rightarrow N = 3\text{bit}$$

$$(-V_{out})2^N C = (-V_{ref})(nC)$$

$$V_{out} = \frac{nC}{2^N C} V_{ref}, \quad (n = \text{number of } 1)$$

- $b_1b_2b_3b_4b_5b_6b_7 = 0000001$

$$V_{out} = \frac{1C}{2^3 C} V_{ref} = \frac{1}{8} V_{ref}$$

- $b_1b_2b_3b_4b_5b_6b_7 = 0011111$

$$V_{out} = \frac{5C}{2^3 C} V_{ref} = \frac{5}{8} V_{ref}$$



Fig. 16.16 Thermometer-code charge-redistribution D/A converters

Thermometer-Code Current-Mode D/A Converters



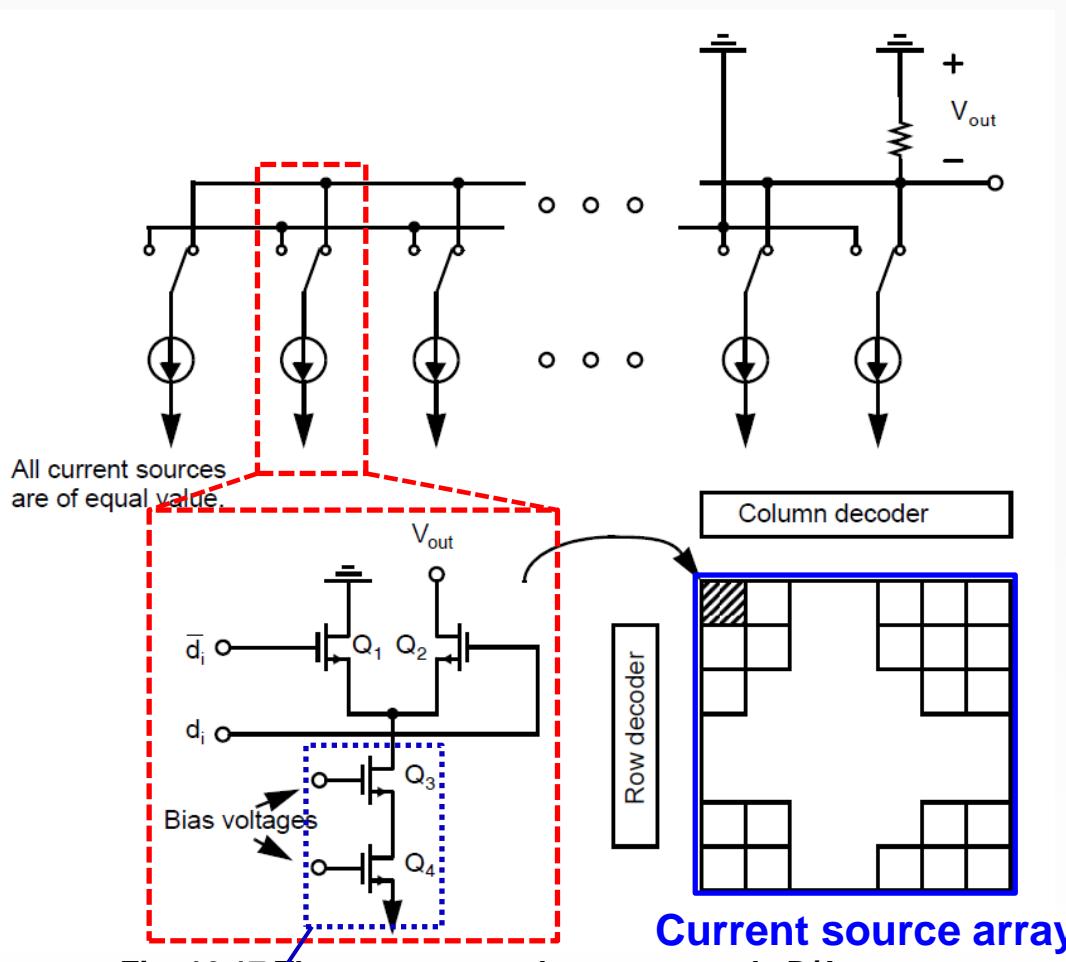


Fig. 16.17 Thermometer-code current mode D/A converter

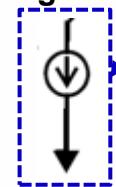


Operation

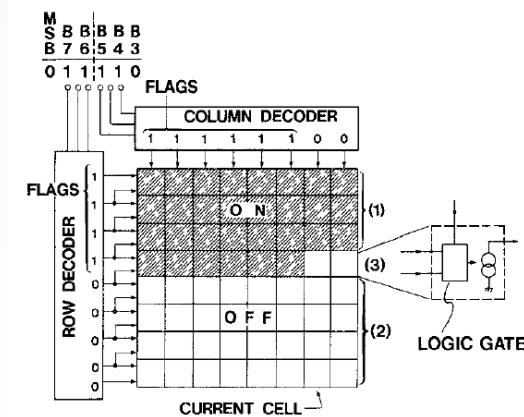- $d_i = 0$, current source = off
- $d_i = 1$, current source = on
- Row/Column
→ monotonicity, decoder area ↓



Matched Current Sources

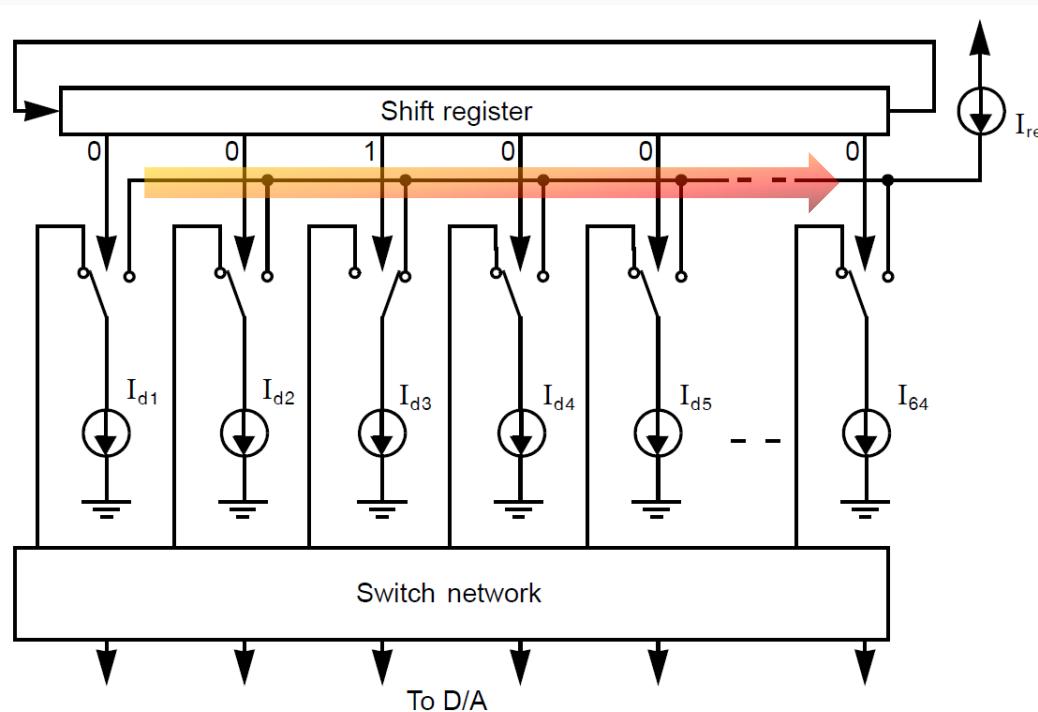Current sources should be **matched** each other → **Calibrated!**



Operation

1. Shift register shifts
2. I_{di} is connected to I_{ref}
3. I_{di} is set to I_{ref}

Fig. 16.19 Dynamically matching current sources for 6 MSB



$I_{di} = I_{ref}$ (accurately match)



Matched Current Sources

The method for calibrating and using one of the current sources

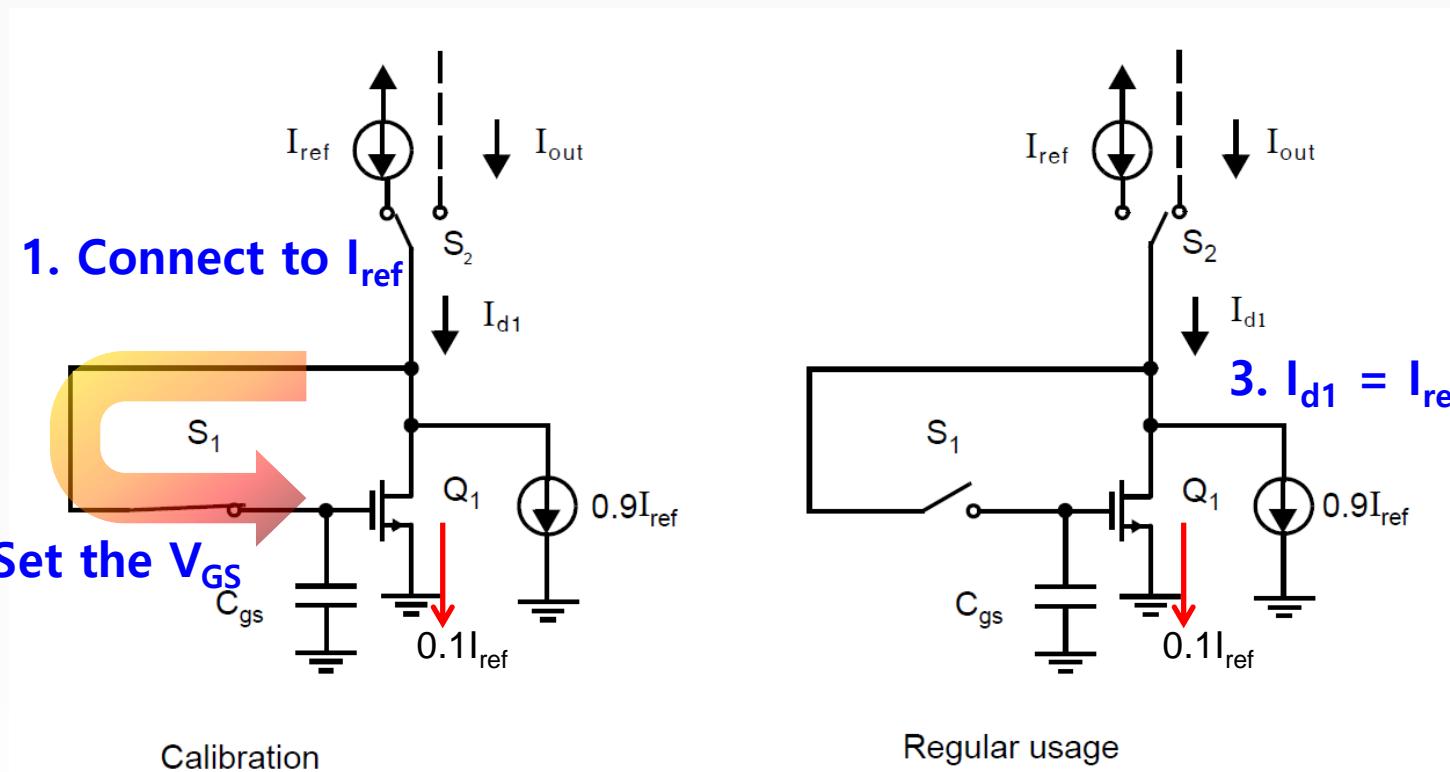


Fig. 16.20 Dynamically setting a current source, I_{d1}




Example 2

1) Find W/L for the Q₁.


Assume that $V_{GS} = 3V$ when $I_{ref} = 500\mu A$, $V_{TH} = 1V$, $\mu_n C_{ox} = 92 \mu A/V^2$.

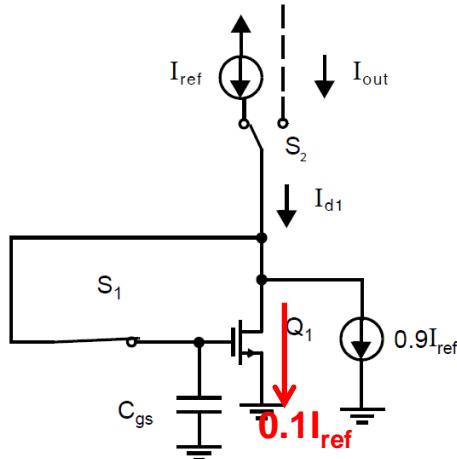2) What is the expected variation of the current?

If switch S₁ cause a random charge injection by 1mV,



Calibration

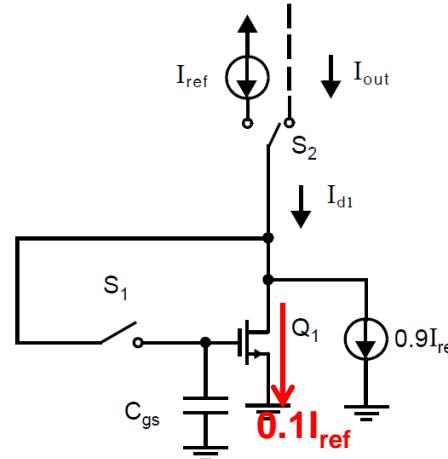

Regular usage

Fig. 16.20 Dynamically setting a current source, I_{d1}

- $W/L = 0.27$
- $V_{GS} = 3V$
- $W/L = 0.35$
- $V_{GS} = 2.76V$

Sol 1)


$$0.1 \cdot I_{ref} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$\frac{W}{L} = \frac{0.2 \cdot 500 \mu A}{92 \mu A/V^2 (3-1)^2} = 0.27$$

Sol 2)

$$I_{out} = 0.9I_{ref} + \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} \pm 1mV - V_{TH})^2$$
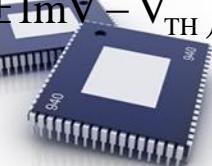
$$I_{out} = 450 \mu A + \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} \pm 1mV - V_{TH})^2 \\ = 500 \mu A \pm 0.3 \mu A$$



Example 2(Cont.)


1) Find W/L for the Q₁.

Assume that V_{GS} = 3V when I_{ref} = 500μA, V_{TH} = 1V, μ_nC_{ox} = 92 μA/V².


2) What is the expected variation of the current?

If switch S₁ cause a random charge injection by 1mV,

Without current source

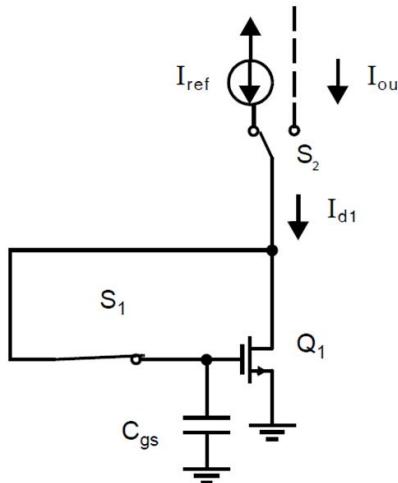

Calibration

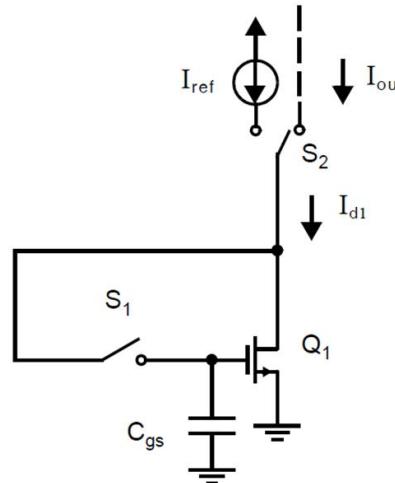

Regular usage

Fig. 16.20 Dynamically setting a current source, I_{d1}

Sol 1)

$$I_{\text{ref}} = \frac{1}{2} \mu_n C_{\text{ox}} \frac{W}{L} (V_{\text{GS}} - V_{\text{TH}})^2$$

$$\frac{W}{L} = \frac{2 \cdot 500 \mu\text{A}}{92 \mu\text{A}/\text{V}^2 (3-1)^2} = 2.7$$

Sol 2)

$$I_{\text{out}} = \frac{1}{2} \mu_n C_{\text{ox}} \frac{W}{L} (V_{\text{GS}} \pm 1\text{mV} - V_{\text{TH}})^2$$

$$= 500 \mu\text{A} \pm 3 \mu\text{A}$$

Charge injection effect ↑



Example 3

Find W/L of the M₂ . (V_{TH} = 0.7V → V_{TH} = 0.82V)

Assume that V_{GS} = 3V, (W/L)_{M1} = 15, I_{ref} = 500μA, μ_nC_{ox} = 12.6 μA/V².

Sol)

$$I_{ref} = \frac{1}{2} \cdot \mu_n C_{ox} \cdot \left(\frac{W}{L} \right) \cdot (V_{GS} - V_{TH})^2$$

$$500\mu A = \frac{1}{2} \cdot 12.6\mu A / V^2 \cdot 15 \cdot (3 - 0.7)^2$$

$$450\mu A = \frac{1}{2} \cdot 12.6\mu A / V^2 \cdot 15 \cdot (3 - 0.82)^2$$

$$50\mu A = \frac{1}{2} \cdot 12.6\mu A / V^2 \cdot \left(\frac{W}{L} \right)_{M2} \cdot (3 - 0.82)^2$$

$$\left(\frac{W}{L} \right)_{M2} = 1.67$$

