

# LECTURE 1

Soo-Won Kim  
[swkim@korea.ac.kr](mailto:swkim@korea.ac.kr)

# **1. Integrated-Circuit Devices And Modeling**

**1.1 Semiconductors and pn Junctions**

**1.2 MOS Transistors**

**1.3 Device Model Summary**


**1.4 Advanced MOS Modeling**

**1.5 SPICE-Modeling Parameters**

**1.6 Passive Devices**



# Semiconductors

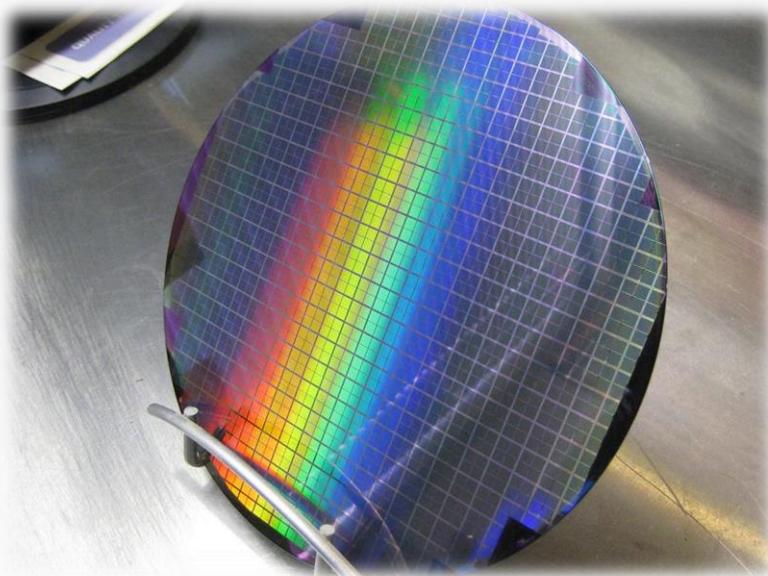

- Semiconductor = crystal lattice structure (free electrons + free holes)
- *Intrinsic* silicon has equal numbers of free electrons and holes
- Intrinsic carrier concentration,  $n_i = 1.1 \times 10^{16}$  carriers/cm<sup>3</sup>





# History of Semiconductors

- Incandescent lamp(백열등) : By Edison (1879.10.21)
- Vacuum Tube(진공관) : By John Ambrose Fleming(1904)
  - Ex) ENIAC: First computer
    - Consists of 17,468 Vacuum Tube + other devices




## Size, power, stability issue

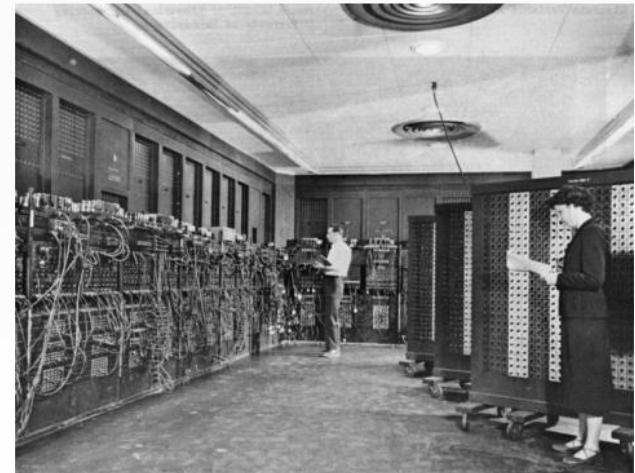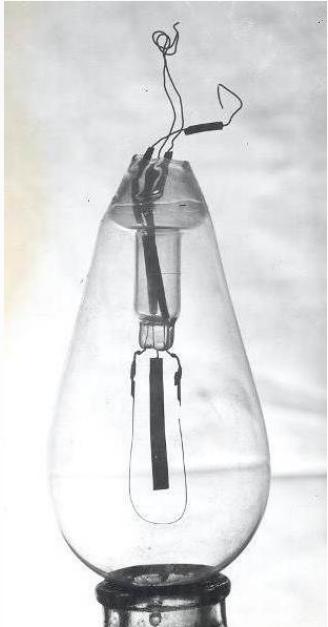

# History of Semiconductors

- World war II: 1939.9 ~ 1945.8

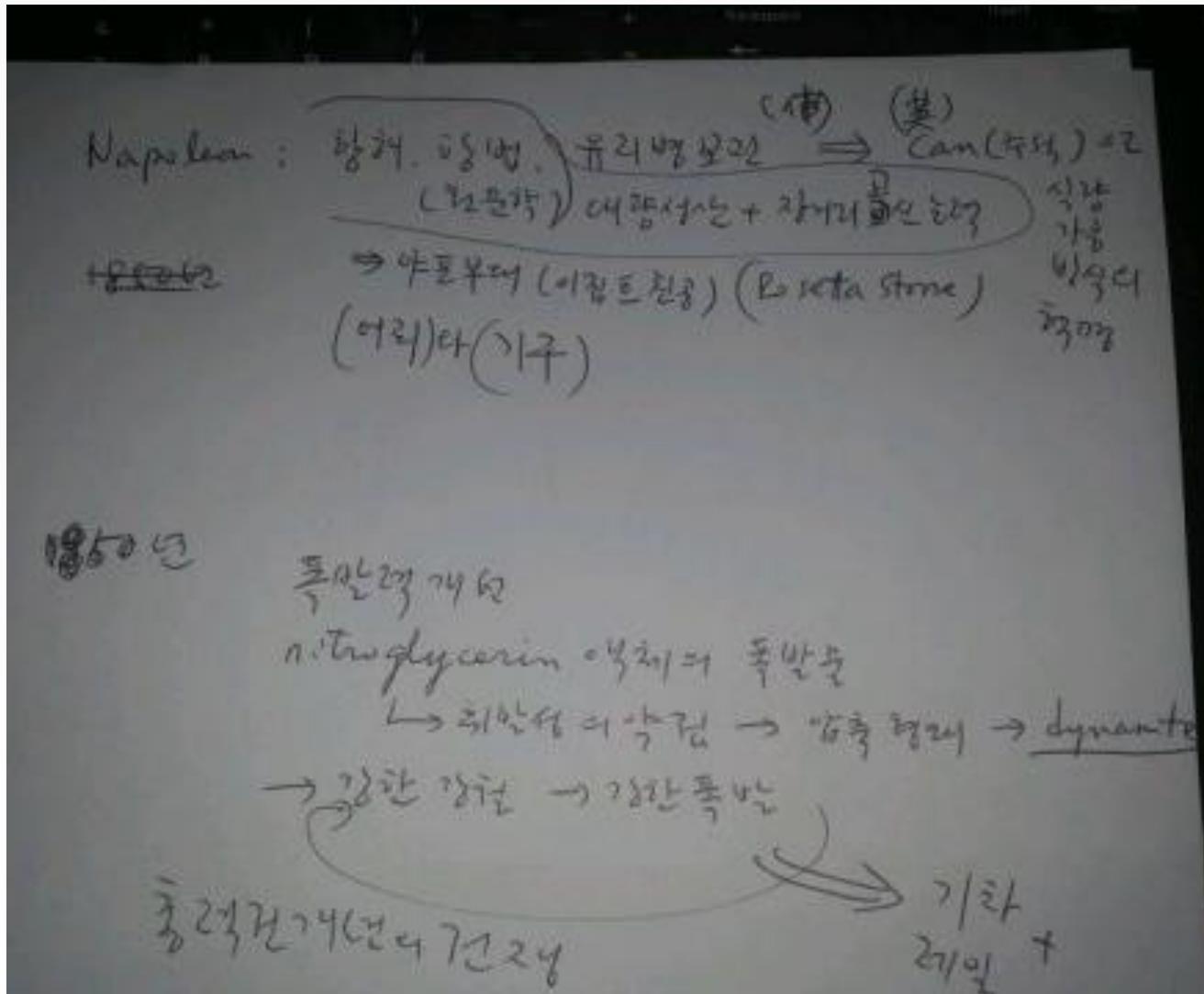

# History of Semiconductors

1900 Haber  
화학 : 흑금강은 나트륨과 반응하는 히드록시아이온을 비롯한 다양한 화합물을 발견  
결산나트륨의 발견자이며  
 $\Rightarrow$  노벨상을 (어려움) 공유  $\Rightarrow$  Nobel

1914년 질식수소는 폭발물의 원인  
Haber 수소를 태우기로

1915년 Phosgene (포스기네) 발견  $\Rightarrow$  Mask

Albert Einstein 이론 :  
전기장에 미치는 전기장의 특성


전쟁 - 무기 - 과학 - 인류 (3/10)



# History of Semiconductors

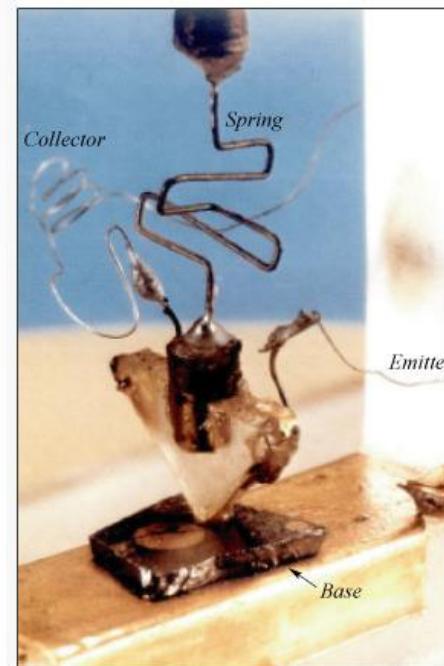
## ■ Transistor

- In 1947: The first point contact transistor was developed
    - ✓ John Bardeen and Walter Brattain in Bell Lab.)
  - In 1956: The Nobel Prize winner
    - ✓ William Shockley was included


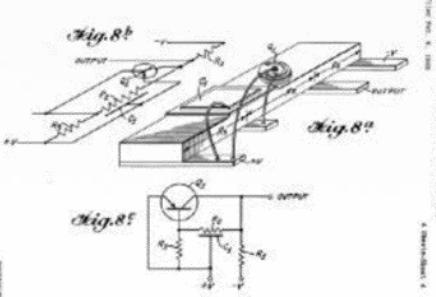
# History of Semiconductors


- In 1958: The first IC was invented
  - By Jack Kilby of Texas Instruments
    - ✓ The Nobel Prize winner in 2000




# History of Semiconductors




1962 Fairchild IC

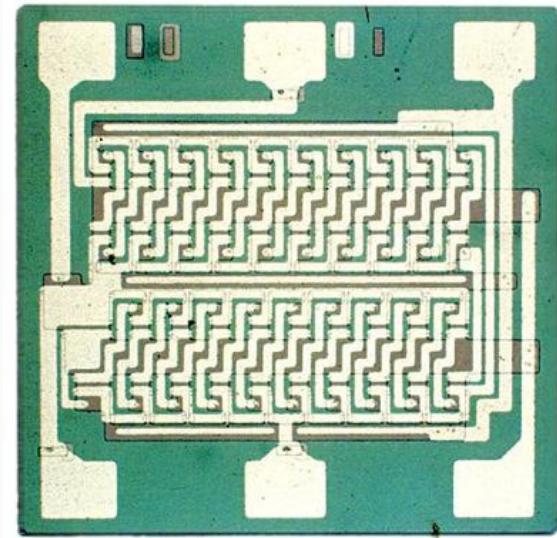

1964 First MOS IC

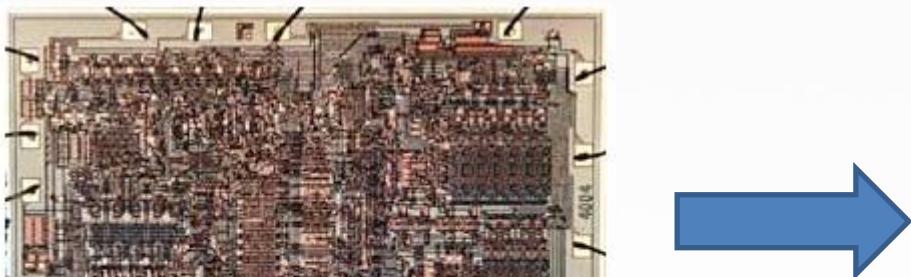

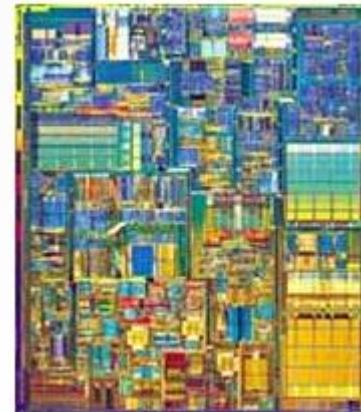1971 Intel 4004 microprocessor  
(2,300 transistors, 144mm<sup>2</sup>)



2011 Intel i7  
(560,000,000 transistors, 296mm<sup>2</sup>)



# Diodes (=PN junction)

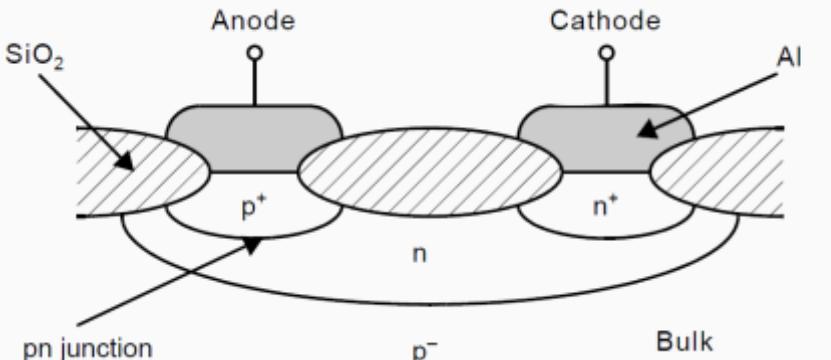


Fig. 1.1 A cross section of a pn diode

- **Anode** : p-type, **Cathode** : n-type
- **Depletion region**
  1. Diffusion of free carriers of p side & n side
  2. It extends farther into the more lightly doped side
- **Built-in voltage** = potential difference between the n and p side

$$\Phi_0 = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right) \quad (1.6)$$



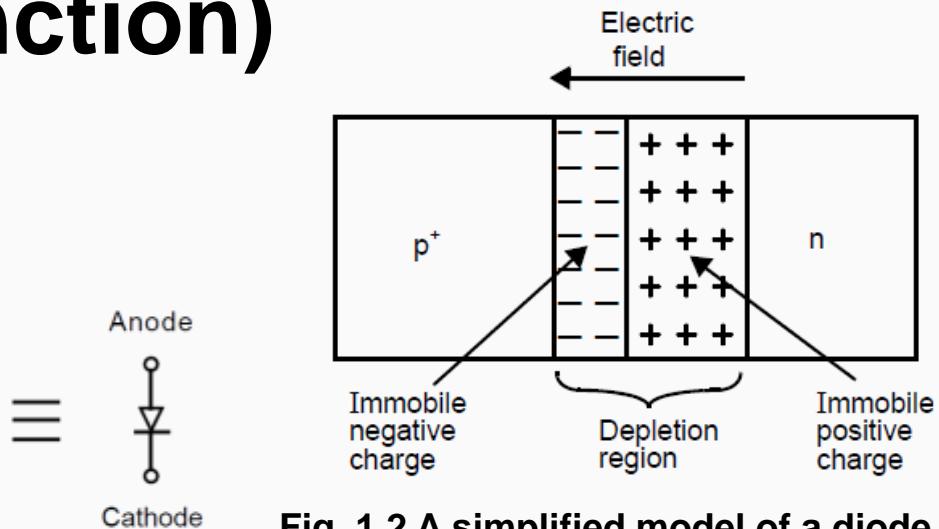


Fig. 1.2 A simplified model of a diode

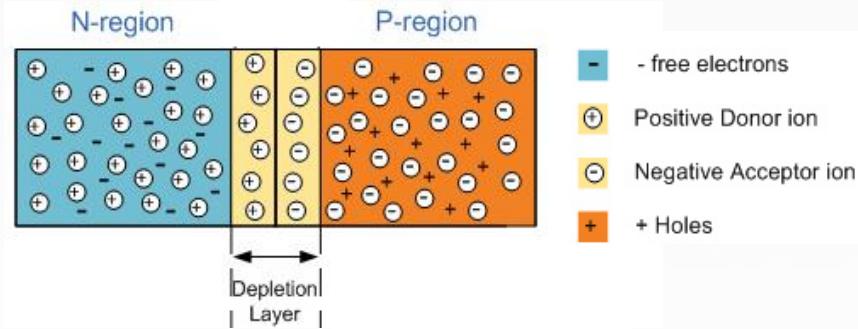

# Diodes (=PN junction)


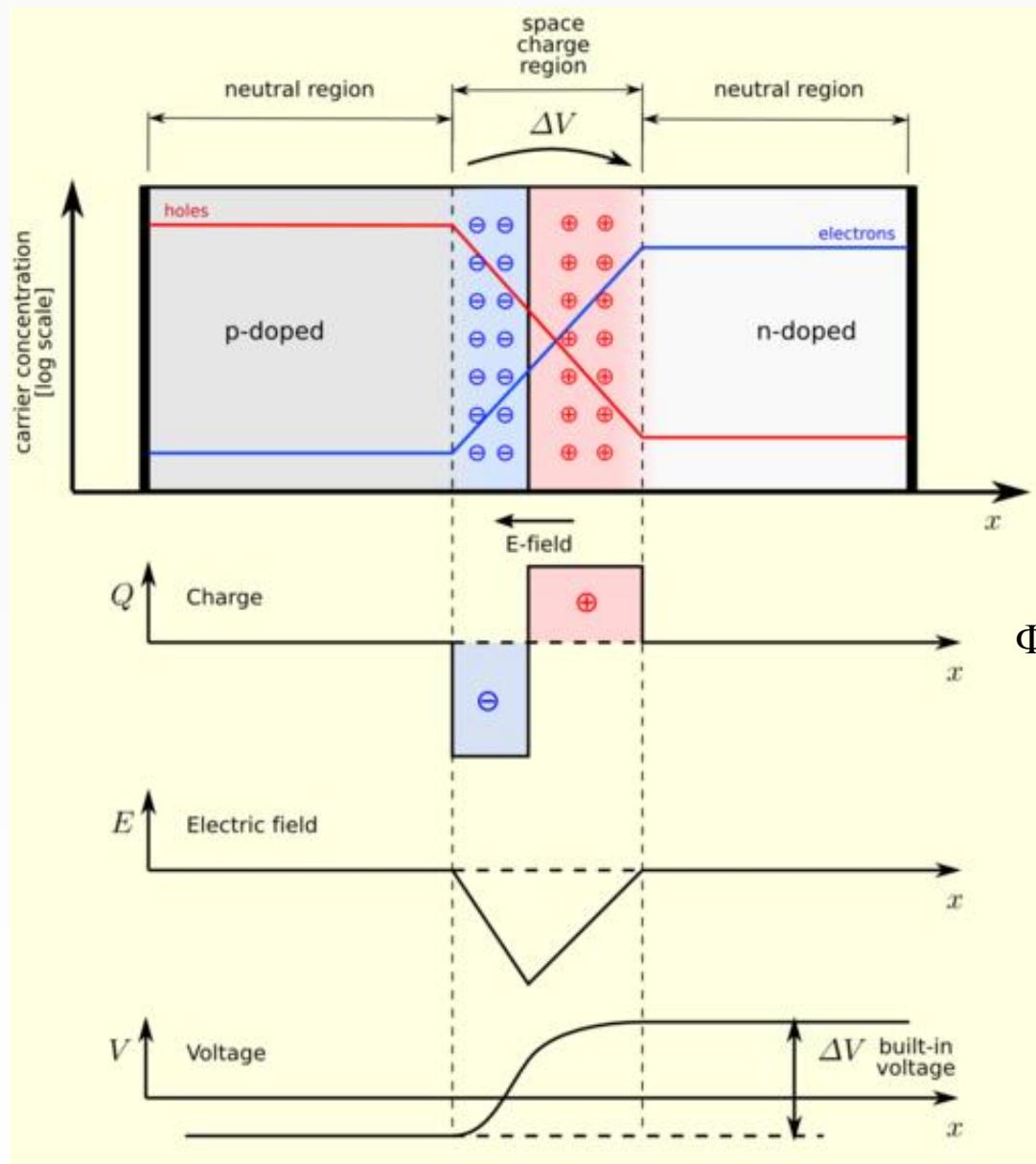


$$\Phi_0 = V_T \ln \left( \frac{N_A N_D}{n_i^2} \right) \quad (1.6)$$



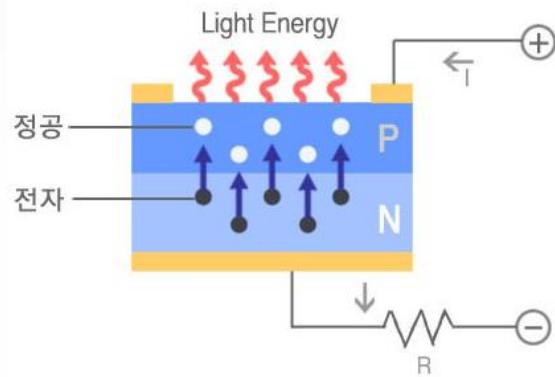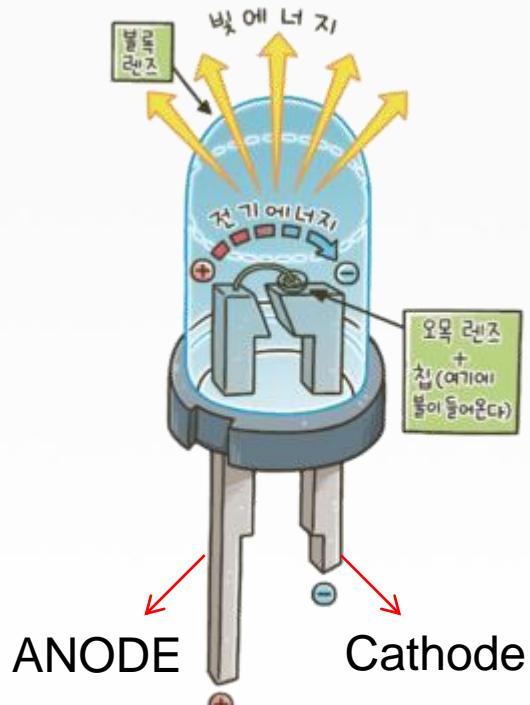
# Diode's Application: LED

- PN junction은 실리콘만 사용하지 않고 다른 물질을 사용하여 다양한 용도로 사용이 가능하다.
- LED(Light Emitting Diode) : 다이오드를 이용하여 순방향 전류가 흐르는 경우 전기 에너지를 빛 에너지로 변환하는 소자!



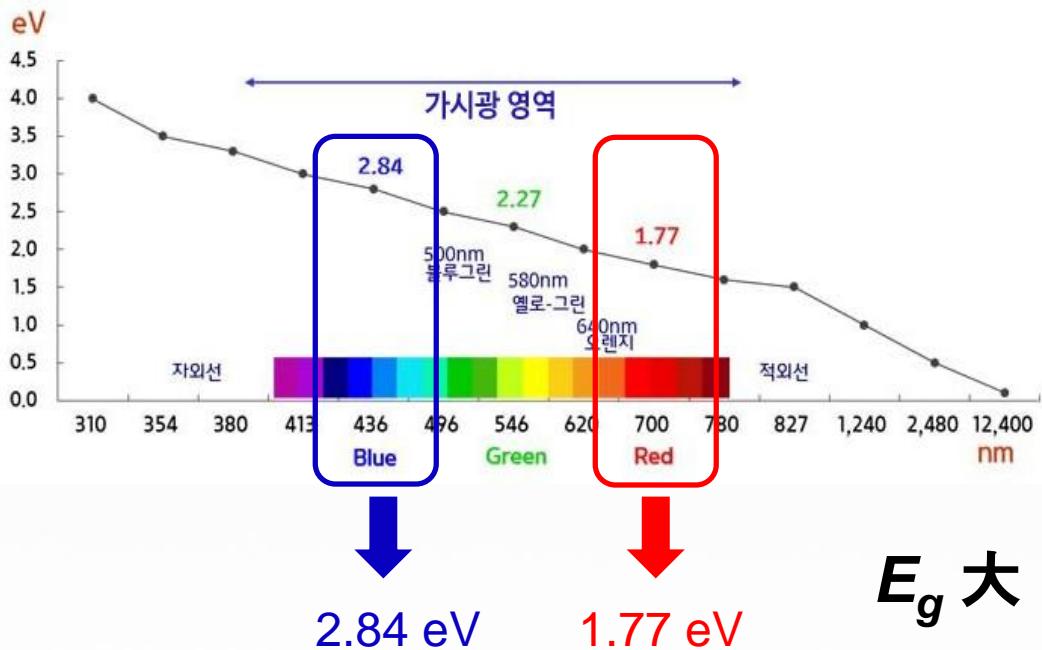
# Diode's Application: LED

- 실리콘이 아닌 3-5족 반도체 다이오드의 경우  
Lighting energy(eV)로 발산(발광) 한다.



$E_g$  大

Color	Wavelength [nm]	Semiconductor material
Infrared	$\lambda > 760$	Gallium arsenide (GaAs) Aluminium gallium arsenide (AlGaAs)
Red	$610 < \lambda < 760$	Aluminium gallium arsenide (AlGaAs) Gallium arsenide phosphide (GaAsP) Aluminium gallium indium phosphide (AlGaNp) Gallium(III) phosphide (GaP)
Orange	$590 < \lambda < 610$	Gallium arsenide phosphide (GaAsP) Aluminium gallium indium phosphide (AlGaNp) Gallium(III) phosphide (GaP)
Yellow	$570 < \lambda < 590$	Gallium arsenide phosphide (GaAsP) Aluminium gallium indium phosphide (AlGaNp) Gallium(III) phosphide (GaP)
Green	$500 < \lambda < 570$	<b>Traditional green:</b> Gallium(III) phosphide (GaP) Aluminium gallium indium phosphide (AlGaNp) Aluminium gallium phosphide (AlGaP) <b>Pure green:</b> Indium gallium nitride (InGaN) / Gallium(III) nitride (GaN)
Blue	$450 < \lambda < 500$	Zinc selenide (ZnSe) Indium gallium nitride (InGaN) Silicon carbide (SiC) as substrate Silicon (Si) as substrate—under development
Violet	$400 < \lambda < 450$	Indium gallium nitride (InGaN)
Purple	multiple types	Dual blue/red LEDs, blue with red phosphor, or white with purple plastic
Ultraviolet	$\lambda < 400$	Diamond (235 nm) Boron nitride (215 nm) Aluminium nitride (AlN) (210 nm) Aluminium gallium nitride (AlGaN) Aluminium gallium indium nitride (AlGaN) — down to 210 nm
Pink	multiple types	Blue with one or two phosphor layers: yellow with red, orange or pink phosphor added afterwards, or white with pink pigment or dye.
White	Broad spectrum	Blue/UV diode with yellow phosphor

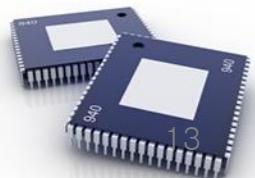

# MOS Transistors

- Diode →
  - Bipolar Transistor
  - MOS(Metal-Oxide Semiconductor) Transistor

CMOS circuit (*Complementary MOS*): contains n-type and p-type transistor

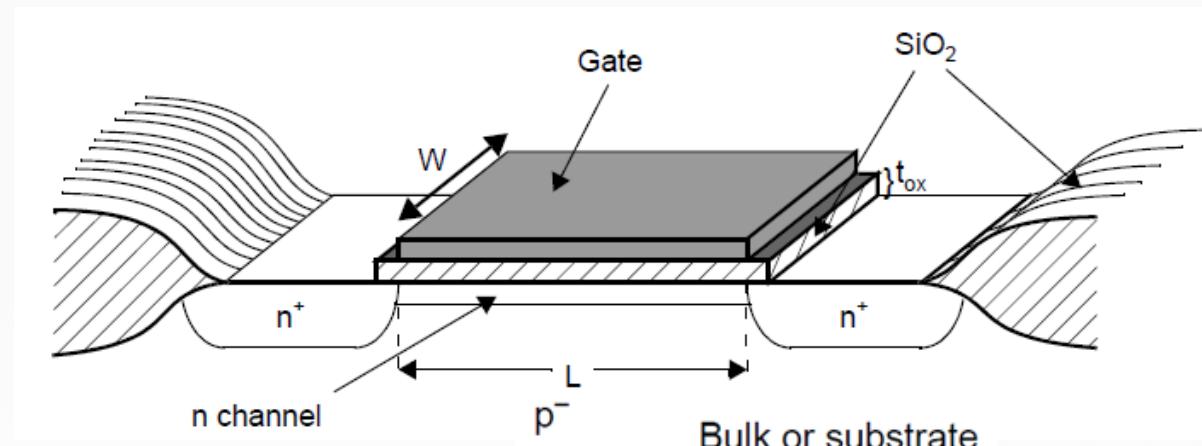


Fig. 1.10 The important dimensions of a MOS transistor

- The used MOS technologies in the Lab, the minimum channel length is about  $0.35\mu\text{m}$  and  $0.18\mu\text{m}$
- *p substrate* is connected to the most **negative** voltage (**NMOS**)
- *n well* is connected to the most **positive** voltage (**PMOS**)



# Symbols for MOS transistors

- MOS transistor are actually four-terminal devices

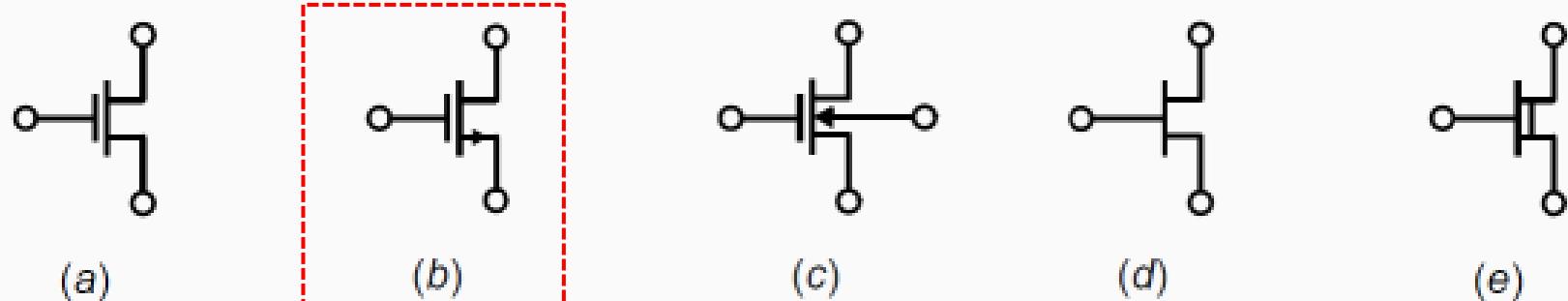


Fig. 1.7 Commonly used symbols for n-channel transistors

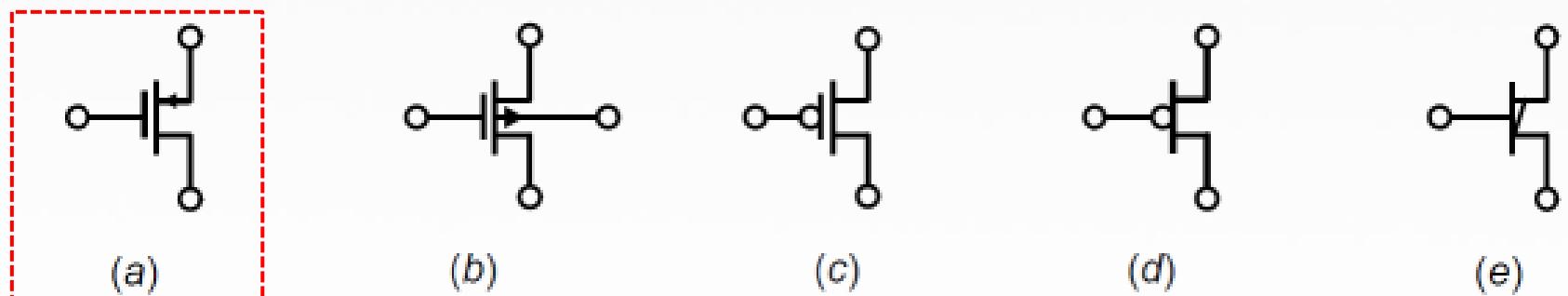


Fig. 1.8 Commonly used symbols for p-channel transistors



# **3. Basic Current Mirrors and Single-Stage Amplifiers**

**3.1 Simple CMOS Current Mirrors**

**3.2 Common-Source Amplifier**

**3.3 Source-Follower or Common-Drain Amplifier**

**3.4 Common-Gate Amplifier**

**3.5 Source-Degenerated Current Mirrors**


**3.6 Cascode Current Mirrors**

**3.7 Cascode Gain Stage**

**3.8 MOS Differential Pair and Gain Stage**





# Amplifier

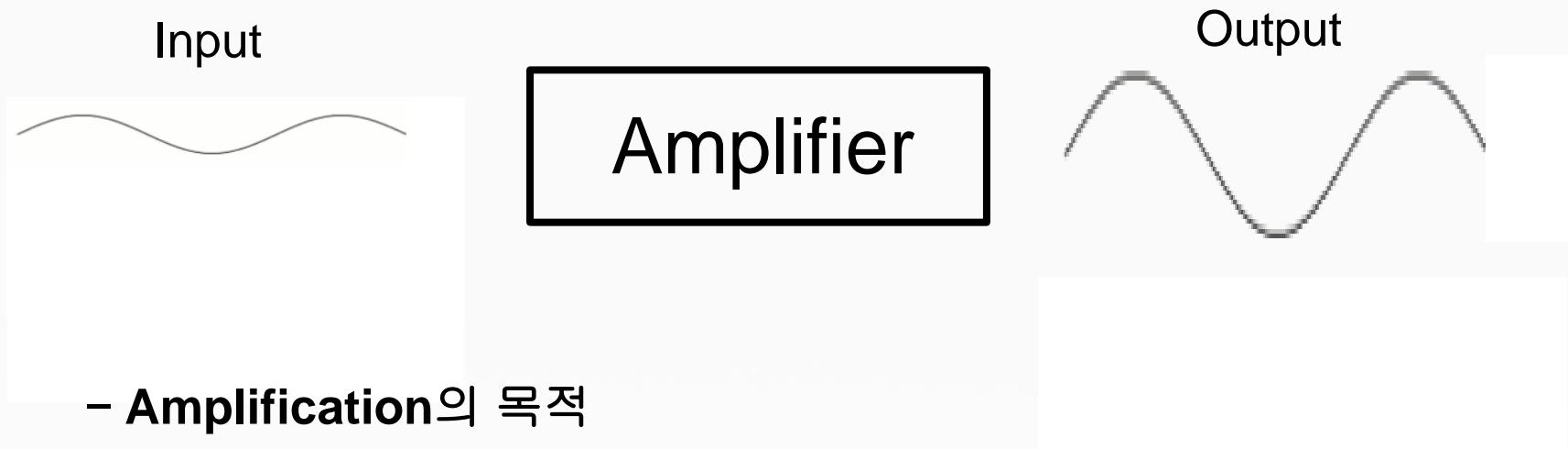

## – **Amplification**의 목적

- ✓ 부하를 구동시킬 만큼의 큰 신호를 만들기 위해
- ✓ 다음 단 회로 블록의 Noise를 무시할 만큼의 큰 신호를 만들기 위해
- ✓ 디지털회로에서 논리레벨을 제공하기 위해

# Common source stage

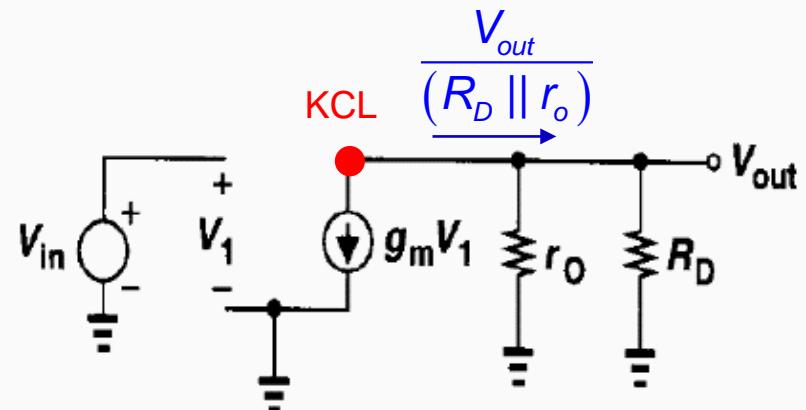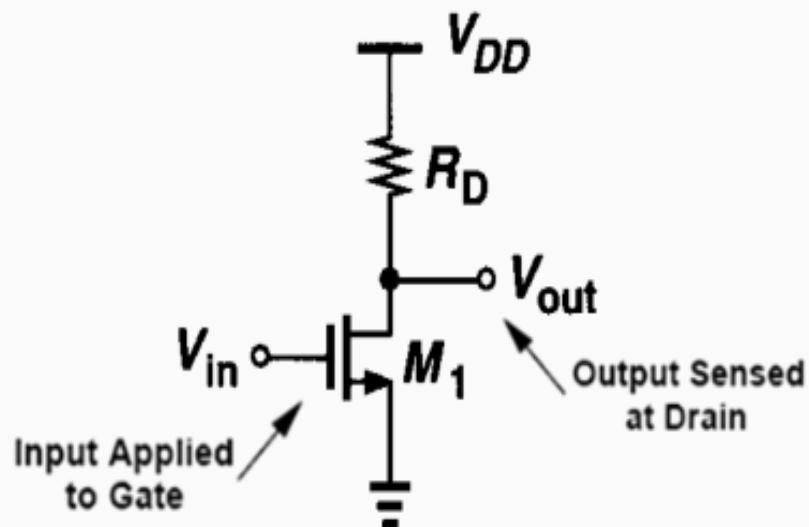

$$\frac{V_{out}}{V_{in}} = -g_m (R_D \parallel r_o)$$

Since  $g_m = \sqrt{2\mu_n C_{ox} (W/L) I_D}$ ,


$$\rightarrow A_v = -g_m (R_D \parallel r_o) = -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} (R_D \parallel r_o)$$

For M1 to remain in saturation,  $V_{GS} < V_{DS} + V_{TH}$

$$\rightarrow V_{GS} < V_{DD} - R_D I_D + V_{TH}$$





# Common-gate stage


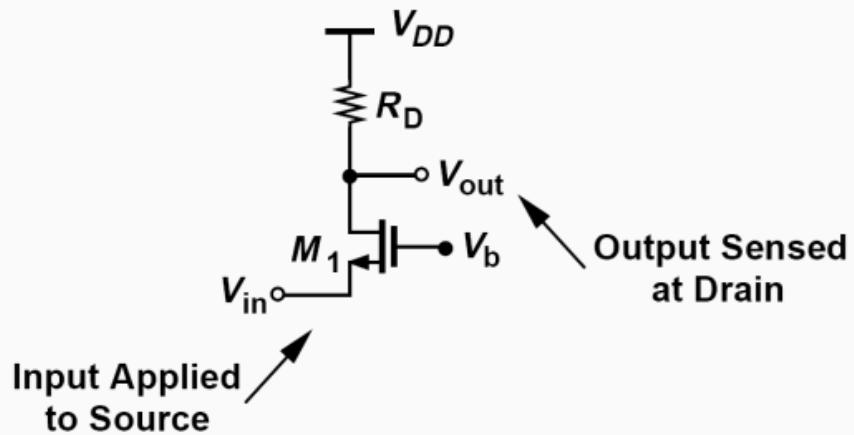


$$A_v \approx g_m R_D \quad (\lambda = 0)$$

- Trade-off : Voltage headroom and gain.

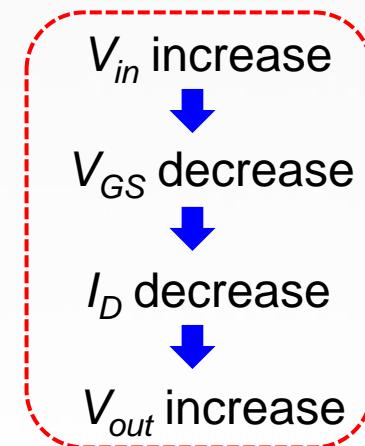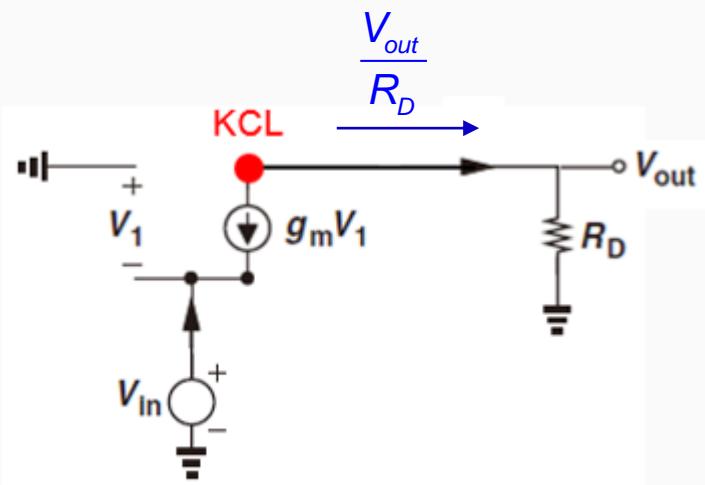

# Source follower stage

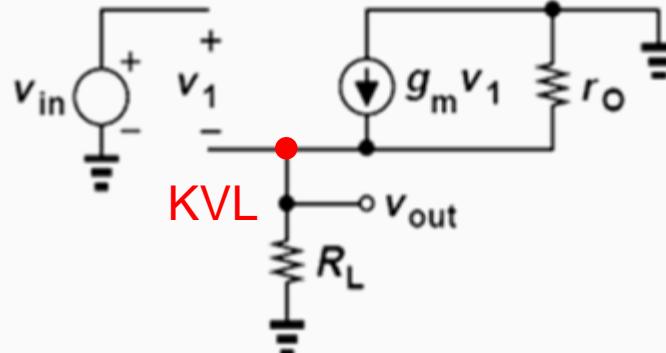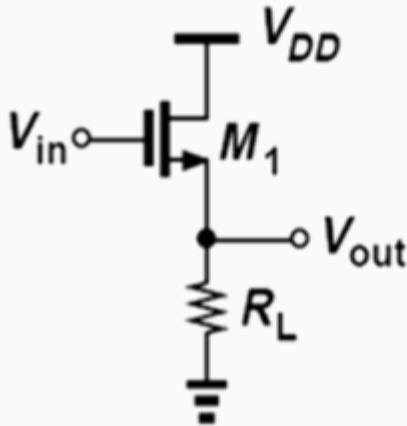

$$\left. \begin{array}{l} g_m v_1 (r_o \| R_L) = v_{out} \\ v_{in} = v_1 + v_{out} \end{array} \right\} \frac{v_{out}}{v_{in}} = \frac{g_m (r_o \| R_L)}{1 + g_m (r_o \| R_L)}$$

$$= \frac{r_o \| R_L}{\frac{1}{g_m} + (r_o \| R_L)}$$


The voltage gain is **positive** and **less than unity**

$$\lambda = 0 \rightarrow = \frac{R_L}{R_L + \frac{1}{g_m}}$$


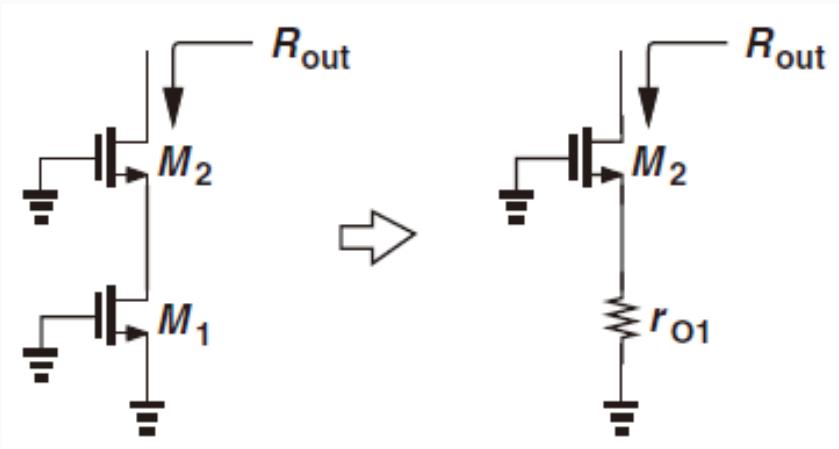
# MOS Cascodes


- Gain( $A_v \approx g_m R_{out}$ )을 증가시키기 위해서  $R_{out}$ 을 증가시킨다.



$$R_{out} = (1 + g_{m2} r_{O2}) r_{O1} + r_{O2}$$

$$\approx g_{m2} r_{O1} r_{O2},$$

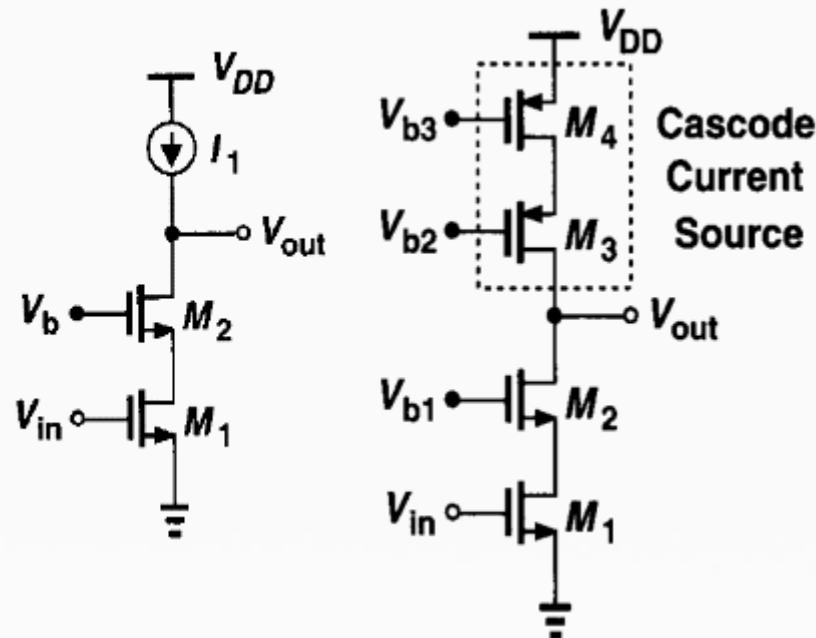where it is assumed  $g_m r_{O1} r_{O2} \gg r_{O1}, r_{O2}$







$$R_{on} = \{ [1 + (g_{m2} + g_{mb2}) r_{O2}] r_{O1} + r_{O2} \}$$

$$R_{op} = \{ [1 + (g_{m3} + g_{mb3}) r_{O3}] r_{O4} + r_{O3} \}$$

$$A_v \approx -g_{m1} [(g_{m2} r_{O2} r_{O1}) \parallel (g_{m3} r_{O3} r_{O4})]$$



# Single stage Amplifiers

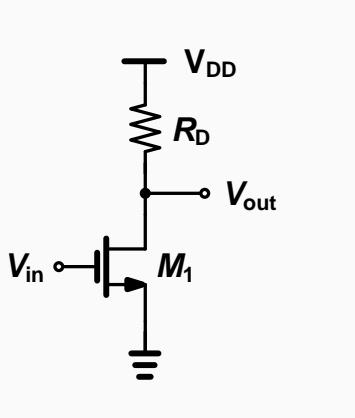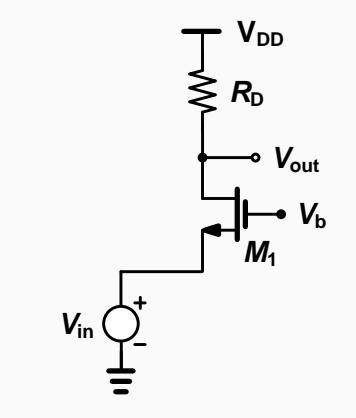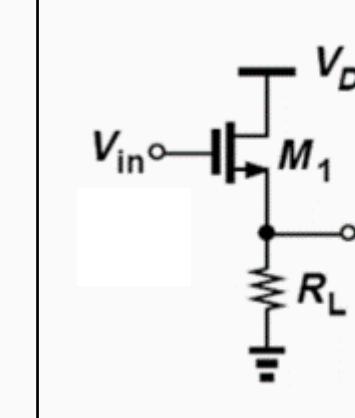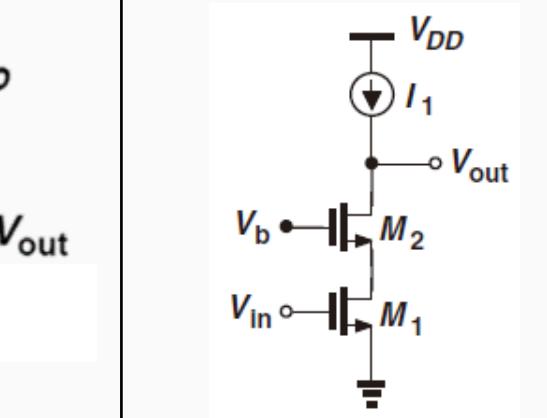			
Common Source	Common Gate	Source Follower	Cascode
$- g_m R_D (\lambda = 0)$	$g_m R_D (\lambda = 0)$	$\frac{R_L}{R_L + \frac{1}{g_m}}$	$g_{m1} g_{m2} r_{o1} r_{o2}$
<ul style="list-style-type: none"> <li>Inverted gain</li> <li>High <math>R_{in}</math>, High <math>R_{out}</math></li> </ul>	<ul style="list-style-type: none"> <li>Non-inverted gain</li> <li>Low <math>R_{in}</math>, High <math>R_{out}</math></li> </ul>	<ul style="list-style-type: none"> <li>Gain is lower than 1</li> <li>High <math>R_{in}</math>, Low <math>R_{out}</math></li> <li>Voltage buffer, Voltage level shifter</li> </ul>	<ul style="list-style-type: none"> <li>Higher gain</li> <li>High <math>R_{in}</math>, Higher <math>R_{out}</math></li> <li>Voltage swing is degraded</li> </ul>

