

LECTURE 10

Soo-Won Kim
swkim@korea.ac.kr

11. Sample-and Hold and Translinear Circuit

11.1 Performance of sample-and-hold circuits


11.2 MOS sample-and-hold basic

11.3 Examples of CMOS S/H circuits




Sample-and-hold circuit




Analog to digital converter

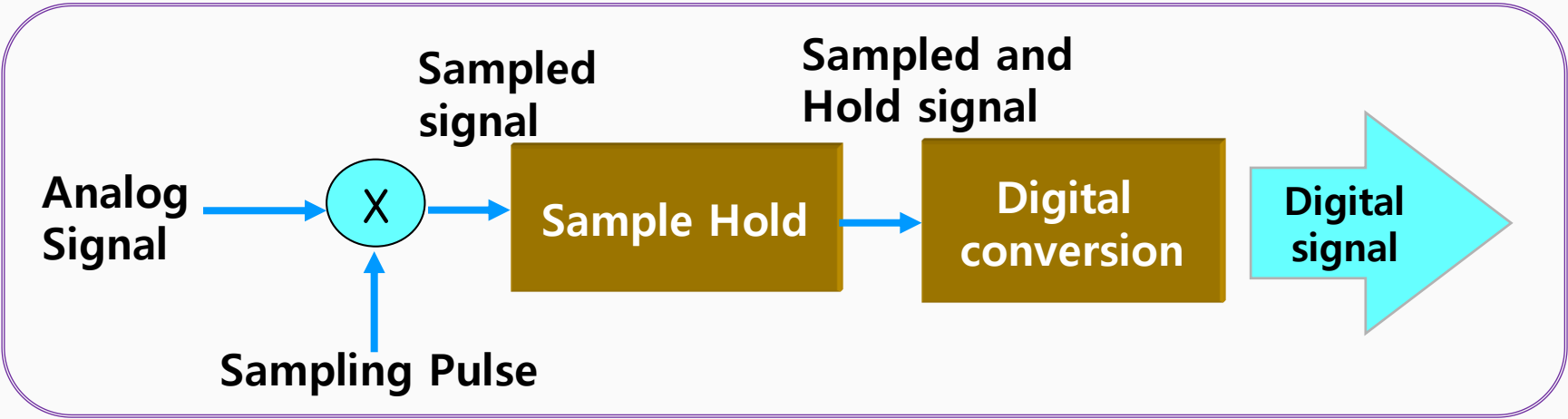


(1) Analog signal

 

(2) Sampled and Hold signal

 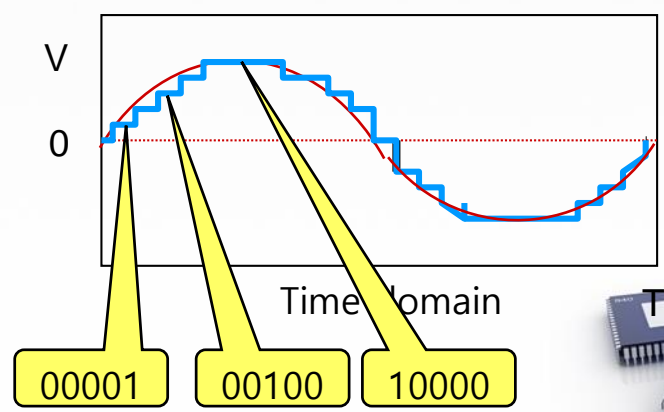 

MOS sample-and-hold basics

 

❖ Operation


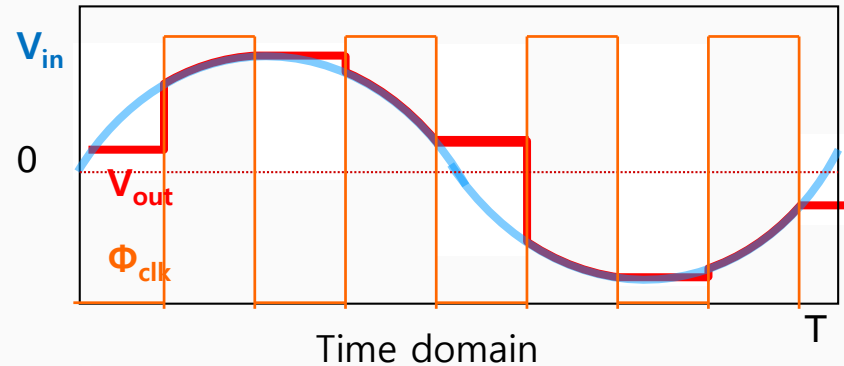


Fig. 11.3 An open-loop track and hold realized using MOS technology

- When Φ_{clk} is closed $\Rightarrow V_{out}$ samples V_{in}
- When Φ_{clk} is opened $\Rightarrow V_{out}$ holds(keep value)

❖ Problem


- 1) Charge injection($\Delta V'$) $\Rightarrow \Delta V' = \frac{\Delta Q_{C-hld}}{C_{hld}} = -\frac{C_{ox}WL(V_{DD} - V_{tn} - V_{in})}{2C_{hld}} \quad (11.3)$
- 2) Low input impedance(lower than Amp)

 

 Example 11.1

Find the hold step for V_{in} equal to 1 V, 0.5V and 0.05V.
 Estimate the average dc offset

$$C_{hld} = 1pF, C_{ox} = 8.5 fF / (\mu m)^2, V_m = 0.45V, (W/L)_1 = (5/0.4), V_{DD} = 2V$$



Using (11.3)

$$\Delta V' = \frac{\Delta Q_{C-hld}}{C_{hld}} = -\frac{C_{ox}WL(V_{DD} - V_m - V_{in})}{2C_{hld}} \quad (11.3)$$

$$\Rightarrow \Delta V' (1V) = -\frac{8.5 f \cdot 5 \cdot 0.4 (2 - 0.45 - 1)}{2p} = -4.7mV$$

$$\Rightarrow \Delta V' (0.5V) = -\frac{8.5 f \cdot 5 \cdot 0.4 (2 - 0.45 - 0.5)}{2p} = -8.9mV$$

$$\Rightarrow \Delta V' (0.05V) = -\frac{8.5 f \cdot 5 \cdot 0.4 (2 - 0.45 - 0.05)}{2p} = -12.75mV$$

Fig. 11.3 An open-loop track and hold realized using MOS technology

Average dc offset $V_{offset-avg} = \frac{\Delta V' (1V) + \Delta V' (0.5V) + \Delta V' (0.05V)}{3} = -8.78mV$

$\Rightarrow V_{in} \downarrow \rightarrow \Delta V' \text{ (charge injection voltage)} \uparrow$



Reduced charge injection

❖ Problem

1) Charge injection

 


Fig. 11.4 An open-loop track and hold realized using a CMOS transmission gate

By transmission gate

😊 Reduced the charge injection

😞 Difficult to make up p and n transistors match
 Difficult to make clocks fast enough

 


Fig. 11.3 An open-loop track and hold realized using an n-channel switch a long with a dummy switch

By Dummy switch

😊 Reduced the charge injection

😞 Difficult to make clocks fast enough



High input impedance

❖ Problem

2) Low input impedance

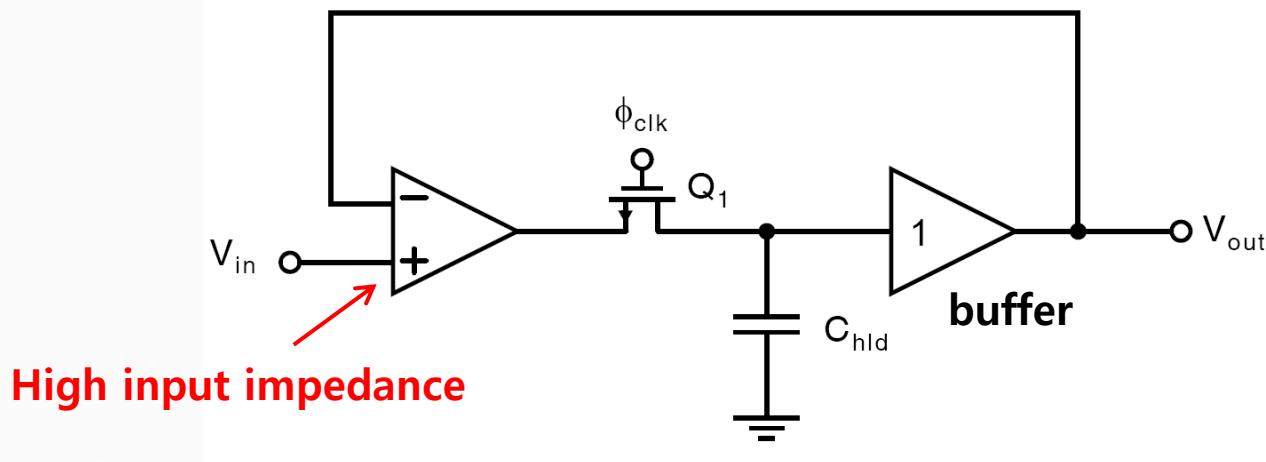


Fig. 11.7 Including an opamp in a feedback loop of a sample-and-hold to increase the input impedance

Advantages

- 1) High input impedance
- 2) Dc offset of buffer divided by loop gain



High input impedance


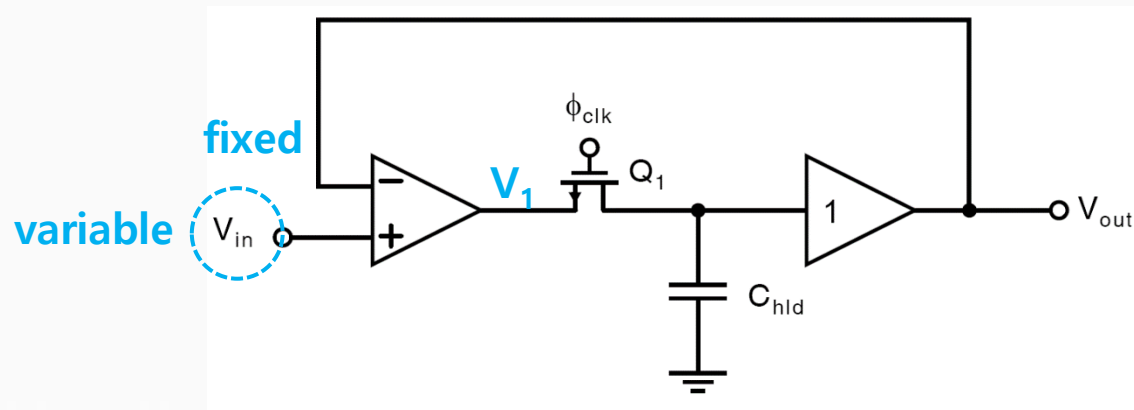


Fig. 11.7 Including an opamp in a feedback loop of a sample-and-hold to increase the input impedance

❖ Operation

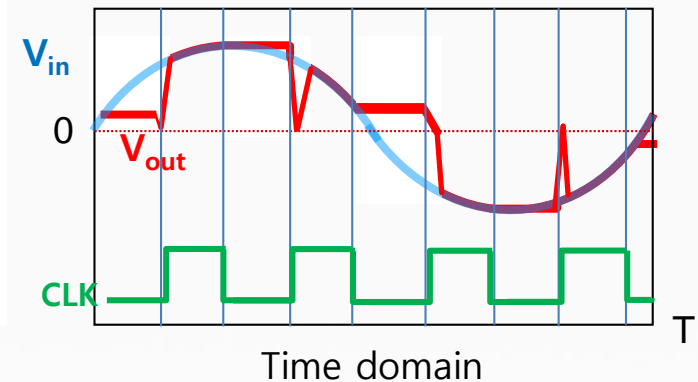

Disadvantages

- 1) In hold mode, V_1 saturate at VDD or GND
- 2) Speed of operation can be degraded
- 3) Power consumption \uparrow




Reduced slew rate requirement

❖ Problem

 1) In hold mode, V_1 saturate at VDD or GND

Closed loop

Not fixed (Hold mode)
→ Follow the V_{in}



❖ Operation

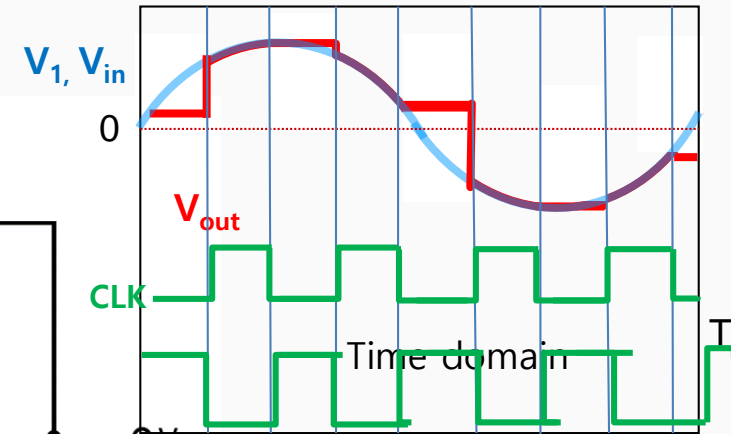


Fig. 11.8 Adding an additional switch to the S/H of Fig. 11.7 to minimize slewing time

Sample-and-hold with an additional switch

- 😊 Minimize the slewing time
- 😞 Charge injection, buffer offset



Input signal independence

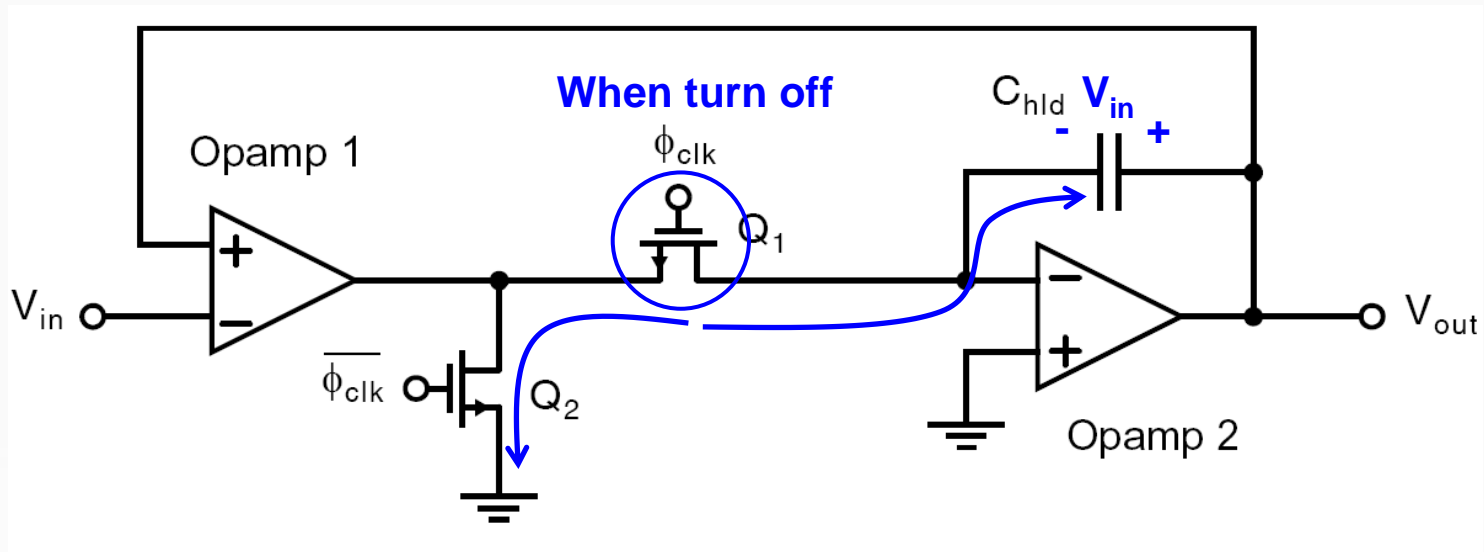


Fig. 11.9 An improved configuration for an S/H as compared to that of Fig. 11.8.

Improved configuration

😊 When hold mode, Input signal is independent
 $C_{\text{hld}} \rightarrow$ charge the V_{in}

😞 **Charge injection**



Example 11.2

Find C_{hld} such that the maximum error in the held voltage is limited to less than 1mV for S/H circuit (Fig. 11.7, 11.9).

$$C_{ox} = 1.92 \text{ fF} / (\mu\text{m})^2, V_m = 0.8\text{V}, (W/L)_1 = (5/0.8) \mu\text{m} / \mu\text{m}, V_{DD} = 2.5\text{V}, V_{in} = \pm 1\text{V}$$

 
 


Fig. 11.7 Including an opamp in a feedback loop of a sample-and-hold to increase the input impedance

Fig. 11.9 An improved configuration for an S/H as compared to that of Fig. 11.8.

$$\Delta V' = \frac{\Delta Q_{C-hld}}{C_{hld}} = -\frac{C_{ox}WL(V_{DD} - V_m - V_{in})}{2C_{hld}} \quad (11.3)$$

$$\Delta V' = \frac{\Delta Q_{C-hld}}{C_{hld}} = -\frac{C_{ox}WL(V_{DD} - V_m)}{2C_{hld}}$$

$$\rightarrow \frac{1.92 \text{ f} \cdot 5 \cdot 0.8 (2.5 - 0.8 - (-1))}{2C_{hld}} \leq 1\text{mV}$$

$$\rightarrow \frac{1.92 \text{ f} \cdot 5 \cdot 0.8 (2.5 - 0.8)}{2C_{hld}} \leq 1\text{mV}$$

$$\rightarrow C_{hld} \geq 10.37 \text{ pF}$$

$$\rightarrow C_{hld} \geq 6.525 \text{ pF}$$

C_{hld} is reduced by 62%



Reduced offset

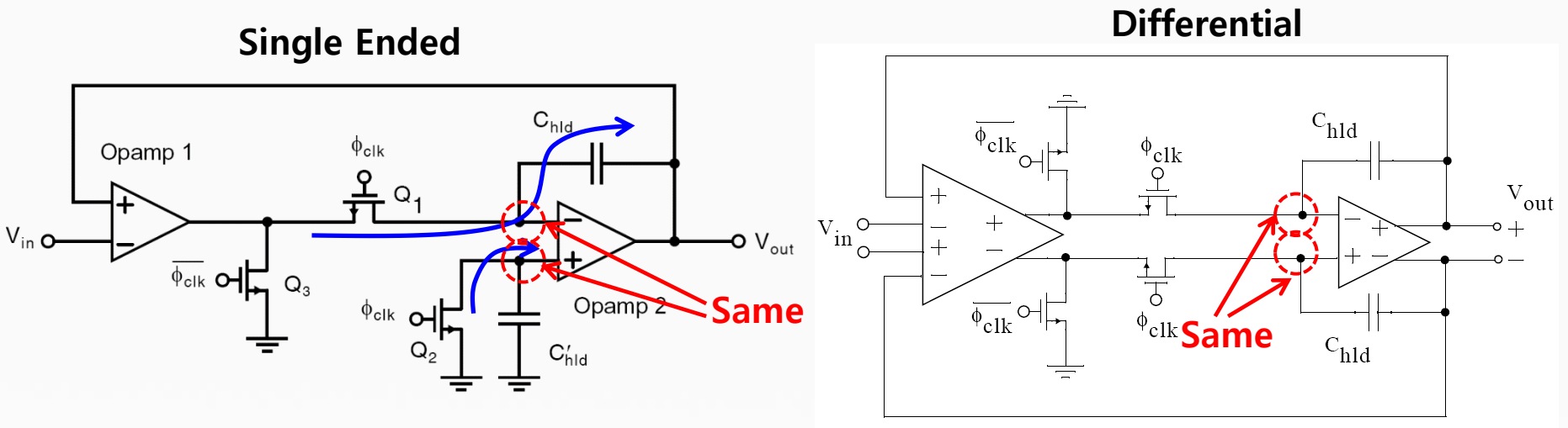


Fig. 11.10 An S/H similar to that of Fig. 11.9, but with clock-feedthrough cancellation circuitry added

Reduced offset circuit

Charge injected by Q_1 matched by Q_2 into C_{hld} or C'_{hld}

